

Mid-term Exam

Date: Feb 24, 2020
Time: 3:00 – 4:00pm

Problem 1 (130 points)

Let us consider an op-amp circuit in Figure 1. We assume that the op-amp has infinite input impedance, zero output impedance, and open-loop transfer function $A(s)$. Figure 2 shows the Bode plot of $A(s)$.

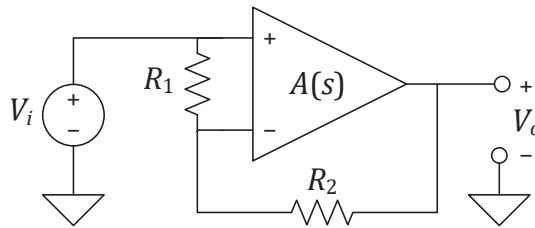


Figure 1: Op-amp circuit for Problem1.

- (a) (20 pt.) Draw a block diagram that shows the feedback relation between the input voltage $V_i(s)$ and output voltage $V_o(s)$.
- (b) (10 pt.) Find the expression for the loop transfer function $L(s)$ in terms of R_1 , R_2 , and $A(s)$.
- (c) (20 pt.) For $R_1 \rightarrow \infty$, $R_2 = 1 \text{ k}\Omega$, and $A(s)$ given in Figure 2, find the gain crossover frequency ω_c and phase margin ϕ_m of $L(s)$.
- (d) (30 pt.) For $R_1 = 1 \text{ k}\Omega$ and $A(s)$ given in Figure 2, find the resistance value R_2 that makes the closed-loop transfer function $G(s) = V_o(s)/V_i(s)$ achieve a -3 dB bandwidth of 100 kHz .
- (e) (20 pt.) What is the dc gain of $G(s)$ designed in part (d)?
- (f) (30 pt.) Suppose $G(s)$ designed in part (d) is excited with an input voltage

$$V_i(t) = \cos(2\pi \times 10^5 t),$$

which is a persistent sinusoid defined for all time including $t < 0$. Find the magnitude M_o and phase ϕ_o of the output voltage

$$V_o(t) = M_o \cos(2\pi \times 10^5 t + \phi_o).$$

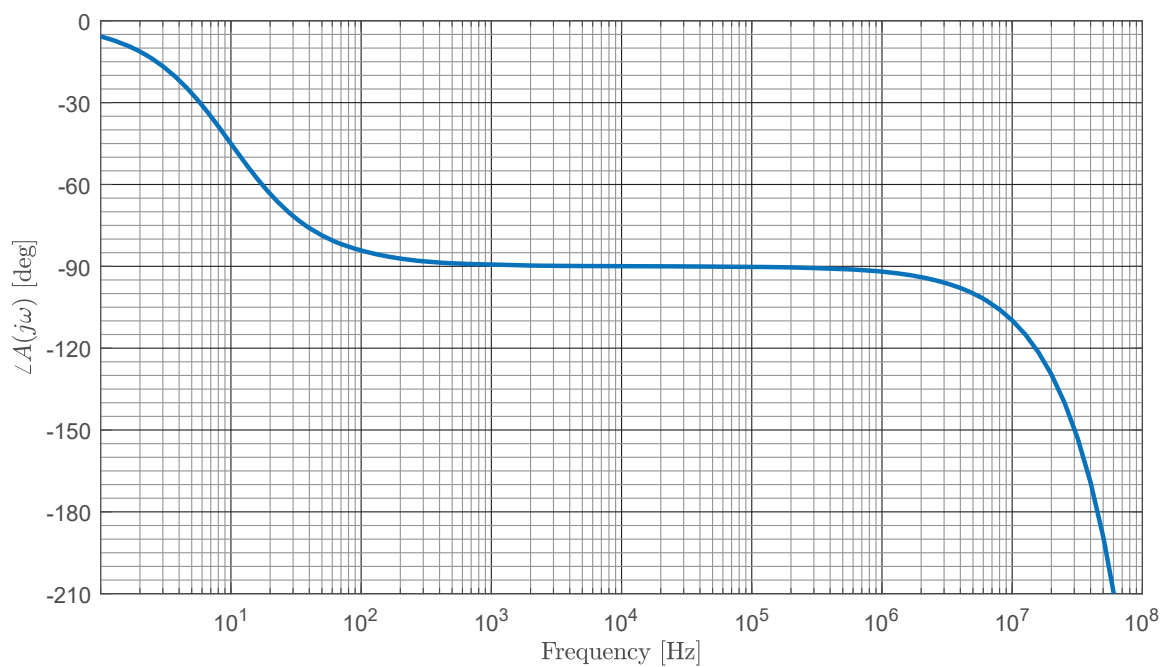
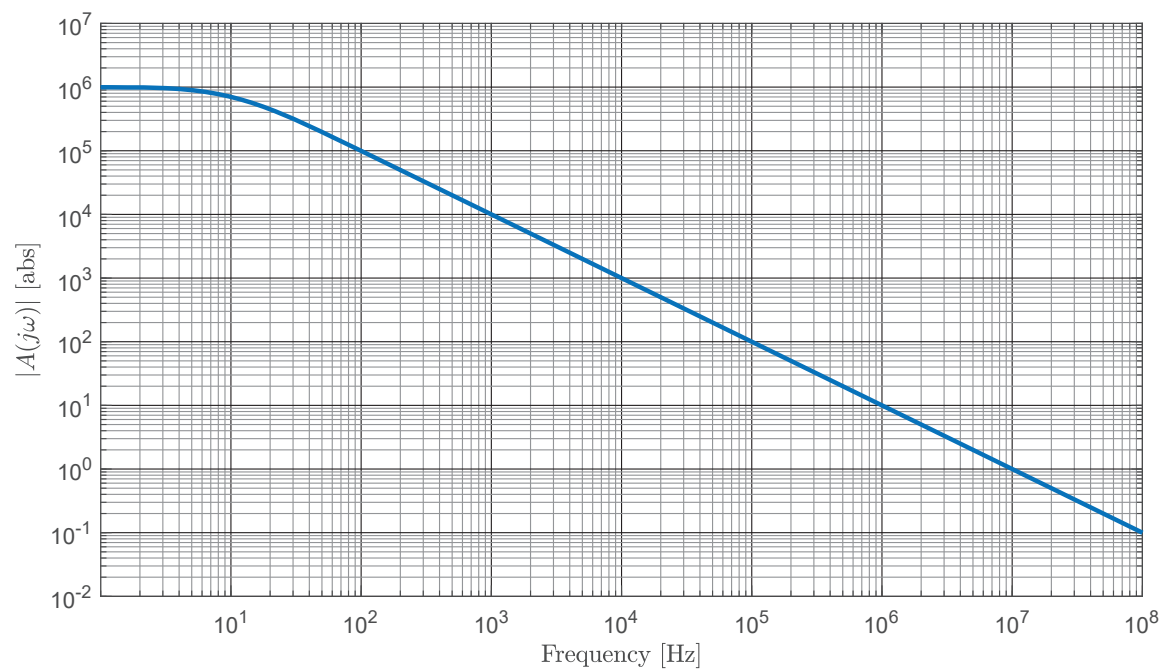


Figure 2: Bode plot of $A(s)$.