


L11 – Differential Measurement

Grounds : A "conductor"


• Symbols



Earth
Mains

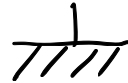

Chassis .

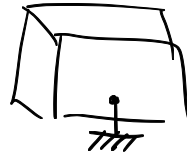

pcb ground .
IC ground .

• "Two Groups"

① Safety ground .

-: Not conducting i during normal ops .

- Role : protect people .



② Signal / power ground

- Conducting i during normal ops.


e.g.) PCB ground plane / trace.

- Role $\begin{cases} \textcircled{1} \text{ voltage : common ref pot. for node voltages.} \\ \textcircled{2} \text{ current : common low-}\omega \text{ path for return currents} \end{cases}$

< Common-mode Voltage >

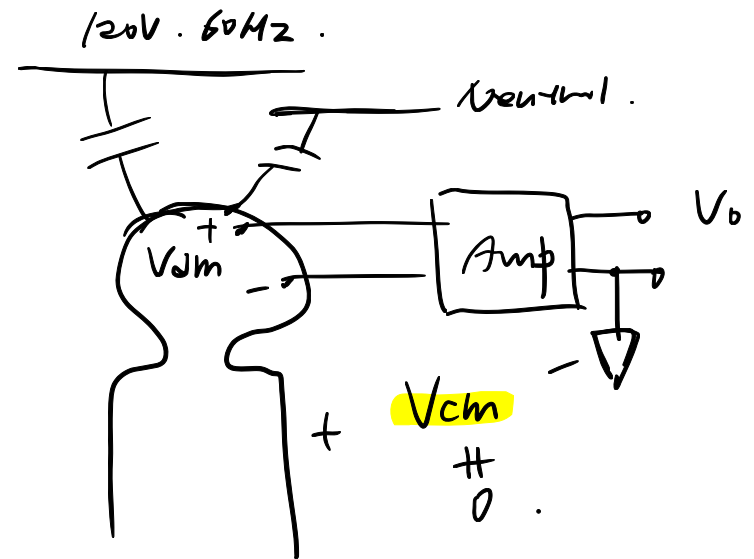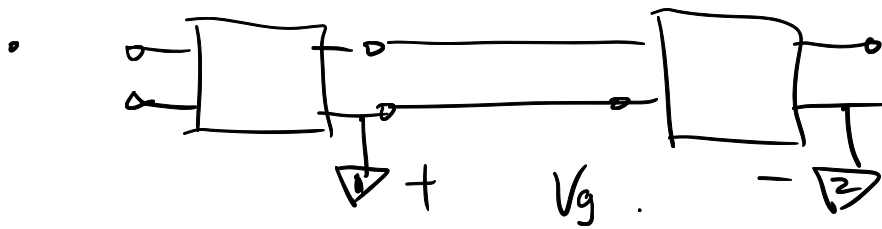

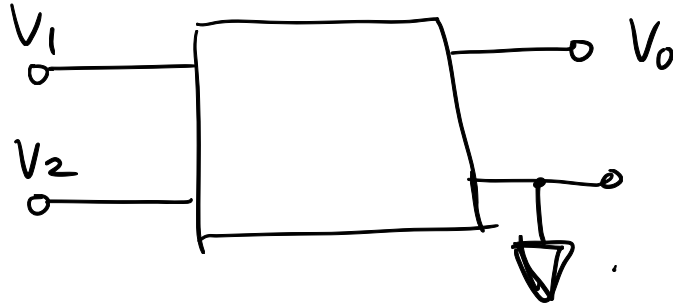- Need an amp : Diff-input . single-ended output
"Differential Amp"



$$\left\{ \begin{array}{l} \text{Common-mode Voltage : } V_{cm} \triangleq \frac{V_1 + V_2}{2} \\ \text{Differential Voltage : } V_{dm} \triangleq V_1 - V_2 \end{array} \right.$$

- In many cases, V_{cm} is unwanted & unknown.
 \Rightarrow we want to reject it


- V_{dm} contains info. but is small. \Rightarrow we want amplification

$$V_o = \uparrow A_{dm} (V_1 - V_2) + \downarrow A_{cm} \left(\frac{V_1 + V_2}{2} \right)$$

Common-mode Rejection Ratio (CMRR)

$$CMRR = \frac{A_{dm}}{A_{cm}} \quad \text{if } A_{cm} \rightarrow 0 \quad \Rightarrow \quad \boxed{CMRR \rightarrow \infty}$$


Diff Amp

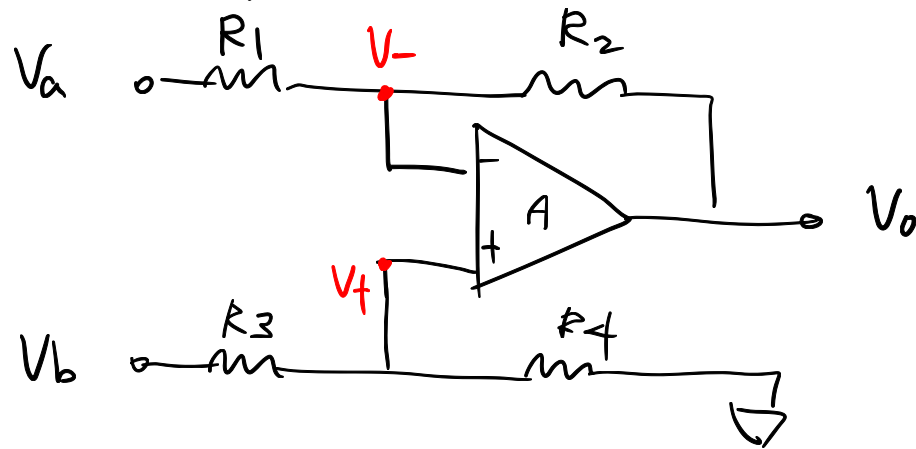

$$V_+ = \frac{R_4}{R_3 + R_4} V_b$$


$$V_- = \frac{R_2}{R_1 + R_2} V_a + \frac{R_1}{R_1 + R_2} V_o$$

• $V_o = A (V_+ - V_-)$

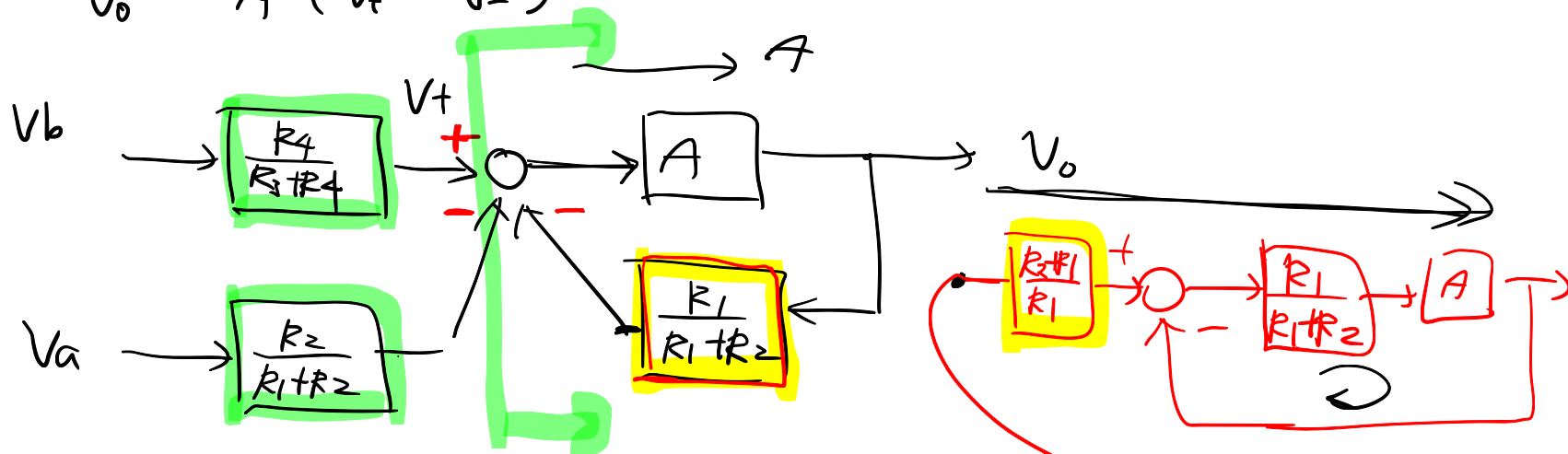

Ⓢ If $\frac{R_4}{R_3} = \frac{R_2}{R_1} \Rightarrow \frac{R_4}{R_3+R_4} = \frac{R_2}{R_1+R_2}$

① $L(s)$
②

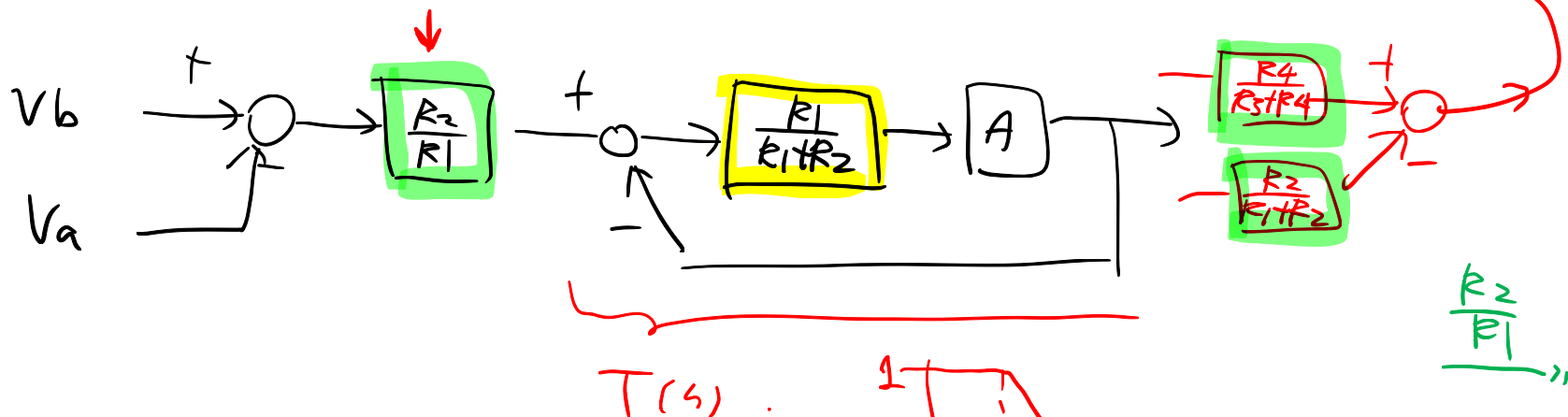

• Below wh : $V_o = \frac{R_2}{R_1} (V_b - V_a)$

$$\begin{aligned}
 V_{cm} &= \frac{1}{2} (V_b + V_a) \quad \Rightarrow \quad V_o = \underbrace{\frac{R_2}{R_1}}_{A_{dm}} \cdot V_{dm} + \underbrace{0}_{A_{cm}} \cdot V_{cm} \\
 V_{dm} &= (V_b - V_a)
 \end{aligned}$$

$$CMRR = \frac{A_{dm}}{A_{cm}} \rightarrow \infty.$$

• $A_{cm} \neq 0$, $CMRR$ is finite.

• $CMRR$ is limited by R . tolerance . (ϵ)


$$\left(CMRR \geq \frac{R_2/R_1 + 1}{4\epsilon} \right)$$

• Diff-Amp . when ① the source Σ is small.


② . V_{cm} is large .

$$\underline{V_{cm} > V_s}$$

• Limitations

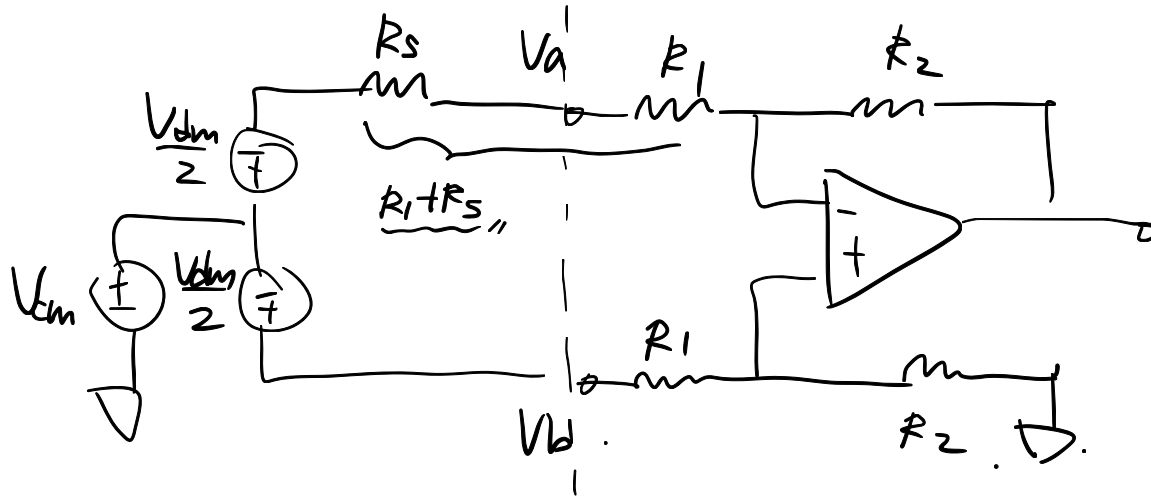

< Buffered Diff - Amp >

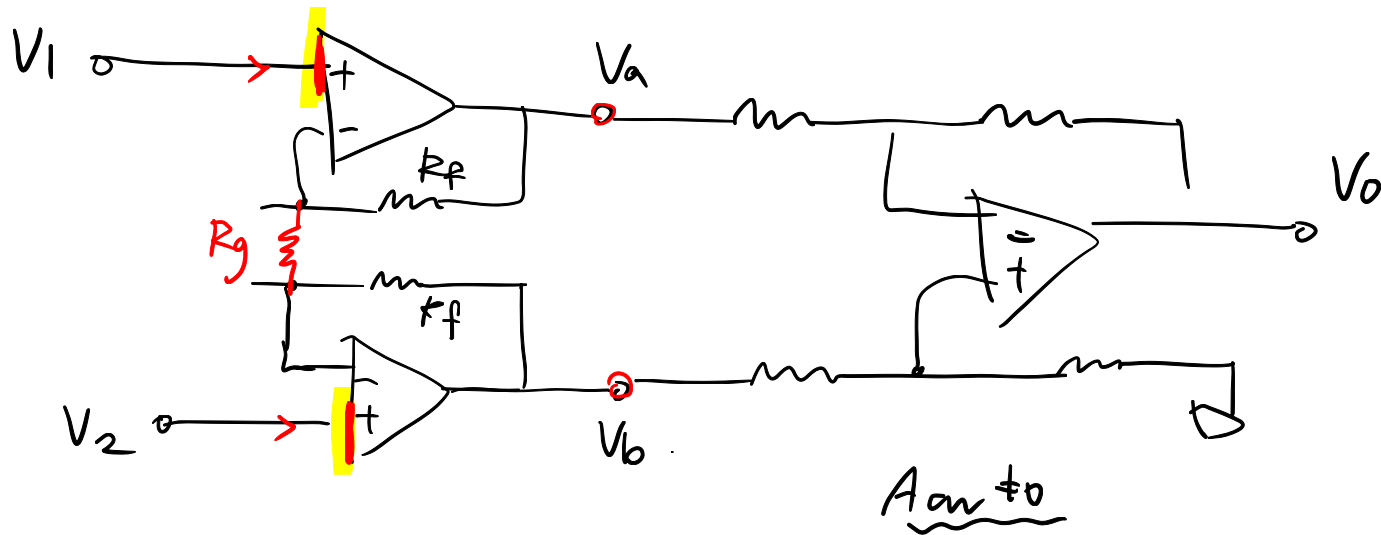

$$V_a = \frac{R_f + R_{g/2}}{R_{g/2}} V_1$$

$$V_b = \frac{R_f + R_{g/2}}{R_{g/2}} V_2$$

$$V_o = \underbrace{A_{dm} \left(\frac{R_f + R_{g/2}}{R_{g/2}} \right)}_{A_{dm}'} (V_2 - V_1) + \underbrace{A_{cm} \left(\text{"} \right)}_{A_{cm}'} \left(\frac{V_2 + V_1}{V_2} \right)$$

$$\therefore CMRR' = \frac{A_{dm}'}{A_{cm}'} = \frac{A_{dm}}{A_{cm}}$$

