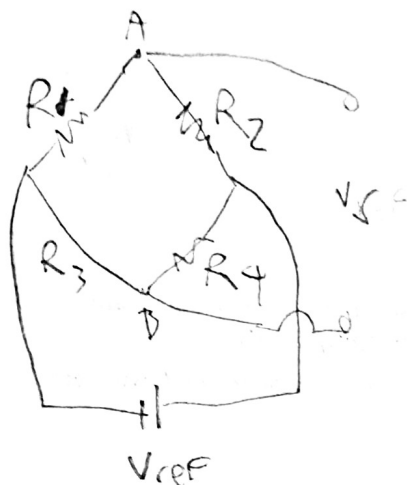


11



$$R_1 = R_r = R(1 + \alpha \Delta T)$$

$$R_2 = R_3 = R_4 = R$$

[Rathannan Prabiray]
#63205165

Wheat stone bridge equation:


$$V_s = V_A - V_B = \frac{R_1 R_4 - R_2 R_3}{(R_1 + R_2)(R_3 + R_4)} V_{ref}$$

Substitute variables and simplify:

$$V_s = \frac{R(1 + \alpha \Delta T)R - R^2}{(R(1 + \alpha \Delta T) + R)(2R)} V_{ref}$$

$$= \left(\frac{R^2}{R^2} \right) \left(\frac{(1 + \alpha \Delta T) - 1}{((1 + \alpha \Delta T) + 1)(2)} \right) V_{ref}$$
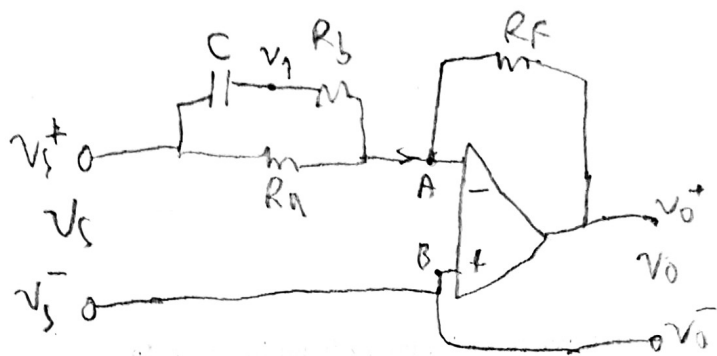
$$= \frac{\alpha \Delta T}{4 + 2\alpha \Delta T} V_{ref}$$



$$v_s = v_s^+ - v_s^-$$

$$v_o = v_o^+ - v_o^-$$

$$v_o^- = v_s^-$$

Properties of ideal op-amp:

$$v_A = v_B = v_s^- = v_o^-$$

← potential at lead are equal

$$i_A = i_B = 0$$

← current at lead = 0

Apply rules & substitute & simplify:

$$\frac{v_s^+ - v_A}{R_b} + \frac{v_s^+ - v_A}{R_a} + \frac{v_o^+ - v_A}{R_f} = 0$$

← junction rule at A

$$v_A = v_B = v_o^- = v_s^-$$

$$\frac{v_1 - v_s^-}{R_b} + \frac{v_s}{R_a} + \frac{v_o}{R_f} = 0 \Rightarrow \underbrace{\frac{v_1 - v_s^-}{R_b}}_{(i)} = \underbrace{-\frac{v_s}{R_a} - \frac{v_o}{R_f}}_{(ii)} \Rightarrow v_1 = +v_s^- - \frac{R_b v_s}{R_a} - \frac{R_b v_o}{R_f}$$

← current series is same


$$C \frac{d(v_s^+ - v_1)}{dt} = \frac{v_1 - v_s^-}{R_b}$$

$$C \frac{d(v_s^+ - (v_s^- - \frac{R_b v_s}{R_a} - \frac{R_b v_o}{R_f}))}{dt} = \frac{-v_s^- - v_o}{R_a} - \frac{v_o}{R_f}$$

← substitute eq (i) & eq (ii) as derived

$$C \frac{d(v_s + \frac{R_b}{R_a} v_s + \frac{R_b}{R_f} v_o)}{dt} = -\frac{v_s}{R_a} - \frac{v_o}{R_f}$$
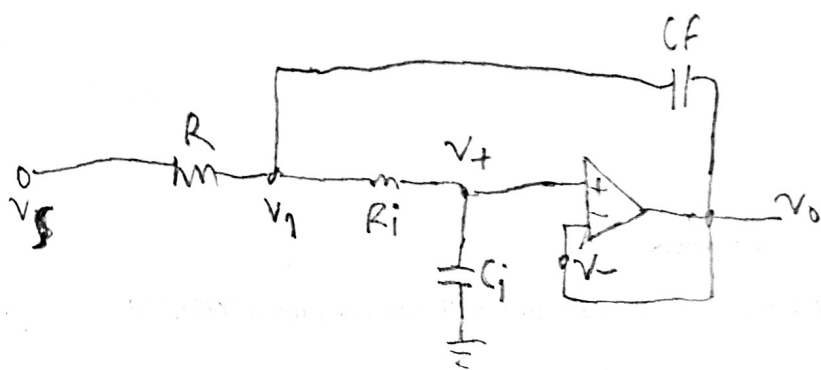
$$C(1 + \frac{R_b}{R_a}) \frac{dv_s}{dt} + \frac{v_s}{R_a} = -\frac{CR_b}{R_f} \frac{dv_o}{dt} - \frac{v_o}{R_f}$$



Op Amp properties:

$$V_- = V_+ = V_0$$

$$i_- = i_+ = 0$$

Apply junction rule:

$$C_i \frac{d(0 - V_+)}{dt} + \frac{V_1 - V_+}{R_i} = 0 \rightarrow V_1 = R_i C_i \frac{dV_+}{dt} + V_+ \quad (i)$$

$$\frac{V_S - V_1}{R} + C_f \frac{d(V_0 - V_1)}{dt} = \frac{V_1 - V_+}{R_i} \quad (ii)$$

Substitute (i) into (ii) to get rid of V_1 , & sub V_- & V_+ with V_0 :

$$\frac{V_S}{R} = \frac{V_1}{R} - C_f \frac{d(V_0 - V_1)}{dt} + \frac{V_1 - V_+}{R_i}$$

$$\frac{V_S}{R} = \frac{R_i C_i \frac{dV_+}{dt} + V_+}{R} + \frac{V_+}{R_i} - C_f \frac{d(V_0 - R_i C_i \frac{dV_+}{dt} - V_+)}{dt} + C_i \frac{dV_+}{dt}$$

$$\frac{V_S}{R} = \frac{R_i C_i}{R} \frac{dV_0}{dt} + \frac{V_0}{R} - \cancel{C_f \frac{dV_0}{dt}} + R_i C_i C_f \frac{d^2 V_0}{dt^2} - \cancel{C_f \frac{dV_0}{dt}} + C_i \frac{dV_0}{dt}$$

$$V_S = R R_i C_i C_f \frac{d^2 V_0}{dt^2} + (R_i C_i + R C_i) \frac{dV_0}{dt} + V_0$$

26 -

Convert to s domain (assume $v_s(0) = v_o'(0) = v_o(0) = 0$):

$$V_s(s) = RR_i C_i C_f s^2 V_o(s) + C_i (R_i + R) s V_o(s) + V_o(s)$$

$$\frac{V_o(s)}{V_s(s)} = \frac{1}{RR_i C_i C_f s^2 + C_i (R_i + R) s + 1} = H(s)$$

$$H(s) \omega = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$H(j\omega) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\omega_n^2 = \frac{1}{RR_i C_i C_f}$$

$$\zeta = \frac{C_i (R_i + R)}{2} \sqrt{RR_i C_i C_f}$$

$$H(j\omega) = \frac{\omega_n^2}{(\omega_n^2 - \omega^2) + j2\zeta\omega_n \omega} = \frac{1}{(1 - \frac{\omega^2}{\omega_n^2}) + j2\zeta\frac{\omega}{\omega_n}}$$

$$|H(j\omega)| = \frac{1}{\sqrt{(1 - \frac{\omega^2}{\omega_n^2})^2 + (2\zeta\frac{\omega}{\omega_n})^2}}$$

Band width $\rightarrow |H(j\omega)| = \frac{|H(0)|}{\sqrt{2}}$, get ω

$$|H(0)| = \frac{1}{\sqrt{1+0}} = 1$$

$$\frac{|H(0)|}{\sqrt{2}} = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{(1 - \frac{\omega^2}{\omega_n^2})^2 + (2\zeta\frac{\omega}{\omega_n})^2}}$$

$$2 = 1 - \frac{2}{\omega_n^2}(\omega^2) + \frac{1}{\omega_n^4}(\omega^4) + \frac{2\zeta^2}{\omega_n^2}(\omega^2)$$

$$0 = (\omega^4 + (-\omega_n^2 2 + \omega_n^2 4\zeta^2)\omega^2 - \omega_n^4)$$

$$\omega^2 = \frac{-(-\omega_n^2 2 + \omega_n^2 4\zeta^2) \pm \sqrt{(-\omega_n^2 2 + \omega_n^2 4\zeta^2)^2 + 4\omega_n^4}}{2\omega_n^2}$$

$$= \frac{(-(-2 + 4\zeta^2) \pm \sqrt{(-2 + 4\zeta^2)^2 + 4})}{2} \omega_n^2$$

$$\omega^2 = \left((1 - 2\zeta^2) \pm \sqrt{4\zeta^2 - 4\zeta + 2} \right) \omega_n^2$$

$$= \frac{1}{R R_i C_i C_f} \left(\left(1 - 2 \frac{C_i^2 (R + R_i)^2 (R R_i C_f)}{4} \right) \pm \sqrt{4 \frac{C_i^2 (R + R_i)^2 R R_i C_f}{4} - \frac{4}{2} C_i (R + R_i) \sqrt{R R_i C_i C_f} + 2} \right)$$

$$2c. \tau_s = \frac{1}{\zeta \omega_n} = \frac{2}{C_i (R + R_i)}$$

$$2d. C_i = \frac{2}{\zeta (R + R_i)} = \frac{1}{11} F$$

$$\omega_n^2 = \frac{1}{C_f (K \Omega) (10 K \Omega) \frac{1}{11} F}$$

$$= \frac{1.1 \times 10^{-6} F \left(\frac{rad}{s} \right)^2}{C_f}$$

Bandwidth should exceed resonance $\rightarrow \omega^2 = \omega_n^2$

$$\omega^2 = \omega_n^2 = \frac{1.1 \times 10^{-6}}{C_f} = \frac{1}{R R_i C_i C_f} (\dots)$$

$$0 = -1 + \left(1 - 4.545 \times 10^{11} C_f \pm \sqrt{7.513 \times 10^{23} C_f - 476731 \sqrt{C_f} + 2} \right)$$

Use solver

$$x = \sqrt{C_f} = .00190, .0019 \rightarrow C_f = 3.61 \times 10^{-6} F$$

According to Nyquist frequency theory, sampling frequency should be double operating frequency. Assume operate at bandwidth (max operable frequency).

$$\omega = \omega_n = \sqrt{\frac{1}{3.61 \times 10^{-6} (1000) (10000) \left(\frac{1}{11} \right)}} = 3.282 \frac{rad}{s} \rightarrow f_c = .52 Hz$$

$$f_s = 2f_c = 1.044 Hz$$

3a. $p=1 \rightarrow$ ignored

$$J_e = J_m + J_{gm} + (J_{gp} + J_p) + m r_p^2$$

b. $T = J \alpha \rightarrow (\alpha [\text{rad/s}^2]) \left(\frac{1 \text{ rev}}{2\pi \text{ rad}} \right) \left(\frac{60 \text{ s}}{\text{min}} \right) = \alpha \left[\frac{\text{rpm}}{\text{s}} \right]$

$$\eta T_m = J_e \alpha + m r_p^2 (\alpha + g/r_p)$$

$$T_m = \frac{\alpha}{\eta} (J_m + J_{gm} + J_{gp} + J_p + m r_p^2) + \frac{m r_p g}{\eta}$$

has to overcome gravity term,
or load will yank on motor

c. $\omega = v_{\max} / r_p$

$$= \frac{5}{.4} \frac{\text{rad}}{\text{s}} \left(\frac{\text{rev}}{2\pi \text{ rad}} \right) \left(\frac{60 \text{ s}}{\text{min}} \right)$$

$$= 119.37 \text{ rpm}$$

\rightarrow all 3 motors can operate at this rpm

$$\alpha = \frac{v_{\max} - v_0}{T - T_0}$$

$$= \frac{(51.4 - 0) \text{ rad/s}}{.25 - 0}$$

$$= 62.5 \text{ rad/s}^2$$

$$T_m = \frac{62.5}{.8} (J_m + 4 \times 10^{-2} + 7 \times 10^{-2} + 15 \times 10^{-2} + 15 \times 0.4^2) + \frac{15 \times 0.4 \times 9.81}{.8}$$

$$= 78.125 \frac{\text{Nm}}{\text{s}^2} J_m + 281.4 \text{ Nm}$$

Motor	$J_m (\text{kgm}^2)$	$T_m (\text{Nm})$	T at 119.5 rpm	$T_m < T_{\text{at } 120} ?$
1	6×10^{-2}	286.15	24 Nm	X
2	8×10^{-2}	287.4	42 Nm	X
3	11×10^{-2}	290.0	68 Nm	X

None suitable, load too large