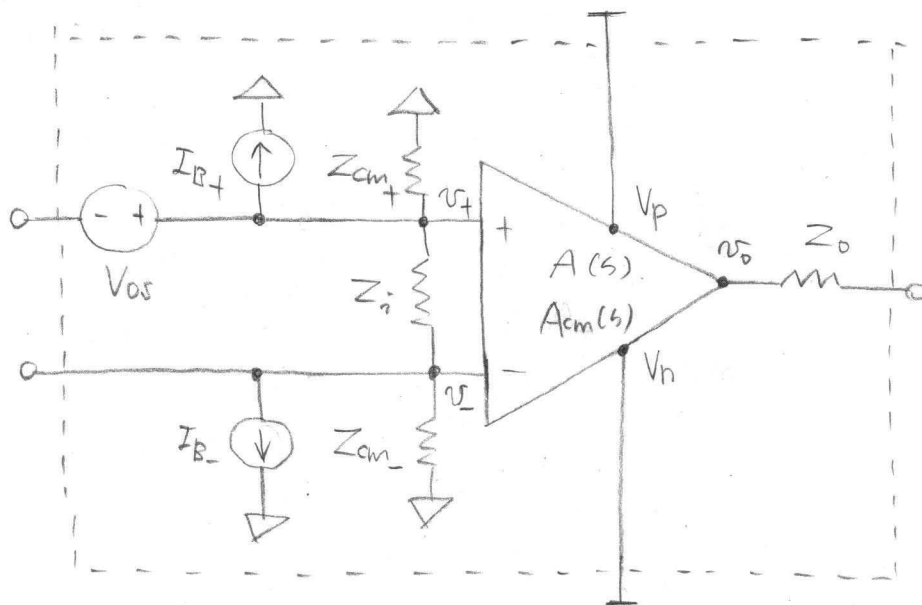


< Non idealities of Op-Amps & In-Amps. >

So far, we studied various non idealities of op-amps / In-amps.

Today's lecture will summarize those, and introduce some more.



Note:


Many of them can be modeled as linear elements.

① Voltage Gains & Voltage Ranges.

$$v_o = A(v_+ - v_-) + A_c \left(\frac{v_+ + v_-}{2} \right) + \underbrace{A_p \Delta V_p + A_n \Delta V_n}_{= A_s \Delta V_s \text{ if perturbed symmetrically.}}$$


- open-loop gain $A(j\omega)$
- Common-mode rejection ratio $CMRR = \frac{A(j\omega)}{A_c(j\omega)}$
- power-supply rejection ratio $\begin{cases} PSRR_+ = \frac{A(j\omega)}{A_p(j\omega)} \\ PSRR_- = \frac{A(j\omega)}{A_n(j\omega)} \end{cases}$
- Input voltage range : $V_{min} < v_+, v_- < V_{max}$
- Output voltage range : $V_{min} < v_o < V_{max}$ → Cause "Clipping"

② Input offset voltage (V_{os})

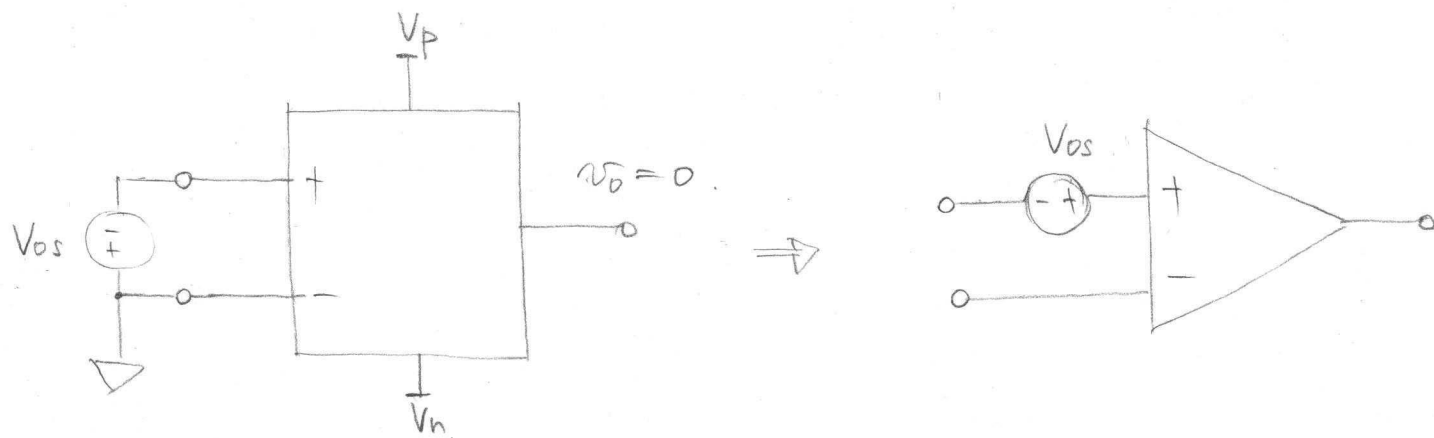

- Actual op-amp requires small non-zero differential input voltage to make the output voltage zero.
- This can be modeled as a small internal voltage V_{os} opposing the external voltage.
- It occurs due to mismatches in the internal circuits.
- It can saturate op-amp circuits with high DC gain.


Example Microphone Amplifier

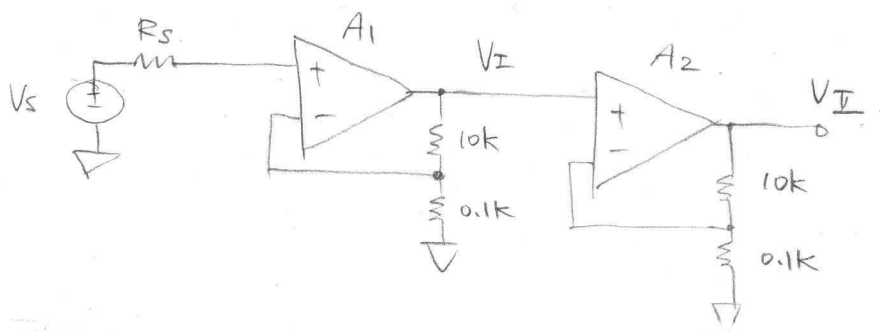

- If A_1 has $V_{os} = 2\text{mV}$ $V_I = 200\text{mV}$ $V_{II} = 20\text{V}$
Saturates!



- Some op-amps provide pins for trimming V_{os}
- Implementing AC coupling (e.g. 1st order high-pass filter) between two stages can resolve the issue.

③ Input Bias Current: (I_{B+} , I_{B-})


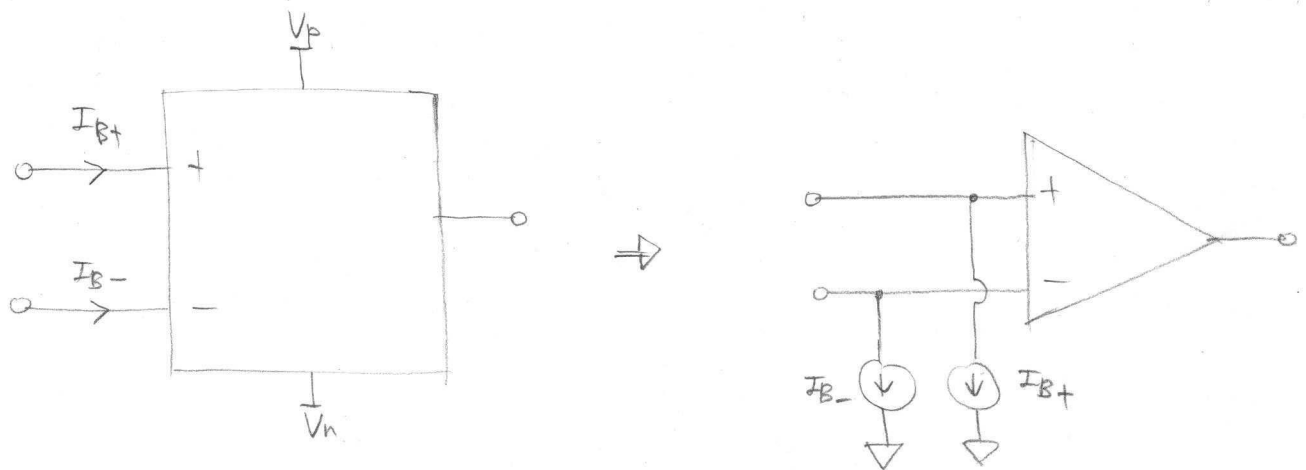


- Input terminals of an actual op-amp must draw (or source) small DC currents.
- For example, those op-amps with bipolar transistors at the input stage, input bias currents correspond to the base currents.
- If circuits around an op-amp cannot conduct I_B , the op-amp does not work. (It cannot breathe!)

Example: Thermocouple Amplifier

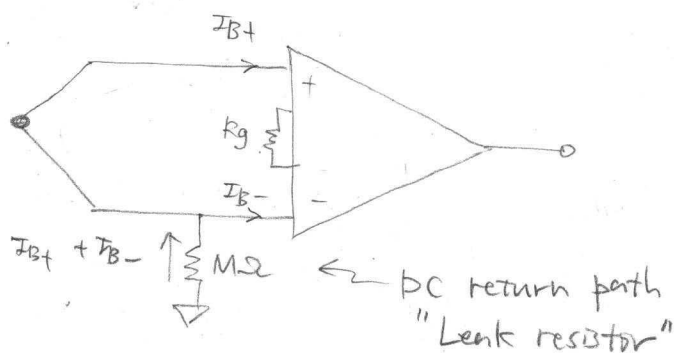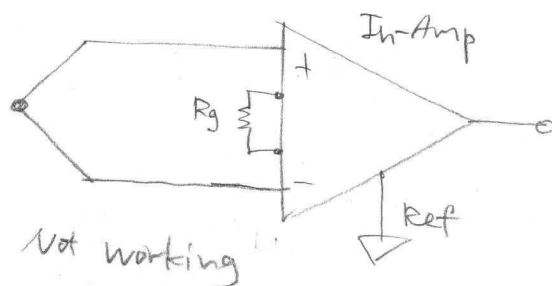

Example: AC-coupled Amplifier

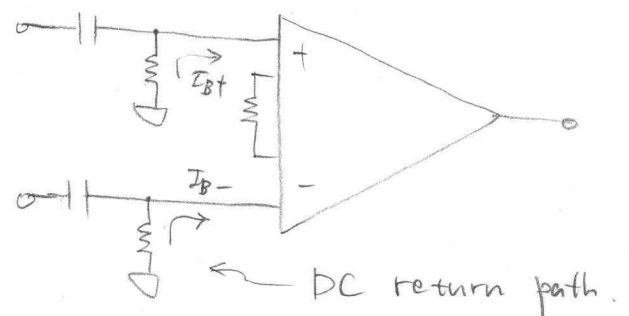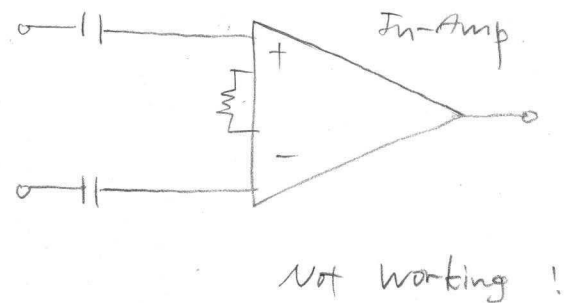

- Bias current compensation

- Many of modern op-amps have built-in circuits that provide the bias currents internally. (e.g. op 27)
- These are called bias current compensated op-amps.
- Therefore, the external bias current requirements are very low.
- Such op-amps can be quickly identified from the datasheet by looking at the " \pm (plus and minus)" sign for I_B .

④ Input Offset Current (I_{OS})


- A small difference between I_{B+} and I_{B-} is called "Input offset current" $I_{OS} = I_{B+} - I_{B-}$

- For those op-amps with bias current compensation, the values for I_B and I_{OS} are the same or similar in the order of magnitude.

⑦ Impedances

• Output Impedance : Z_o

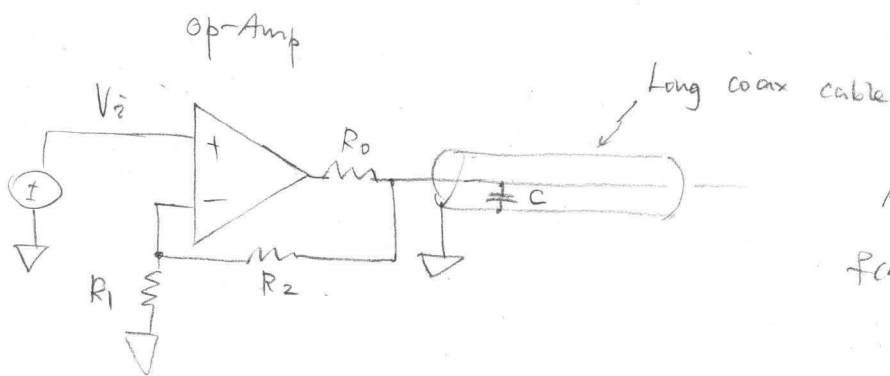- In most cases, Z_o is resistive (R_o) and small.
- It can affect stability when driving a capacitive load. (e.g. coax cable capacitance), as it forms an RC low-pass filter in the feedback path.




Assuming $R_1, R_2 \gg R_o$

$$f(s) = \underbrace{\left(\frac{1}{R_o s + 1} \right)}_{\text{phase lag in the loop}} \cdot \frac{R_1}{R_1 + R_2}$$

• Input Impedance: Z_i , Z_{int} , and Z_{in}

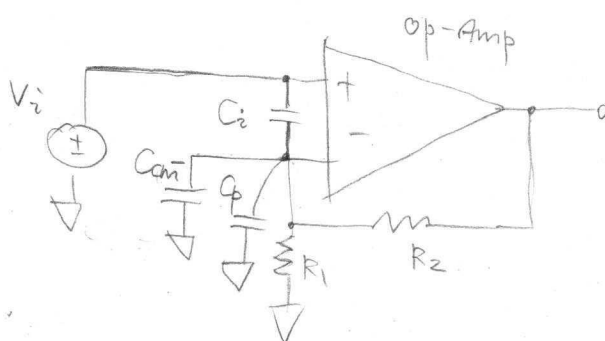- In most cases, these are large resistances (M Ω - G Ω) in parallel with small capacitances.
- The intrinsic values (as in the datasheet) can be affected by parasitic resistance/capacitances between the PCB and chip. (leakage path)
- The net input capacitance C_{net} can affect the loop stability.



$$C_{net} = C_i + C_{in} + C_p$$

$$f(s) = \frac{R_1}{R_1 + R_2} \underbrace{\left(\frac{1}{R_1 R_2 C_{net} s + 1} \right)}_{\text{phase lag in the loop}}$$


- Z_{cm+} and Z_{cm-} are important for In-amps.

They need to be 1) High and


2) Well-matched ($Z_{cm+} \approx Z_{cm-}$)

for a good interference rejection.


Example Biopotential Amplifier

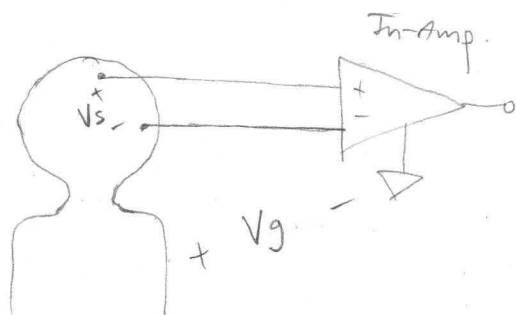

⇒ Simplified Model

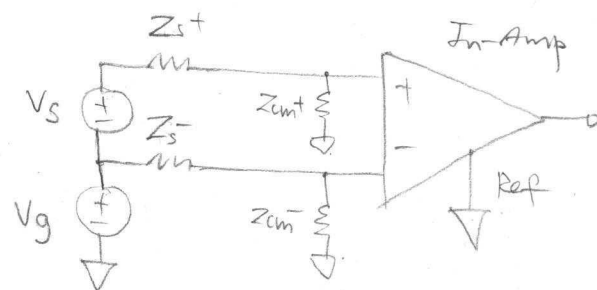

Consider a case where $V_d = 0$.

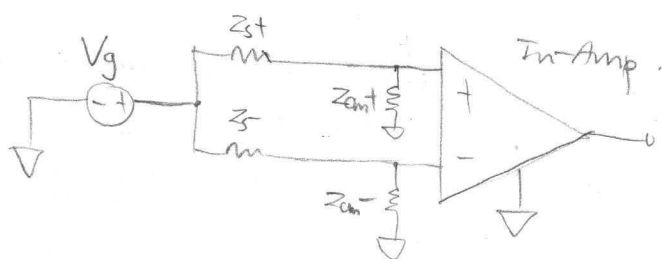

Seen from the in-amp:

$$V_{cm} = \frac{1}{2} (V_+ + V_-)$$

$$V_{dm} = V_+ - V_-$$

i) $Z_{s+} = Z_{s-}$ (matched) , $Z_{cm+} = Z_{cm-}$ (matched)

$$V_+ = \frac{Z_{cm}}{Z_s + Z_{cm}} V_g$$

$$V_- = \frac{Z_{cm}}{Z_s + Z_{cm}} V_g$$

$$\Rightarrow \boxed{V_+ = V_-}$$

$$V_{dm} = 0$$

$$V_{cm} = \frac{Z_{cm}}{Z_s + Z_{cm}} V_g$$

↳ will be attenuated by A_{cm}

ii) $Z_{s+} \neq Z_{s-}$ (mismatched) $Z_{cm+} = Z_{cm-}$ (matched)

$$\boxed{V_+ \neq V_-}$$

$V_{dm} = V_+ - V_-$ will be amplified through A_{ds} .

iii) $Z_{s+} \neq Z_{s-}$ (mismatch), $Z_{cm+} = Z_{cm-}$ (matched) and $Z_{cm} \gg Z_s$ ★

$$V_+ = \frac{Z_{cm}}{Z_{s+} + Z_{cm}} V_g \approx V_g$$

$$V_- = \frac{Z_{cm}}{Z_{s-} + Z_{cm}} V_g \approx V_g$$

$$\Rightarrow \boxed{V_+ \approx V_-}$$

Large Z_{cm} can accommodate mismatch between Z_{s+} & Z_{s-}

⑥ Slew Rate (SR)

$$\max \left\{ \frac{dv_o}{dt} \right\} \leq SR$$

Slew rate effectively limits the "power bandwidth"

$$\text{Let } v_o(t) = V_o \cdot \sin \omega t, \quad V_o = \text{const.}$$

$$\frac{dv_o}{dt} = \omega V_o \cdot \cos \omega t$$

$$\max \left\{ \frac{dv_o}{dt} \right\} = \omega V_o \leq SR$$

$$\therefore \omega \leq \frac{SR}{V_o} \quad \text{to avoid distortion.}$$

$$\therefore \omega_{\max} = \frac{SR}{V_o} \quad \text{"power bandwidth"}$$

For an op-amp generating a sinusoidal output with a fixed amplitude V_o , the maximum frequency it can deliver without distorting the output is called power bandwidth. $\therefore \omega_{\max} = \frac{SR}{V_o}$

(Perhaps) Better Illustration .

