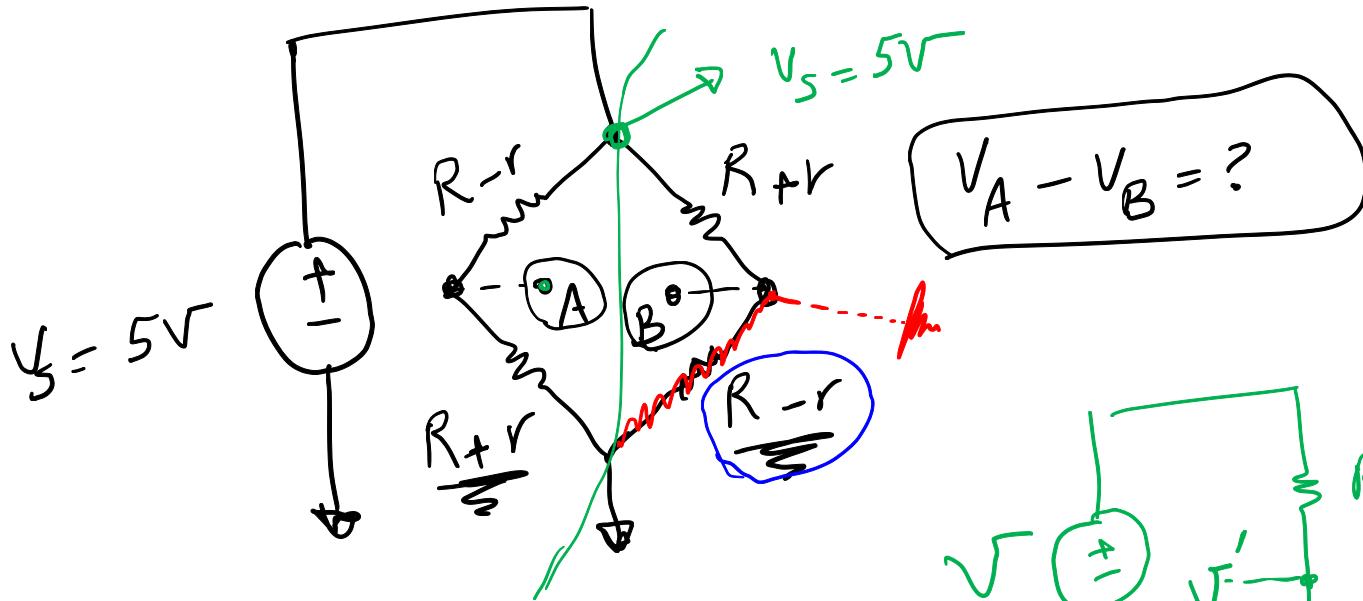



Let us consider a full-bridge strain gauge circuit in Figure 4. Here, $V_s = 5\text{V}$ is the supply voltage, R is the nominal resistance, and r is the resistance change due to the strain.

- (a) (10 pt.) Find the expression for the voltage between the output terminals A and B in terms of R and r .



$$V_A = \frac{R+r}{R-r+R+r} \times V_s$$

$$= \frac{R+r}{2R} V_s$$

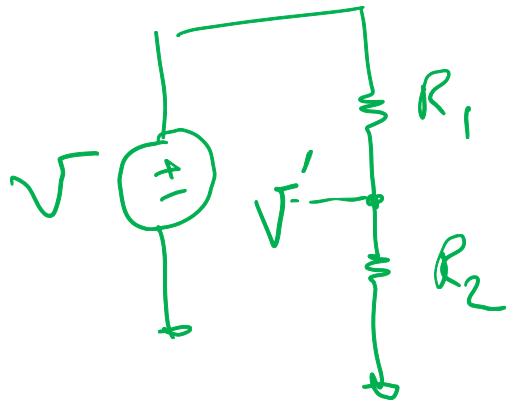


$$V' = \frac{R_2}{R_1 + R_2} \times V$$

$$V_B = \frac{R-r}{R-r+R+r} = \frac{R-r}{2R} V_s$$

$$\underline{V_A - V_B} = \left(\frac{R+r}{2R} - \frac{R-r}{2R} \right) V_s = \frac{r}{R} V_s = \frac{r}{R} 5\text{V}$$

\boxed{R}

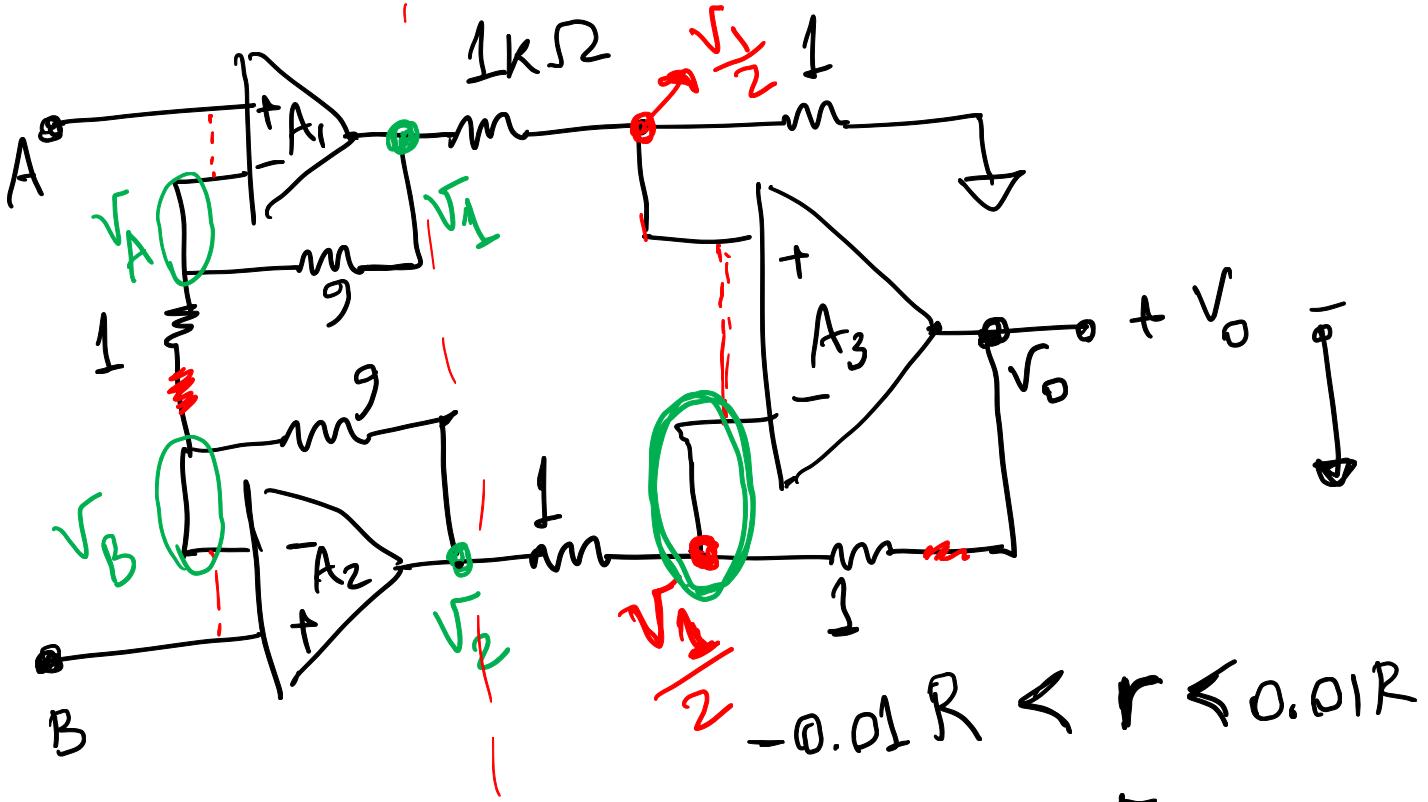- (b) (30 pt.) The output terminals A and B of the bridge circuit are connected to the input terminals A and B of the op-amp circuit in Figure 5. The grounds of the two systems are also connected together. Suppose the op-amps are ideal (i.e., infinite input impedance, zero output impedance, and infinite open-loop gain) and do not saturate, and r varies such that $-0.01R < r < 0.01R$. Find the range of the output voltage V_o .



KCL ∇_A :

$$\frac{V_A - V_B}{1} + \frac{V_A - V_1}{9} = 0 \quad \left. \begin{array}{l} \\ \end{array} \right\} C-1$$

KCL ∇_B :

$$\frac{V_B - V_A}{1} + \frac{V_B - V_2}{9} = 0$$

$$(V_A - V_B) - (V_B - V_A) + \frac{V_A - V_1}{9} - \frac{V_B - V_2}{9} = 0$$

$$2(V_A - V_B) + \frac{1}{9}(V_A - V_B) + \underbrace{\frac{1}{9}(V_2 - V_1)}_{\text{arrow}} = 0$$

$$\frac{19}{9}(V_A - V_B) = \frac{1}{9}(V_1 - V_2)$$

$$V_1 - V_2 = 19(V_A - V_B)$$

KCL for negative part of A_3 :

$$\frac{\frac{V_1}{2} - V_2}{1} + \frac{\frac{V_1}{2} - V_0}{1} = 0$$

$$\Rightarrow V_1 - V_2 - V_0 = 0 \Rightarrow V_0 = V_1 - V_2$$

$$V_0 = V_1 - V_2 = 19(V_A - V_B)$$


$$\text{strain gauge: } V_A - V_B = 5 \frac{r}{R}$$

$$-0.01R < r < 0.01R \Rightarrow -0.01 < \frac{r}{R} < 0.01 \Rightarrow$$

$$-0.05 < \frac{5r}{R} < 0.05 \xrightarrow{(\times 19)} -0.95 < 19(V_A - V_B) < 0.95$$

$$\Rightarrow -0.95 < V_0 < 0.95$$

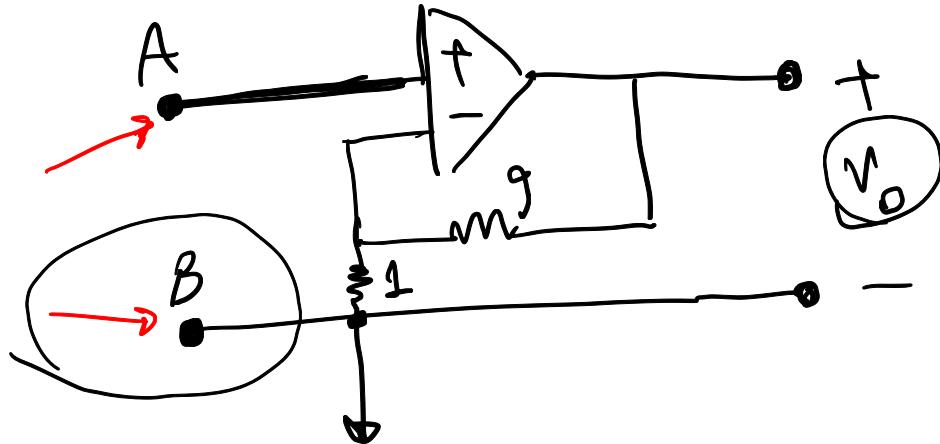- (c) (30 pt.) The output terminals A and B of the bridge circuit are connected to the input terminals A and B of the op-amp circuit in Figure 7. The grounds of the two systems are also connected together. Suppose the op-amp is ideal (i.e., infinite input impedance, zero output impedance, and infinite open-loop gain) and does not saturate, and r varies such that $-0.01R < r < 0.01R$. Find the range of the output voltage V_o .



$$f = \frac{1}{1+g} = \frac{1}{10}$$

$$G(s) = \frac{A(s)}{1 + A(s)f} \rightarrow G = \frac{1}{f} = 10$$

$$V_o = 10 V_A \quad V_A = \left(\frac{R+r}{2R}\right) 5 = \left(1 + \frac{r}{R}\right) 2.5$$

$$-0.01R < r < 0.01R \Rightarrow -0.01 < \frac{r}{R} < 0.01$$

$$\Rightarrow 0.99 < \left(1 + \frac{r}{R}\right) < 1.01 \Rightarrow 2.475 < 2.5 \left(1 + \frac{r}{R}\right) < 2.525$$

$$24.75 < V_o < 25.25$$