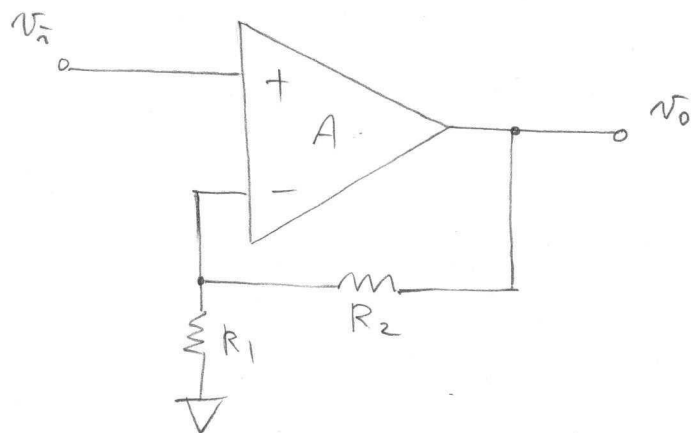


# < Operational Amplifier - Dynamic Model >


Minkyun Noh.  
2020/1/20.



Assume:

$$\begin{cases} Z_i \rightarrow \infty \\ Z_o \rightarrow 0 \end{cases}$$

①  $A(s) = \frac{\omega_0}{s}$

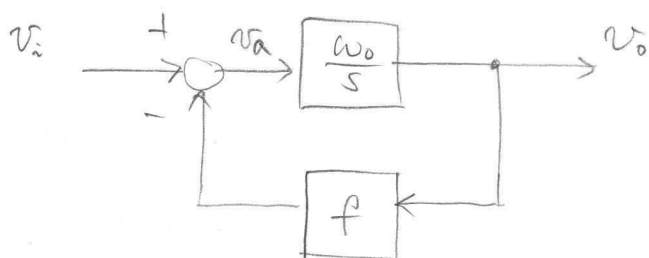

- Note that  $|A| \rightarrow \infty$  as  $\omega \rightarrow 0$ .
- $\omega_0$  is a characteristic frequency of an op-amp.
- For op27.  $|A(f)| \approx 60 \text{ dB} = 10^3$   
 $f = 10 \text{ kHz}$

$$\left| \frac{\omega_0}{2\pi \cdot 10^4} \right| = 10^3 \quad \therefore \omega_0 \approx 2\pi \cdot 10^7 \text{ [rad/s]}$$


$$f_0 \approx 10 \text{ MHz}$$

$$G(s) = \frac{\omega_0}{s} \frac{1}{1 + \frac{\omega_0}{s} f}$$

$$= \frac{\omega_0}{s + \omega_0 f} \quad \text{"Evens Form"} \rightarrow \text{Directly shows pole location}$$

$$= \frac{1}{f} \left( \frac{1}{\frac{1}{\omega_0 f} s + 1} \right) \quad \text{"Bode Form"} \rightarrow \text{Directly shows DC gain \& time constant.}$$


- Impulse Response ( $v_i = \delta(t)$ )

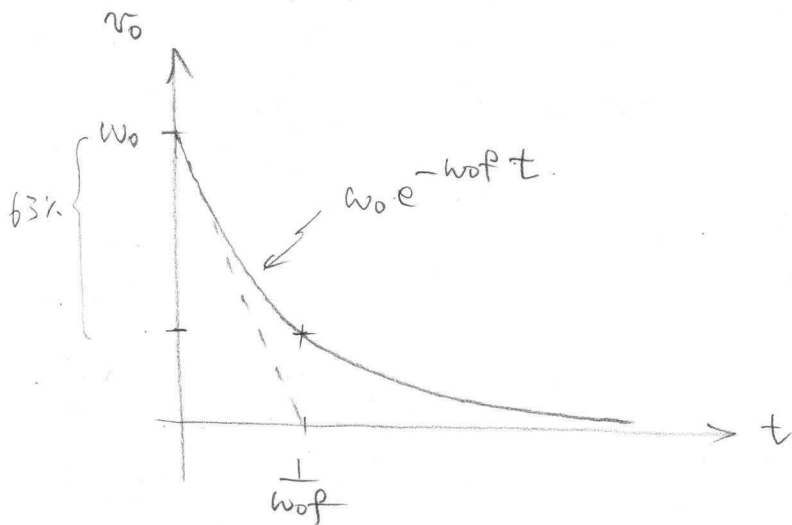


- The block diagram helps us understand the initial resp.

e.g. Impulse, step.

- Step Response ( $v_i = u(t)$ )

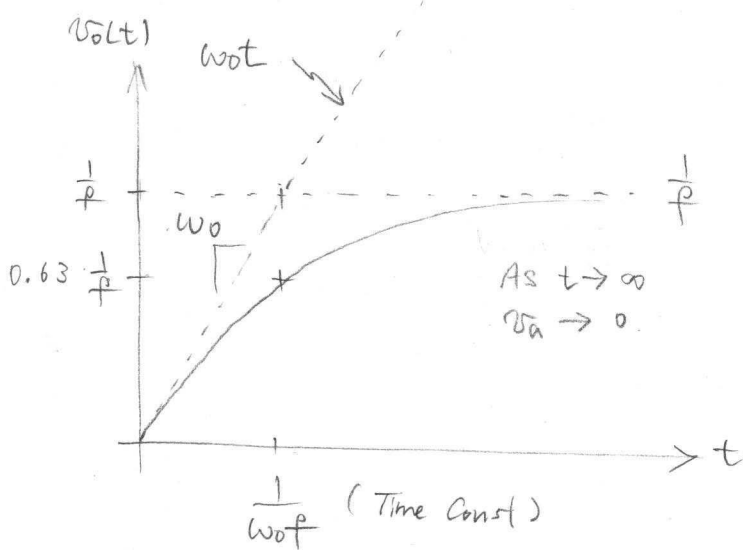

- Bode Plot of  $G(s)$

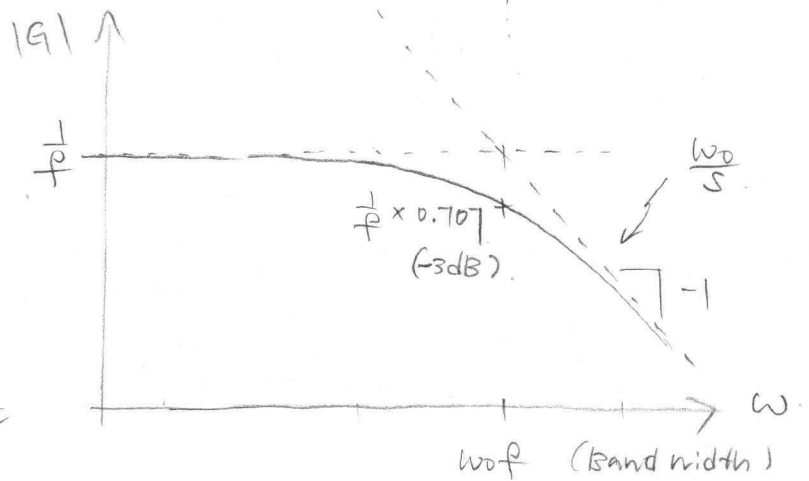

- Note the "duality" between the step resp. & Freq. resp.

Time constant :  $\frac{1}{w_o f}$   
Initial response :  $w_o t$   
Final value :  $\frac{1}{p}$

Bandwidth :  $w_o f$

High-freq response :  $\frac{w_o}{s}$

DC gain :  $\frac{1}{p}$



- Note the trade-off between DC gain & Bandwidth

Gain-bandwidth product =  $(\frac{1}{p}) \cdot (w_o f) = w_o$  (for non-invt amplifier)
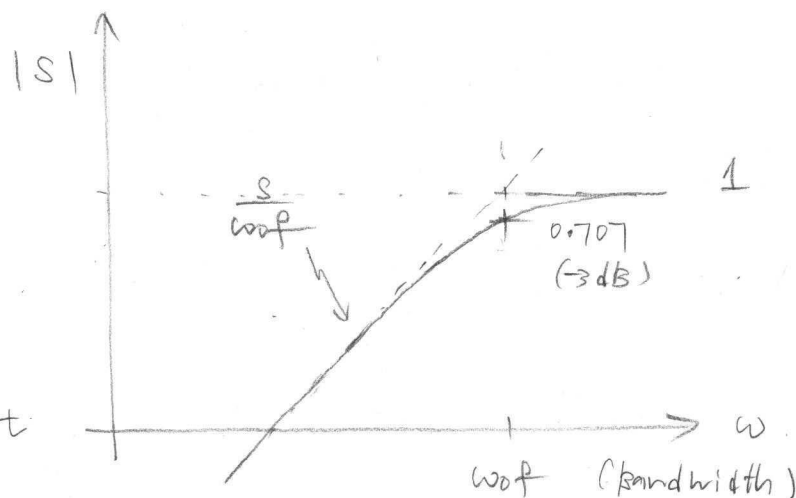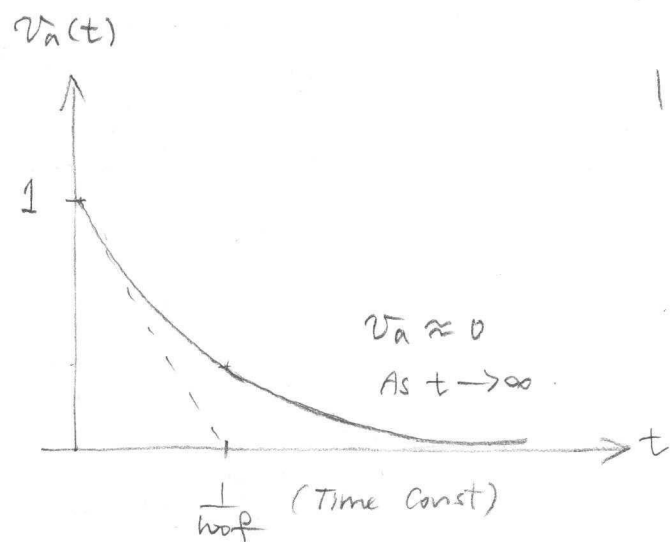
# • Error Dynamics

$$\frac{V_a}{V_i} = S(s) = \frac{1}{1 + \frac{G_{20}}{s} \cdot f} = \frac{s}{s + \omega_{of}} \quad \begin{matrix} \text{The same pole location} \\ \therefore \text{the same time const.} \end{matrix}$$

- Step Response ( $v_a = u(t)$ )
- Bode Plot of  $S(s)$




DC Gain = 0.


Transient:  $v_a \neq 0$

- "Virtual Short" approximation is acceptable when we can ignore this transient.
- For example, when the time constant of the external system is much large.
- Bandwidth
  - i) The frequency upto which a closed-loop system can track reference signals.
  - ii) The frequency upto which a closed-loop system can reject disturbance signals.

②  $A(s)$  in general

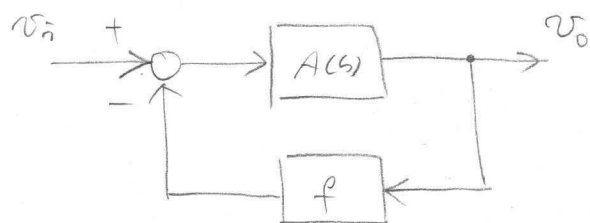

"Unity-feedback Factorization"

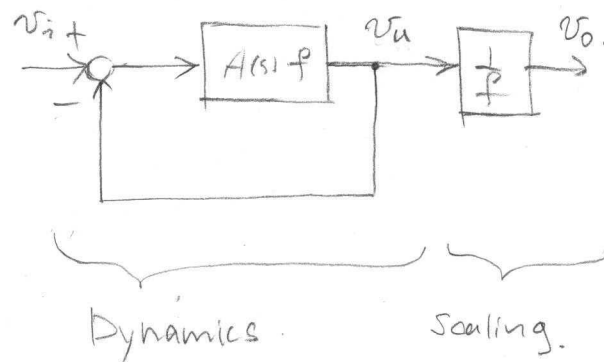


$$L(s) = A(s)f$$

"Loop"

$$T(s) = \frac{V_u}{V_i} = \frac{L}{1+L}$$

"Tracking"

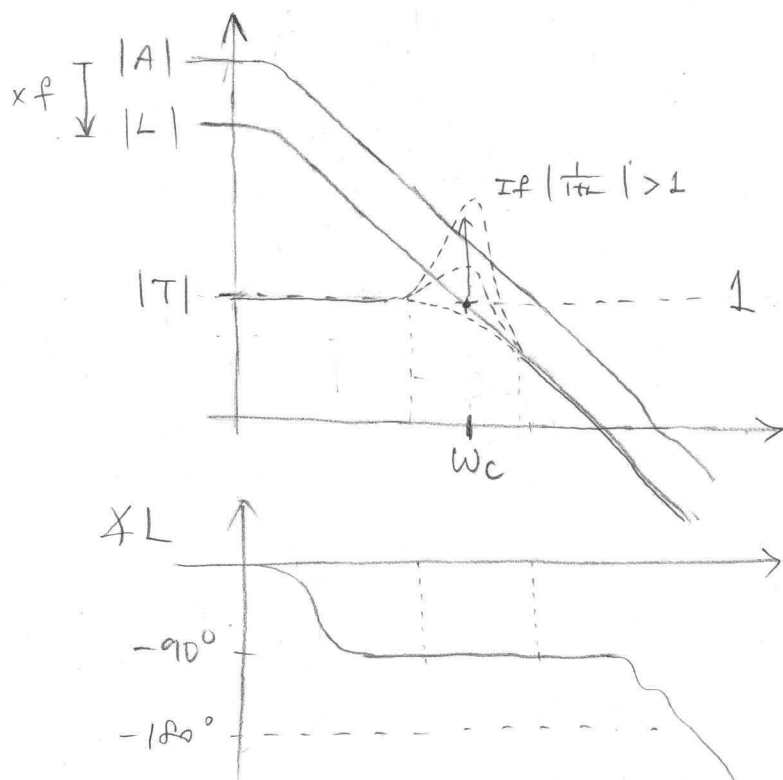

• When  $|L| \gg 1$

$$T \approx 1$$

• When  $|L| \ll 1$

$$T \approx L$$

•  $w_c$ : (Gain) cross-over frequency  $|L(jw)|_{w=w_c} = 1$

- Approximately equal to 3dB-bandwidth  $w_h$ : ( $w_c \approx w_h$ )
- Some people even define  $w_c$  as the bandwidth.
- It allows us to "estimate" the rise time (10% - 90%)


$$t_r \approx \frac{2.2}{w_h} \approx \frac{2.2}{w_c} \left( \frac{0.35}{f_c} \right) \quad \begin{matrix} w_c [\text{rad/s}] \\ f_c [\text{Hz}] \end{matrix}$$

- When  $|L| = 1$ .

$$|T| = \underbrace{|L|}_1 \cdot \underbrace{\left| \frac{1}{1+L} \right|}_s$$

The magnitude of  $T$  at  $\omega = \omega_c$  is determined by the phase of  $L$  at  $\omega = \omega_c$ .

- Vector Diagram for  $1 + L(j\omega_c)$

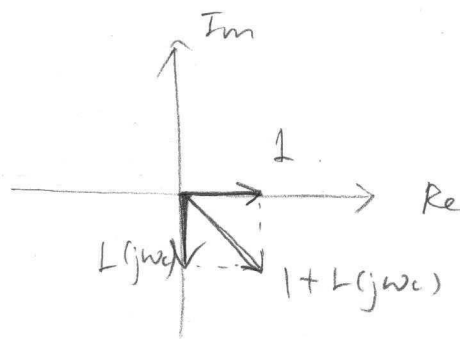


$$\text{if } \angle L(j\omega_c) = -90^\circ$$

$$|1 + L(j\omega_c)| = \sqrt{2}$$

$$\therefore |T| = \frac{1}{\sqrt{2}} \approx 0.707 \quad (-3\text{dB})$$

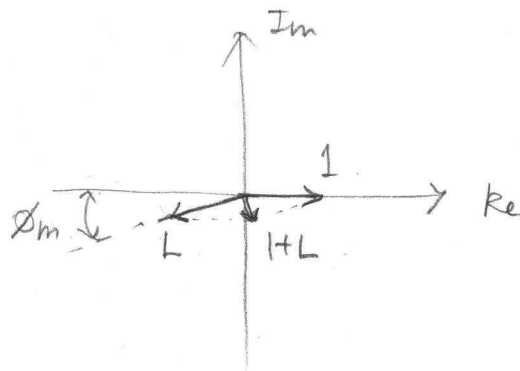Q. What if  $\angle L(j\omega_c)$  approaches  $-180^\circ$ ?



$$|1+L| \approx \phi_m$$

$$\therefore |T| \approx \frac{1}{\phi_m} \approx Q = \frac{1}{2\zeta}$$

From 2nd order syst.

•  $\phi_m$ : phase margin  $\angle L(j\omega) \big|_{\omega=\omega_c} - (-180^\circ)$

- It allows us to "estimate" the damping ratio  $\zeta$

$$\begin{aligned} \zeta &\approx \frac{\phi_m [\text{rad}]}{2} = \frac{\phi_m [\text{deg}] \left( \frac{\pi}{180} \right)}{2} = \frac{\phi_m [\text{deg}]}{114.6} \\ &\approx \frac{\phi_m [\text{deg}]}{100} \end{aligned}$$