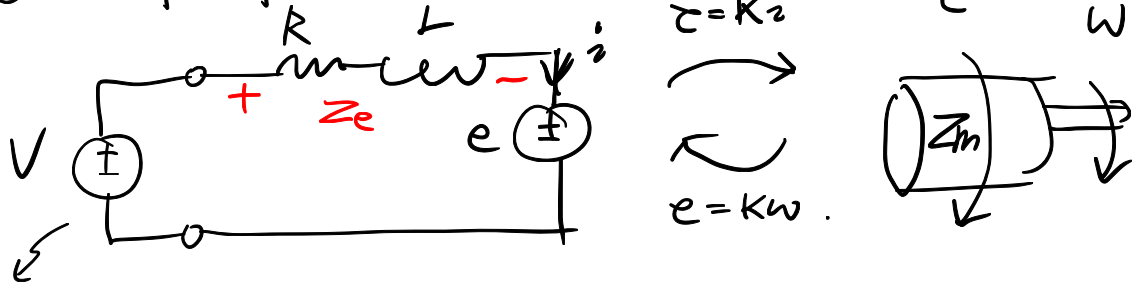


L8 – Voltage-controlled DC Motor


Modeling

① Lumped-parameter Model



Voltage drive



② Block diagram

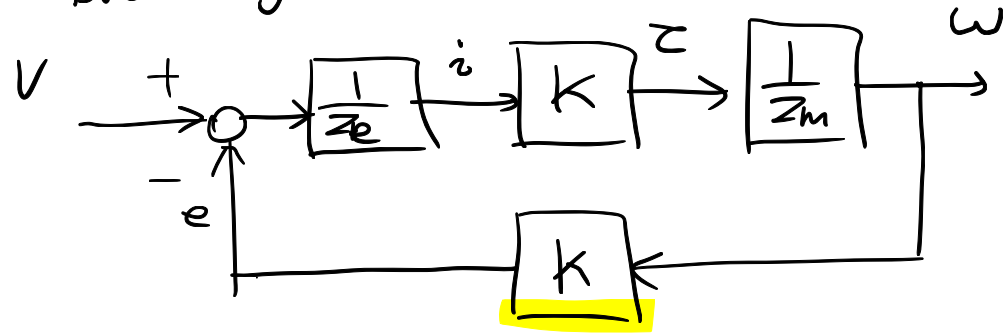

$$L(s) = \frac{K^2}{Z_e \cdot Z_m}$$

"Feed back Loop"

③ Equivalent Mech Model

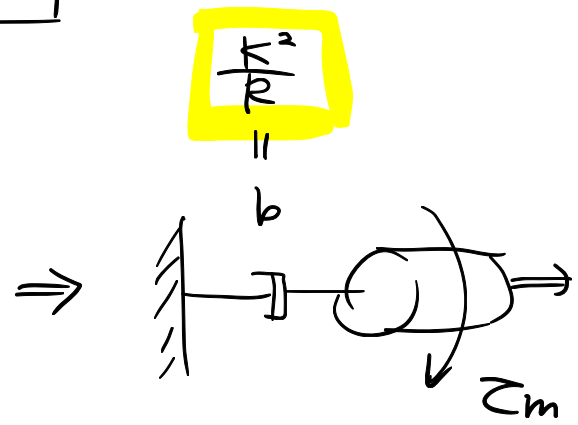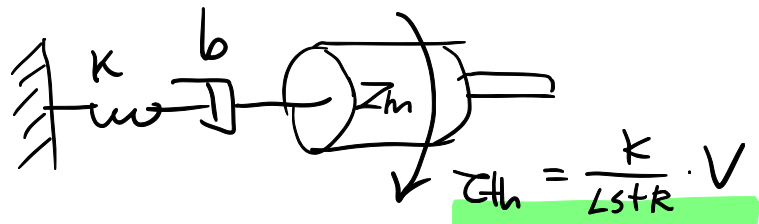


|        | Through   | Across      |
|--------|-----------|-------------|
| Flow   | $\dot{z}$ | $v, \omega$ |
| Effort | $f, \tau$ | $V$         |

↑

Maxwell  
Variable

Generator

flow → effort  
effort ← flow

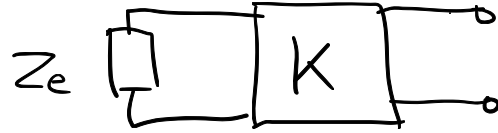

$$Z_m \doteq \frac{K^2}{Z_e}$$




$$Z_e' = T^2 \cdot Z_e$$

366


< Voltage-controlled de motor >

$$G_w \doteq \frac{\omega}{V} = \frac{\frac{K}{Z_e Z_m}}{1 + L}$$
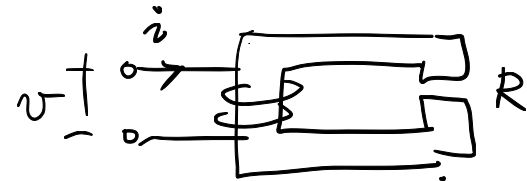
$$G_\tau \doteq \frac{\tau}{V} = \frac{\frac{K}{Z_e}}{1 + L}$$



$$V = N \dot{\phi}$$

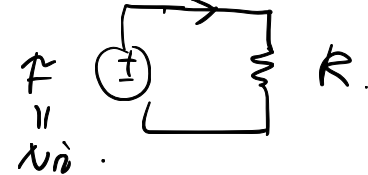



$$\textcircled{1} \text{ Speed Resp : } G_w = \frac{\frac{K}{(Ls+R)Z_m}}{1 + \frac{K^2}{(Ls+R)Z_m}} = \frac{K}{Z_m (Ls+R) + K^2}$$

$$Z_e = Ls + R$$

When  $Z_m = J_s$ . (free Inertia)

$$G_w = \frac{K}{J_s (Ls + R) + K^2} = \frac{K}{JLs^2 + JRs + K^2}$$
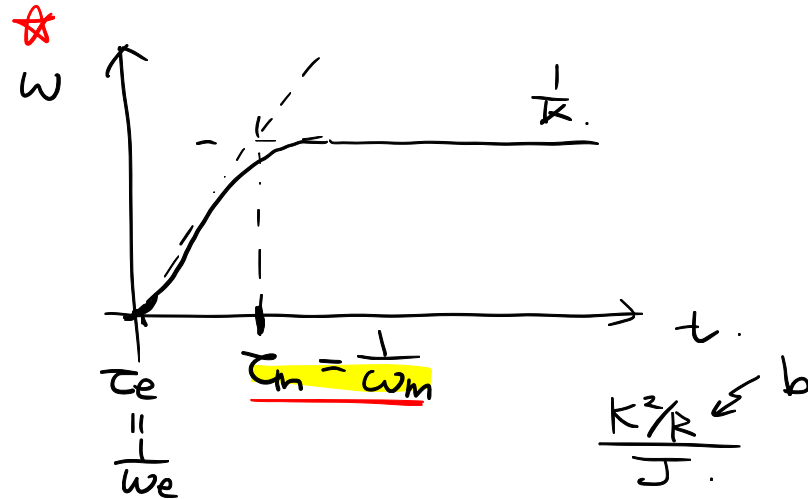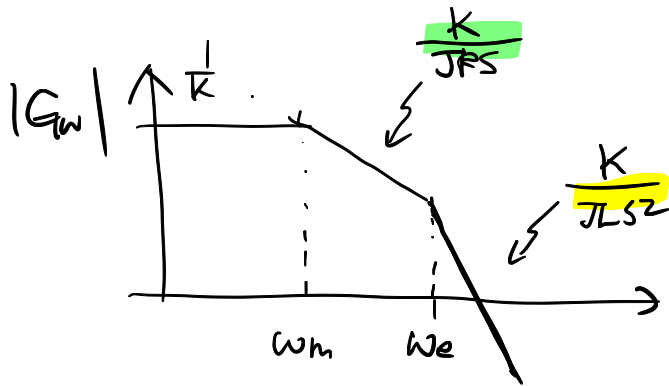
$$\omega_e = \frac{R}{L} \quad \omega_m = \frac{K^2}{JR} \quad , \quad (\omega_m \ll \omega_e)$$



Example parameters.


$$L = 1 \text{ mH} \quad R = 6 \Omega \quad K = 200 \text{ mNm/A} \quad J = 2 \times 10^{-9} \text{ cm}^2$$

$$\begin{cases} \omega_e = 1 \text{ kHz} \\ \omega_m = 6 \text{ Hz} \end{cases}$$

$$\tau_e = 1 \text{ ms}$$

$$\tau_m = 200 \text{ ms}$$

- Mech Model

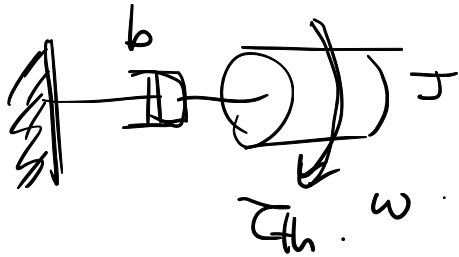

$$\frac{k}{JLs^2 + JRs + k^2}$$

$$\omega = \frac{1}{Js + b} \tau_{th} = \left( \frac{1}{Js + \frac{k^2}{R}} \right) \left( \frac{k}{Ls + R} V \right)$$


$$= \frac{k}{JLs^2 + (JR + \frac{k^2}{R}L)s + k^2} V$$

$$\frac{k^2}{R}L \ll JR \Leftrightarrow \omega_m \ll \omega_e$$

- Steady-state speed:  $\omega = \underline{\text{terminal velocity}}$



- From Q.

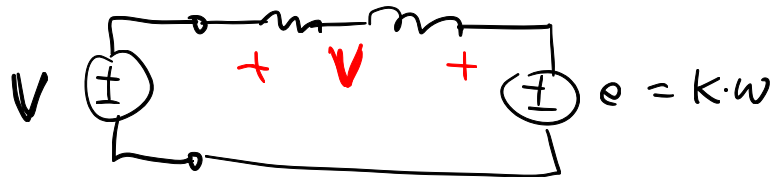


At the ss.

$$\omega = \text{const} \rightarrow \tau = 0 \rightarrow i = 0$$

$$\rightarrow \text{Voltage across } Z_e = 0$$
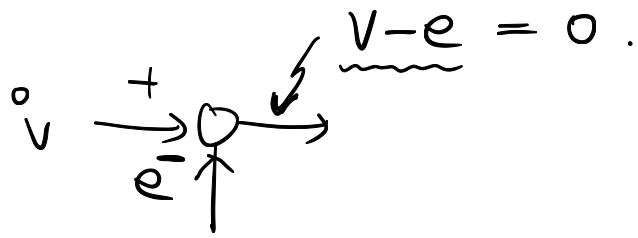
$$\rightarrow \underline{V = e = k\omega} \Rightarrow \underline{\omega = \frac{V}{k}}$$




- ① Open-loop Speed control with "Voltage drive" (source) is common for simple tasks. (e.g. cooling fans).

< Torque Response >.

- Torque = driving variable.
- High torque control, important for vehicles.

Very light loads.

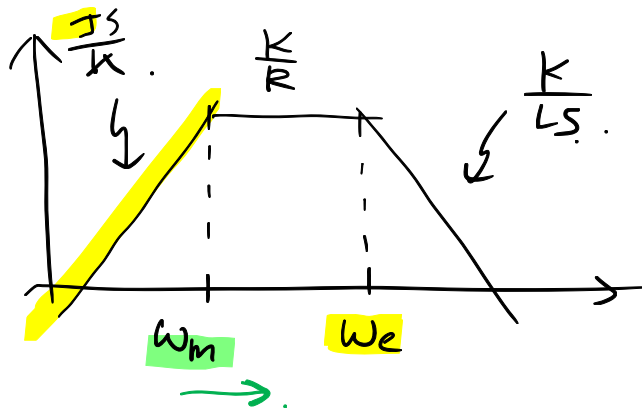
$$G_c = \frac{\tau}{V} = \frac{\frac{K}{Ls+R}}{1 + \frac{K^2}{(Ls+R)Js}} = \frac{K}{Ls+R + \frac{K^2}{Js}}$$




$$\omega_m = \frac{K^2/R}{J} \quad \text{as } J \downarrow \quad \omega_m \uparrow$$

① Back-emf effect :  $\downarrow$  low freq torques.

Mech : "apparent damping" 

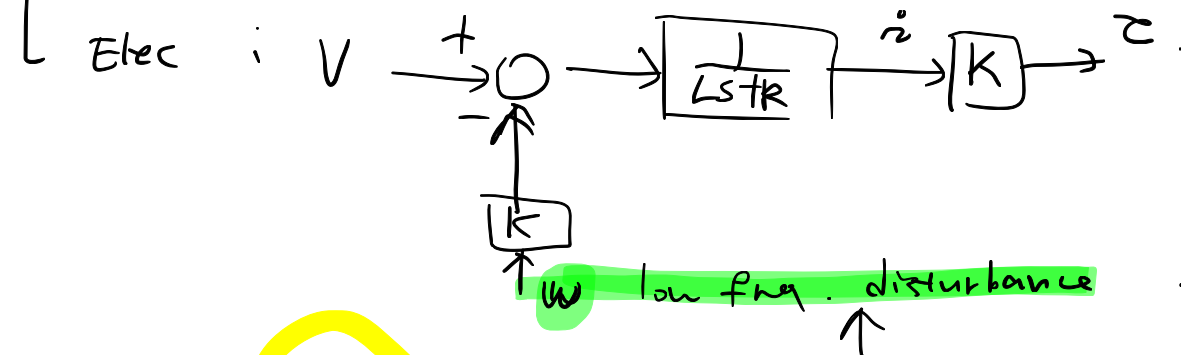


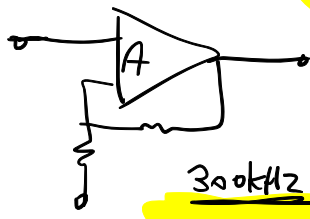②  $\omega_e \approx \underline{11 \text{ kHz}}$



⇒ Voltage-controlled dc motor, not good for torque resp.

⇒ Current-controlled dc motor ⇒

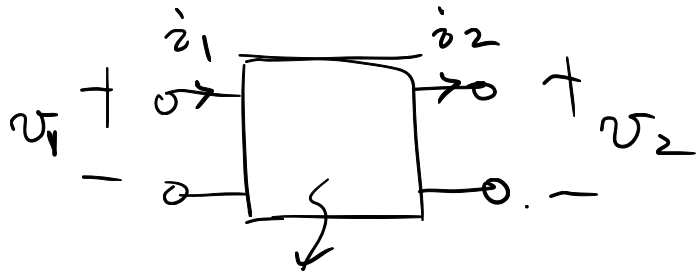

$$\underline{P_{in} = P_{out}}$$

Lossless converter . { ① Thavis  
② Gyari;

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} \begin{bmatrix} N & \\ & Y \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}$$

$$\begin{bmatrix} 0 & K \\ \frac{1}{K} & 0 \end{bmatrix}$$

