
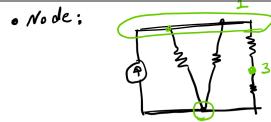


- Node Method
- Superposition
- Thevenin

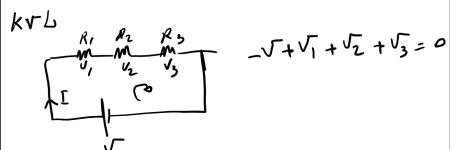


KCL

$$i_1 + i_4 = i_2 + i_3$$



Series:

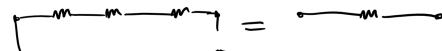

$$R_{eq} = \sum_{k=1}^n R_k$$

$$\frac{1}{R_{eq}} = \sum_{k=1}^n \frac{1}{R_k} \rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$




Node Method

- Identify all the nodes.
- Pick one of the nodes as the reference node.
- Assign a voltage to each node except the reference node.
- Write the KCL equation for all nodes except the reference node.

NOTES:

- Each node's voltage is measured w.r.t the reference node.
- Usually the node with the highest number of branches is picked as the reference node.
- If voltage sources are present in the circuit, and if they are not connected to the reference node (ground) on either side, consider the voltage source and the two nodes around it as a supernode and write KCL equation for the whole supernode.
- As a convention, when writing KCL for a node, we assume all the currents are outgoing except the ones determined by current sources.

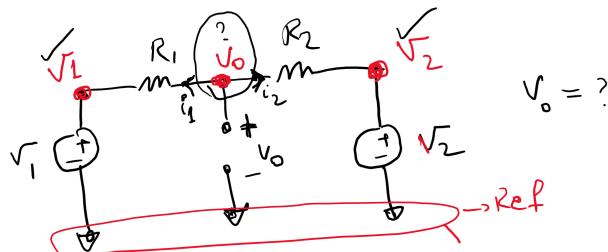


$$V_o : \underbrace{\frac{V_o - V_1}{R_1} + \frac{V_o - V_2}{R_2}}_{\text{outgoing}} = 0 \quad \text{incoming}$$

$$\cancel{\times R_2} R_2 (V_o - V_1) + R_1 (V_o - V_2) = 0$$

$$(R_2 + R_1) V_o - R_2 V_1 - R_1 V_2 = 0$$

$$V_o = \frac{R_1 V_2 + R_2 V_1}{R_1 + R_2}$$
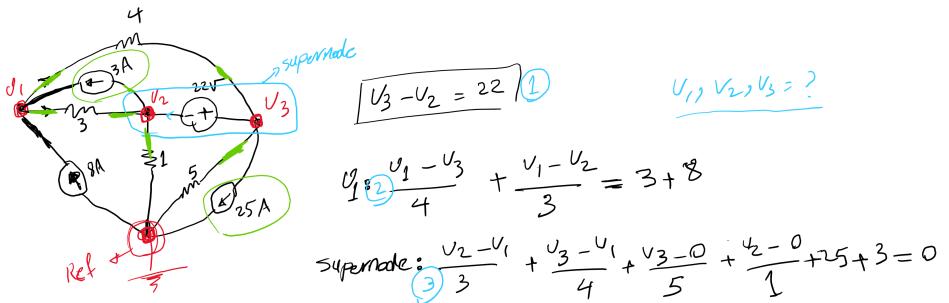
$$= \frac{R_1}{R_1 + R_2} V_2 + \frac{R_2}{R_1 + R_2} V_1$$



<superposition>

- Linear system:


$$\begin{matrix} x_1 \\ x_2 \end{matrix} \xrightarrow{H} \begin{matrix} y_1 \\ y_2 \end{matrix} \quad ax_1 + bx_2 \xrightarrow{H} ay_1 + by_2$$

$$\begin{matrix} 1 & 2 & 3 & 4 \end{matrix} \xrightarrow{\quad} y_1$$

$$\begin{matrix} 1 & 2 & 3 & 4 \end{matrix} \xrightarrow{\quad} y_2 \quad y = y_1 + y_2 + y_3 + y_4$$


$$\begin{matrix} 1 & 2 & 3 & 4 \end{matrix} \xrightarrow{\quad} y_3$$
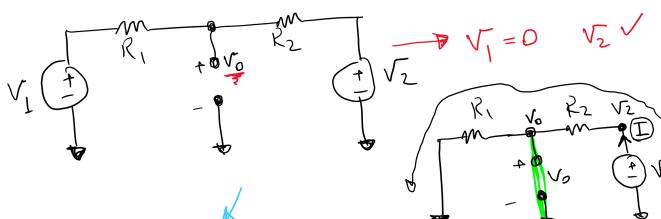
$$\begin{matrix} 1 & 2 & 3 & 4 \end{matrix} \xrightarrow{\quad} y_4$$



Turn off voltage source
short circuit

Turn off a current source:
open circuit

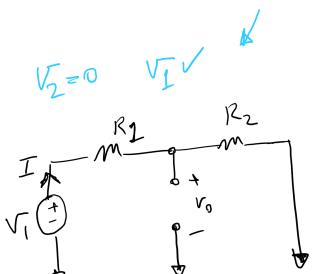

$$V_2 = (R_1 + R_2) I$$

$$I = \frac{V_2}{R_1 + R_2}$$

Ohm's Law $R_2: V_2 - U_0 = R_2 I$

$$U_0 = U_2 - R_2 I$$


$$U_0 = U_2 - R_2 \left(\frac{U_2}{R_1 + R_2} \right)$$

$$U_{02} = \frac{R_1}{R_1 + R_2} U_2$$

$$U_{02} = \frac{R_2}{R_1 + R_2} U_1$$



Superposition: $U_0 = U_{01} + U_{02} = \frac{R_1}{R_1 + R_2} U_2 + \frac{R_2}{R_1 + R_2} U_1$

< Thevenin Method >

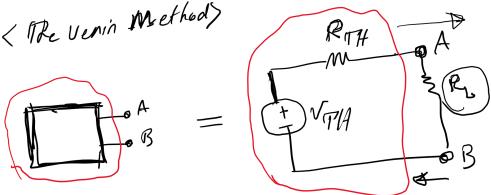


- Thevenin voltage: The voltage between A and B, when no load is connected to A and B (V_{OC}) (open circuit voltage)

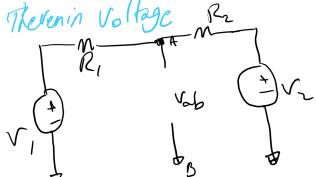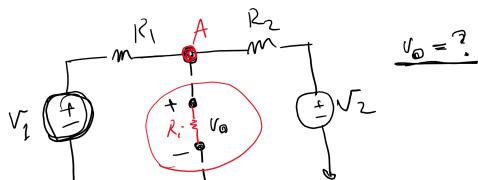- Thevenin Resistor: The equivalent resistor between A and B when all sources are turned off (killed).



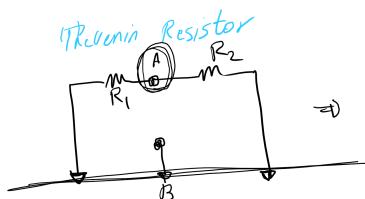
$$V_{ab} = V_{OC} = \frac{V}{R_{TH}} = \frac{R_1}{R_1 + R_2} V_2 + \frac{R_2}{R_1 + R_2} V_1$$



$$R_{TH} = R_1 // R_2 \Rightarrow R_{TH} = \frac{R_1 R_2}{R_1 + R_2}$$



Equivalent circuit

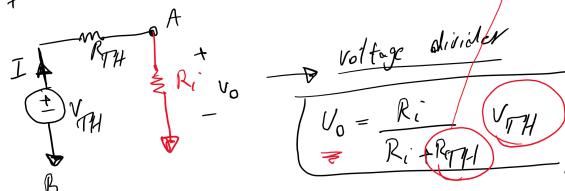

$$I = \frac{V_{TH}}{R_i + R_{TH}}$$

$$V_0 = R_i \times I = \frac{R_i}{R_i + R_{TH}} V_{TH}$$

Non-inverting Op-Amp with Z_i

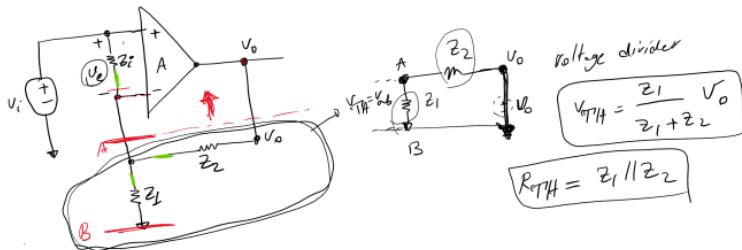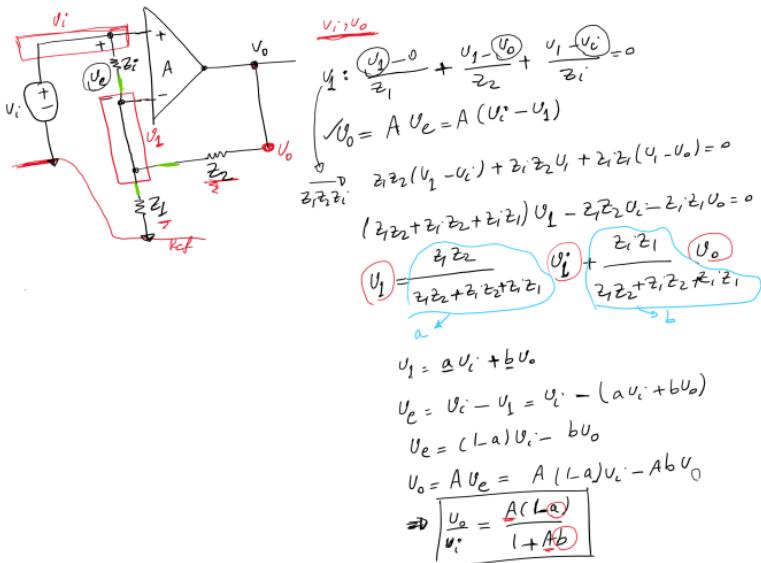

KVL:



$$-V_i + Z_1 I + \frac{V_{TH}}{Z_1} I + V_{TH} = 0$$

$$I = \frac{V_i - V_{TH}}{Z_1 + Z_2}$$


$$U_e = Z_1 I = \frac{Z_1}{Z_1 + Z_2} (V_i - V_{TH})$$

$$U_e = \frac{Z_1}{Z_1 + Z_2} \left(V_i - \frac{Z_1}{Z_1 + Z_2} V_o \right)$$

$$U_o = A U_e$$

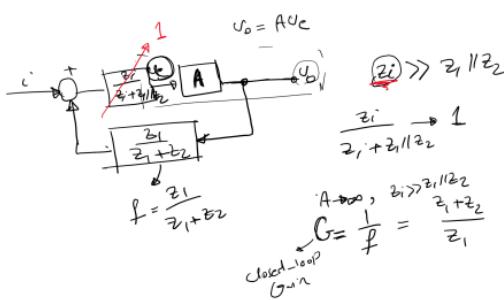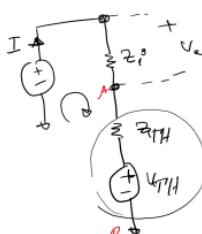

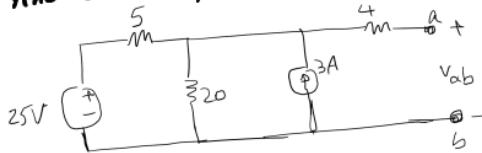Another example for Thevenin Method (Not solved in class)





< Thevenin Voltage >

$$V_{OC} = V_{ab} = ?$$


Let's use superposition for finding V_{ab}

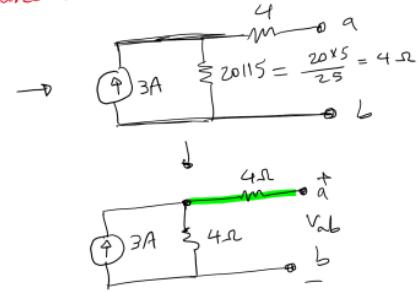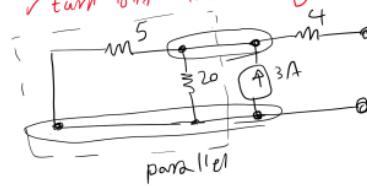✓ turn off the voltage source and find V_{ab}



$$V_{ab1} = 3 \times 4 = 12 \text{ V}$$

✓ turn off the current source


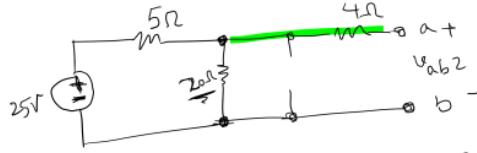


$$\text{Voltage divider} \rightarrow V_{ab2} = \frac{20}{20+5} \times 25 = \frac{20}{25} \times 25 = 20 \text{ V}$$

$$\Rightarrow \text{superposition: } V_{ab} = V_{ab1} + V_{ab2} = 20 \text{ V} + 12 \text{ V} = 32 \text{ V}$$

$$\Rightarrow V_{OC} = V_{TH} = 32 \text{ V}$$

< Thevenin Resistor >

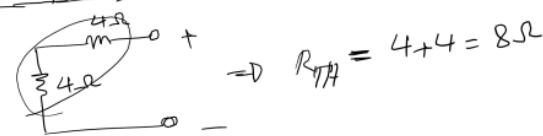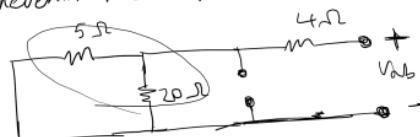

$$\Rightarrow R_{TH} = 4 + 4 = 8 \Omega$$

