

Homework 4

Assigned: Mar 2, 2021

Due: Mar 9, 2021

Problem 1

Figure 1 shows a transconductance amplifier driving a brushed dc motor. Here, $A_p(s)$ is the open-loop gain of a power op-amp, $A_s(s)$ is the open-loop gain of a signal op-amp, and Z_3 , Z_4 , and Z_5 are impedances to be designed. We assume infinite input impedance and zero output impedance for the op-amps.

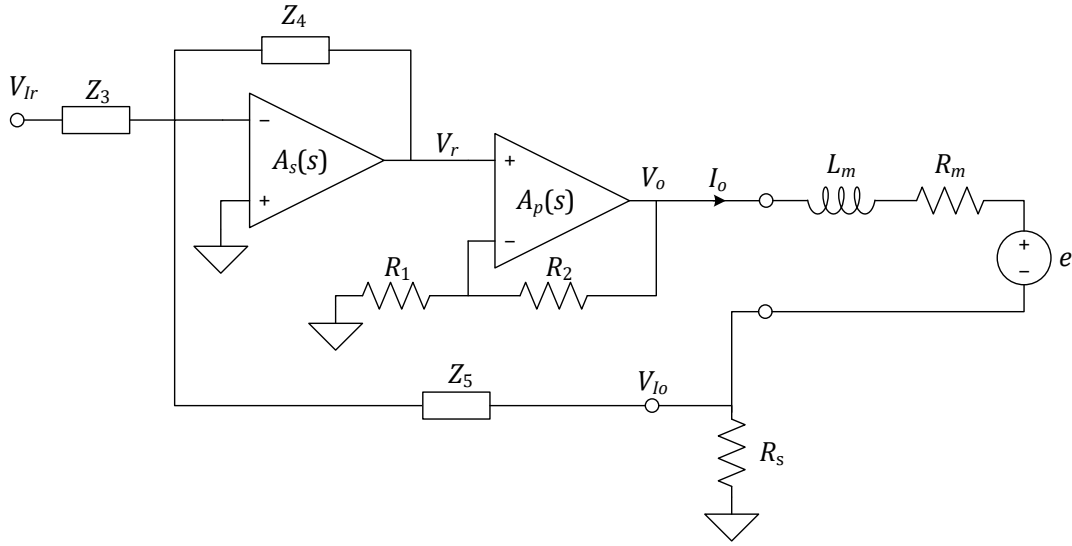


Figure 1: Schematic of a transconductance amplifier.

- For the signal op-amp stage, draw a block diagram that shows the relation between the V_{Ir} , V_{Io} , and V_r . The block diagram should show a feedback loop around $A_s(s)$ (Tip: do not use the virtual short approximation for V_- . Instead, use the superposition method to find the inverting terminal voltage V_-).
- Find the expression for the loop transfer function $L_s(s)$ of the signal op-amp stage in terms of Z_3 , Z_4 , Z_5 , and $A_s(s)$.
- Carry out block diagram algebra on the result of part (a) to complete the equivalent block diagrams in Figure 2.

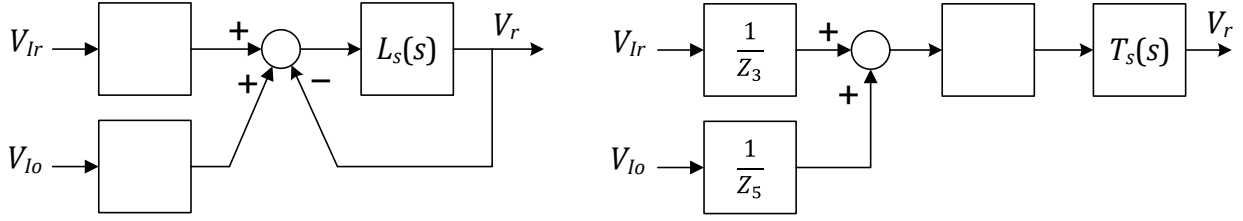


Figure 2: Equivalent block diagram, where $T_s(s) = \frac{L_s(s)}{1+L_s(s)}$

Problem 2

Figure 3 shows the full block diagram of the transconductance amplifier. Here, the motor back EMF e is modeled as a disturbance signal, and the load impedance and feedback gain are approximated for $R_s \ll R_5$. The op-amp open-loop transfer functions and circuit parameters are given as follows

$$\begin{aligned} A_s(s) &= \frac{5 \times 10^7}{s} & A_p(s) &= \frac{10^7}{s} & R_1 &= 1 \text{ k}\Omega & R_2 &= 9 \text{ k}\Omega \\ L_m &= 1 \text{ mH} & R_m &= 5.8 \Omega & R_s &= 0.2 \Omega & R_5 &= 1 \text{ k}\Omega. \end{aligned}$$

We will select values for R_3 , R_4 , and C_4 to complete the amplifier design. Use MATLAB for the design process.

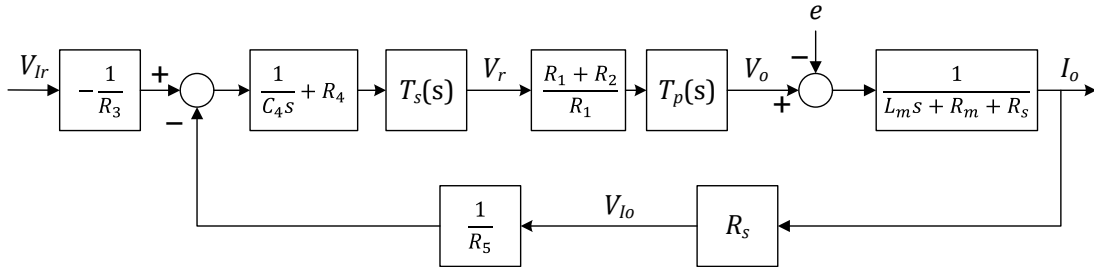


Figure 3: Transconductance amplifier block diagram.

- Selecting R_3 : Suppose we use a digital-to-analog converter (DAC) whose output range is $\pm 10 \text{ V}$ to drive V_{Ir} . Also, suppose the motor is designed for dc current range of $\pm 2 \text{ A}$. Find the value R_3 that allows maximum utilization of the DAC dynamic range. Assume that the loop transfer function has infinite dc gain.
- Selecting R_4 : This step corresponds to the design of proportional control. For now, let us assume that the bandwidth of $T_s(s)$ is infinitely high (i.e., $T_s = 1$) and capacitance C_4 is infinitely large. Find the value R_4 rounded to the nearest $\text{k}\Omega$ that makes the loop transfer function achieve the highest crossover frequency ω_c while guaranteeing phase margin $\phi_m \geq 90^\circ$. Note that this step should account for the finite bandwidth of $T_p(s)$. Draw the Bode plot of the loop transfer function and find ω_c and ϕ_m .

- (c) Selecting C_4 : This step corresponds to the design of integral control. A capacitor C_4 in series with R_4 makes the loop transfer function achieve higher dc gain, thereby improving the closed-loop tracking and disturbance rejection performance. However, C_4 can decrease the phase margin. Find the value C_4 rounded to the nearest nF that achieves the highest loop gain while guaranteeing phase margin $\phi_m \geq 85^\circ$. Draw the Bode plot of the loop transfer function and find ω_c and ϕ_m .
- (d) Including $T_s(s)$: Using the R_3 , R_4 , and C_4 values obtained above, draw the Bode plot of the final loop transfer function including $T_s(s)$ and find ω_c and ϕ_m .