
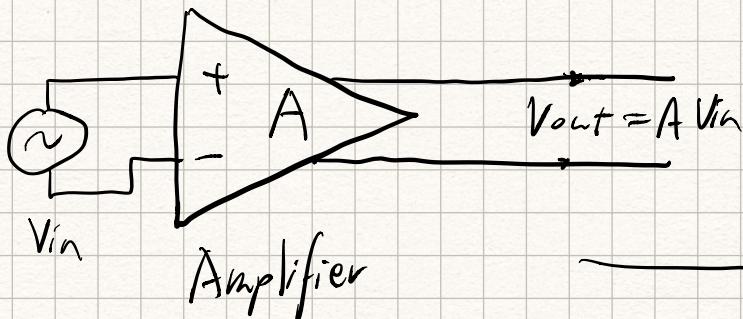


Origins of negative feedback control.

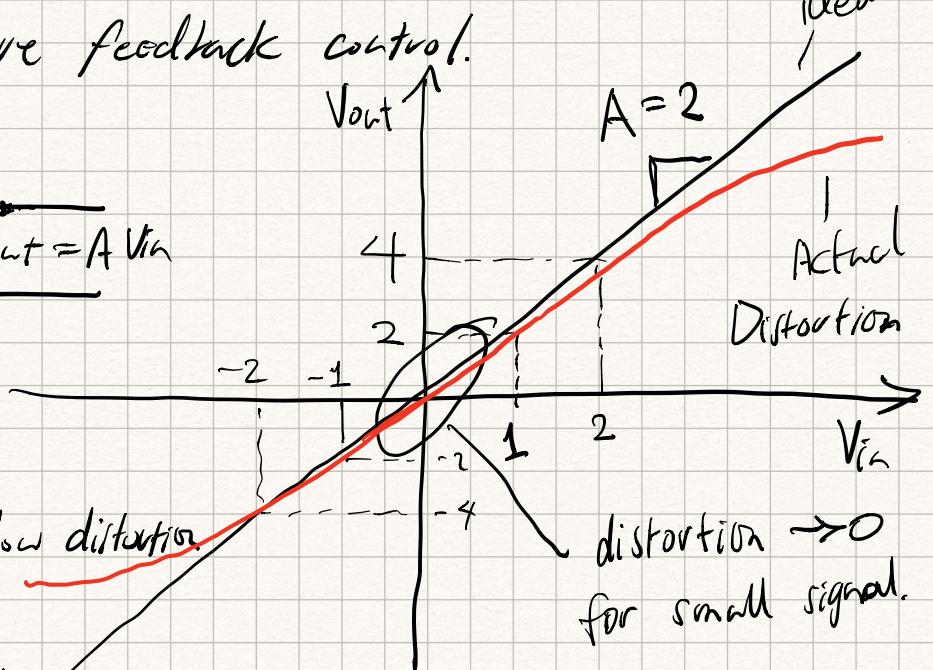


Easy: Gain

Hard: linear gain - low distortion
stable gain




1927 Harold Black

- AT&T Bell Labs

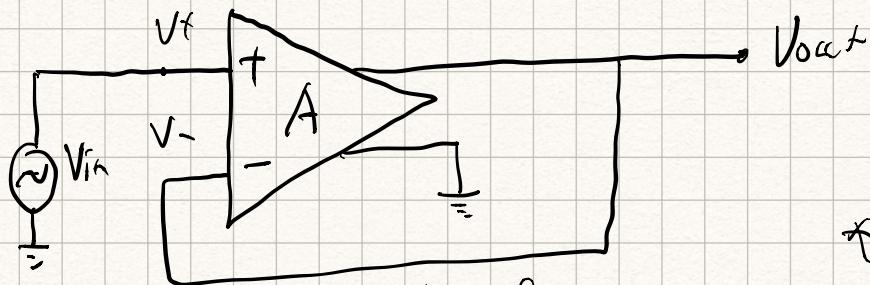

Negative feedback forces
 $V_- \rightarrow V_+$

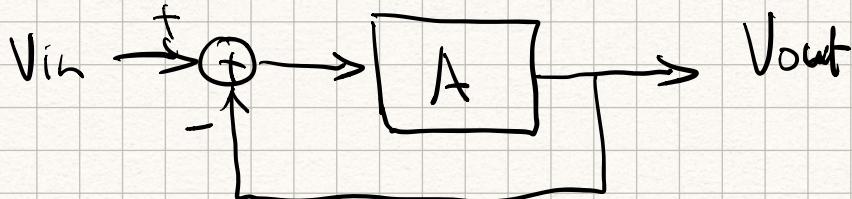Input $\rightarrow 0$ distortion $\rightarrow 0$.



$$V_{out} = A(V_{in} - V_{out})$$

$$V_{out} + AV_{out} = A V_{in}$$

$$\frac{V_{out}}{V_{in}} = \frac{A}{A+1}$$

* If $V_+ > V_-$

$$A(V_+ - V_-) > 0$$

$$V_{out} \uparrow V_- \uparrow V_- \rightarrow V_+$$

* If $V_+ < V_-$

$$A(V_+ - V_-) < 0$$

$$V_{out} \downarrow V_- \downarrow V_- \rightarrow V_+$$


for op Amps

$$A > 10^6$$

$$A \gg 1$$



$$V_{out} \approx V_{in}$$

How do we get gain?

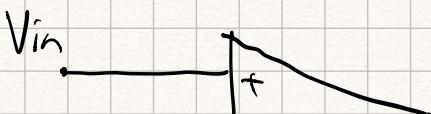

Vout



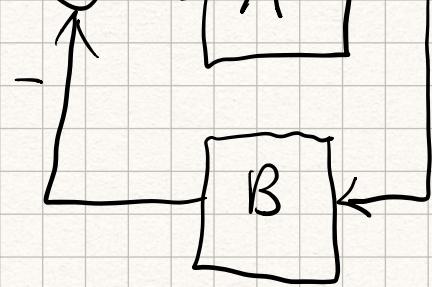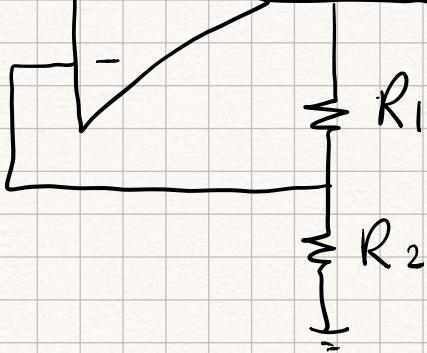


$$B = \frac{R_2}{R_1 + R_2}$$

$$V_{out} = A(V_{in} - BV_{out})$$

$$V_{out}(1+AB) = AV_{in}$$

$$\text{If } AB \gg 1 \text{ then } V_{out} \approx \frac{A}{AB} V_{in} = \frac{1}{B} V_{in}$$

Disturbance Rejection:

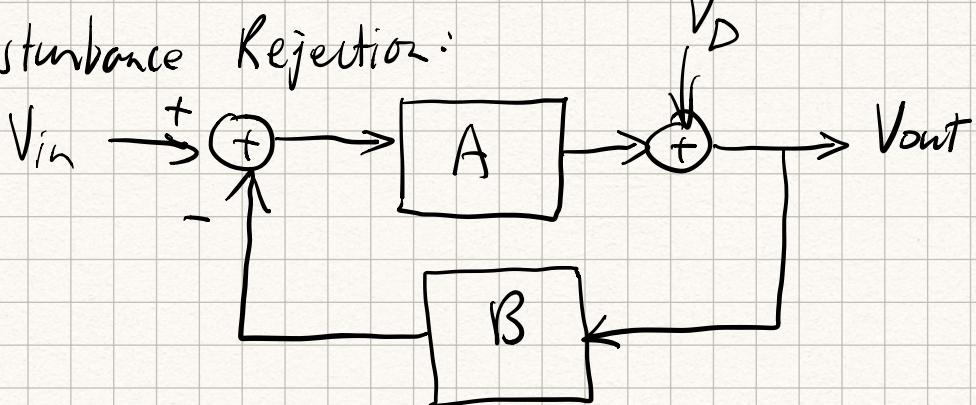

$$V_{out} = V_D + A(V_{in} - BV_{out})$$

$$V_{out}(1+AB) = V_D + AV_{in}$$


$$V_{out} = \left(\frac{A}{1+AB} \right) V_{in} + \left(\frac{V_D}{1+AB} \right)$$

V_D is reduced by a factor of $1+AB$

Negative Feedback: Use gain (AB) to improve system performance: - distortion
- error
- disturbance rejection

Notice: Our Analysis doesn't depend on units — use in elec, mech, chem, ... systems.



Systems with freq. response

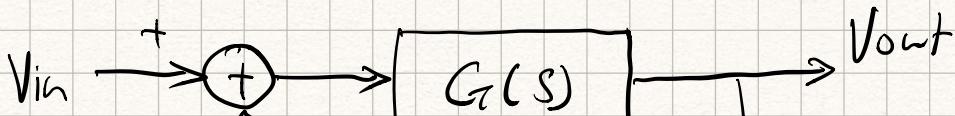

$$G(s) = \frac{A}{s^2 + \omega_n^2}$$



Bode Plot.

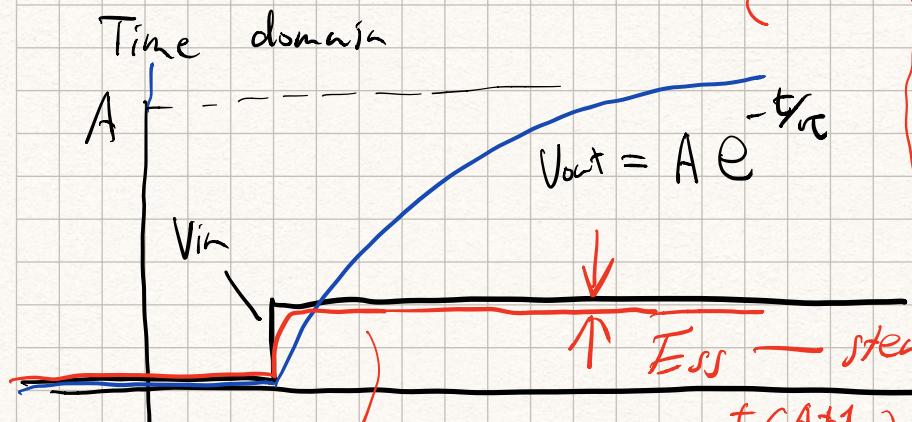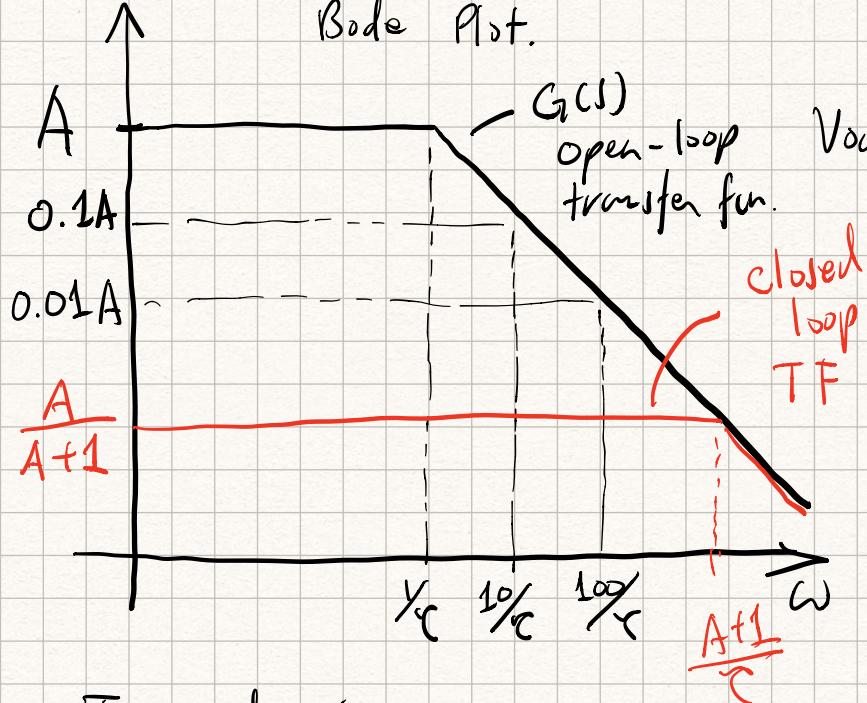

$$s = j\omega$$

$$V_{out} = G(s)(V_{in} - V_{out})$$

$$V_{out}(1 + G(s)) = V_{in}(G(s))$$


$$\frac{V_{out}}{V_{in}} = \frac{G(s)}{1 + G(s)}$$

$$\frac{V_{out}}{V_{in}} = \frac{\frac{A}{\tau s + 1}}{1 + \frac{A}{\tau s + 1}}$$

$$\frac{V_{out}}{V_{in}} = \frac{A}{\tau s + 1 + A}$$

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{A}{(A+1) + (\frac{\tau}{A+1})s}}$$

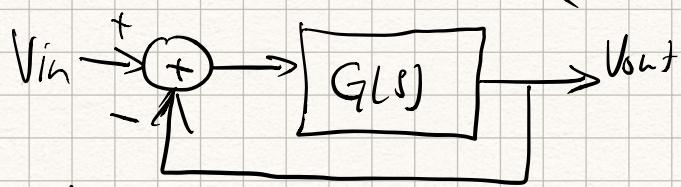What if $G(s) = \frac{A}{(\tau_1 s + 1)(\tau_2 s + 1)}$



① Phase margin $\approx 0^\circ$
- unstable system

② Phase margin $= 45^\circ$
- Typical minimum phase margin for a useful system



③ Phase margin > 60°
- stable enough

