

Problem 2 (35 points)

Let us consider an op-amp circuit in Figure 2. We assume that the op-amp has infinite input impedance, zero output impedance, and open-loop transfer function $A(s)$.

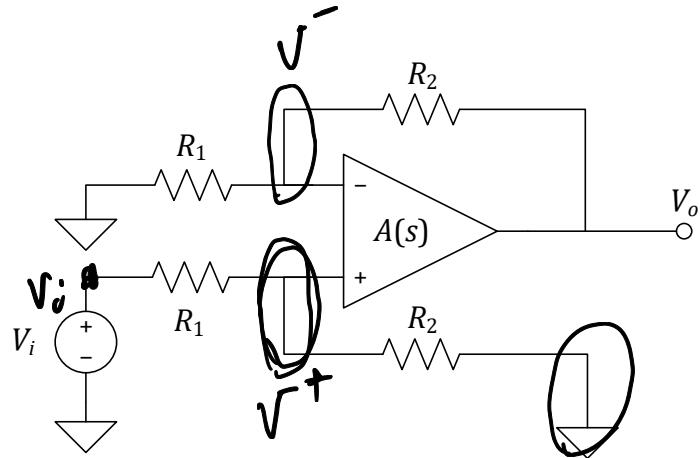


Figure 2: Op-amp circuit for the problem.

- (a) (5 pt.) Draw a block diagram that shows the relation between the input voltages V_i and the output voltage V_o . The block diagram should show a feedback loop around $A(s)$.

$$V^- : \frac{V^- - 0}{R_1} + \frac{V^- - V_o}{R_2} = 0$$

$$V^+ : \frac{V^+ - V_i}{R_1} + \frac{V^+ - 0}{R_2} = 0$$


$$\stackrel{x R_1 R_2}{=} R_2 V^- + R_1 (V^- - V_o) = 0$$

$$\Rightarrow R_2 (V^+ - V_i) + R_1 V^+ = 0$$

$$\stackrel{(R_2 + R_1)}{=} (R_2 + R_1) V^- = R_1 V_o \Rightarrow V^- = \frac{R_1}{R_2 + R_1} V_o \quad (1)$$


$$(R_2 + R_1) V^+ = R_2 V_i \Rightarrow V^+ = \frac{R_2}{R_1 + R_2} V_i \quad (2)$$

$$\rightarrow (V^+ - V^-) A(s) = V_o$$

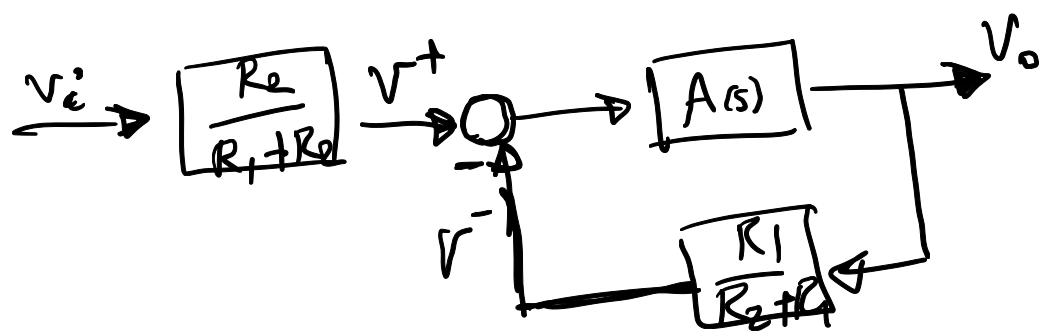

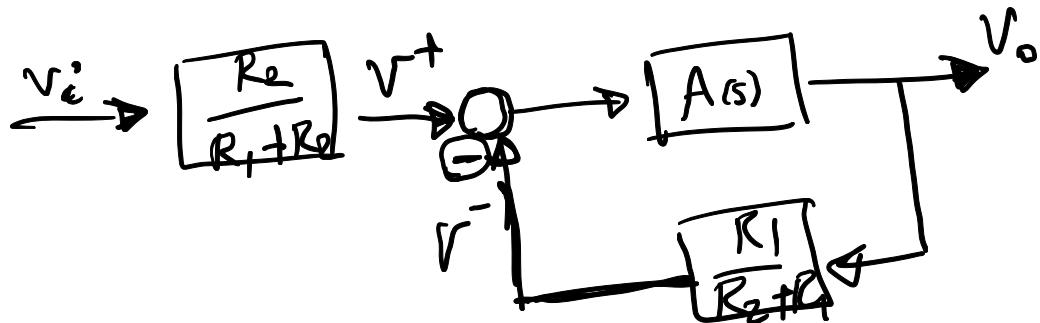(b) (5 pt.) Express the loop return ratio $L(s)$ in terms of R_1 , R_2 , and $A(s)$.

$$L(s) = -LT = -\left(-\frac{R_1}{R_1+R_2} A(s)\right) = \frac{R_1}{R_1+R_2} A(s)$$
$$= f A(s)$$



$$\boxed{L(s) = f A(s)}$$

(c) (5 pt.) For $R_1 = 1 \text{ k}\Omega$, $R_2 = 1 \text{ k}\Omega$, and $A(s)$ given in Figure 3, find the unity-gain crossover frequency ω_c and phase margin ϕ_m of $L(s)$.

$$|L(j\omega)|_{\omega=\omega_c} = 1 \quad f = \frac{R_1}{R_1 + R_2} = \frac{1}{2}$$

$$f |A(j\omega)|_{\omega=\omega_c} = 1$$

$$\Rightarrow \frac{1}{2} |A(j\omega)|_{\omega=\omega_c} = 1 \Rightarrow |A(j\omega)|_{\omega=\omega_c} = 2$$

$$f = 5 \text{ MHz}, \omega_c = 2\pi f_c = \pi \times 10^7 \text{ rad/s}$$

$$\phi_m = \angle L(j\omega)|_{\omega=\omega_c} - (-180) = \begin{aligned} & \angle A(j\omega)|_{\omega=5 \text{ MHz}} + 180 \\ & = -105 + 180 = 75^\circ \end{aligned}$$

$$L(s) = f A(s) \Rightarrow \angle L(j\omega) = \angle A(j\omega)$$

(d) (5 pt.) For $R_1 = 1 \text{ k}\Omega$ and $A(s)$ given in Figure 3, find the resistance value R_2 that makes the closed-loop transfer function $G(s) = V_o/V_i$ achieve a -3 dB bandwidth of 10 kHz .

at 10 kHz

$$\angle A(j\omega) = \angle L(j\omega) = -90^\circ \Rightarrow \phi_m = 90^\circ$$

-3 dB bandwidth = crossover frequency

$$|G(j\omega)|_{\omega=10\text{kHz}} = -3\text{dB} = \frac{1}{\sqrt{2}}$$

$$|L(j\omega)|_{\omega=10\text{kHz}} = 1$$

$$\text{# } |A(j\omega)|_{\omega=10\text{kHz}} = 1 \Rightarrow |A(j\omega)|_{\omega=10\text{Hz}} = \frac{1}{\sqrt{2}}$$

$$b_0^3 = \frac{R_1 + R_2}{R_1} = \frac{1 + R_2}{1}$$

$$R_2 = 10^3 - 1 = 999 \text{ k}\Omega$$

(e) (5 pt.) For the circuit designed in part (d), determine the dc gain of $G(s) = V_o/V_i$.


$$|G(j\omega)|_{\omega=0}$$

$$R_2 = 999 \text{ k}\Omega$$

$$R_1 = 1 \text{ k}\Omega$$

$$G(s) = \frac{R_2 A(s)}{R_1 + R_2 + R_1 A(s)} = \frac{999 A(s)}{1000 + A(s)}$$
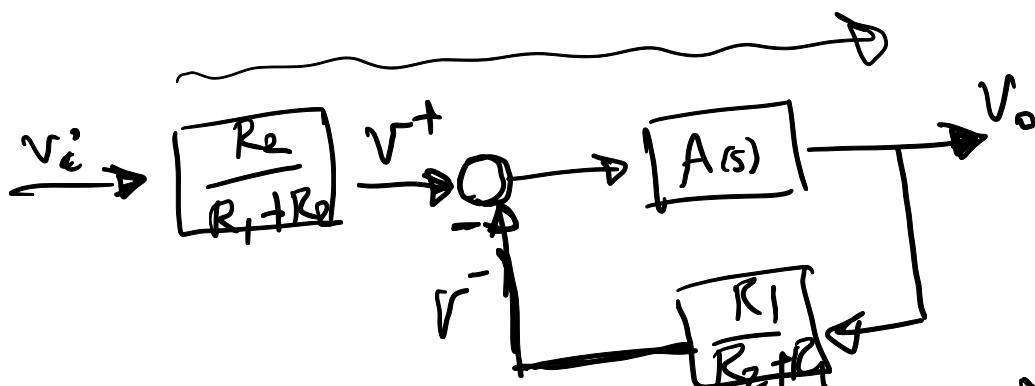
$$G(s) = \frac{V_o}{V_i} = \frac{\frac{R_2}{R_1 + R_2} A(s)}{1 + \frac{R_1}{R_1 + R_2} A(s)}$$



$$|G(j\omega)|_{\omega=0} = \frac{999 A(j\omega)|_{\omega=0}}{1000 + A(j\omega)|_{\omega=0}} = \frac{999 (10^6)}{1000 + 10^6}$$

$$\approx \frac{998}{s}$$

(f) (10 pt.) Suppose the circuit designed in part (d) is excited with an input voltage

$$\hookrightarrow V_i(t) = \cos(2\pi \times 10^7 t)$$

bandwidth loft 2

$$V_o(t) = M_o \cos(2\pi \times 10^7 t + \phi_o)$$

$$G(j\omega) = \frac{R_2}{R_1 + R_2} A(j\omega)$$

$$|G(j\omega)|_{\omega=10^7} = \frac{999}{1000} |A(j\omega)|_{\omega=10^7}$$

$$= 0.999 \times 1 = 0.999$$

$$\angle G(j\omega) = \angle A(j\omega) \Big|_{\omega=10^7} = -120^\circ$$

$$V_o(t) = 0.999 \cos(2\pi \times 10^7 t - 120^\circ)$$

$$G(s) = \frac{R_2 A(s)}{R_1 + R_2 + R_1 A(s)}$$

$$A(j\omega) \Big|_{\omega=10^7} = 1 \angle -120^\circ$$

$$= e^{-\frac{2\pi}{3}j}$$

$$= \cos(-\frac{2\pi}{3}) + j \sin(-\frac{2\pi}{3})$$

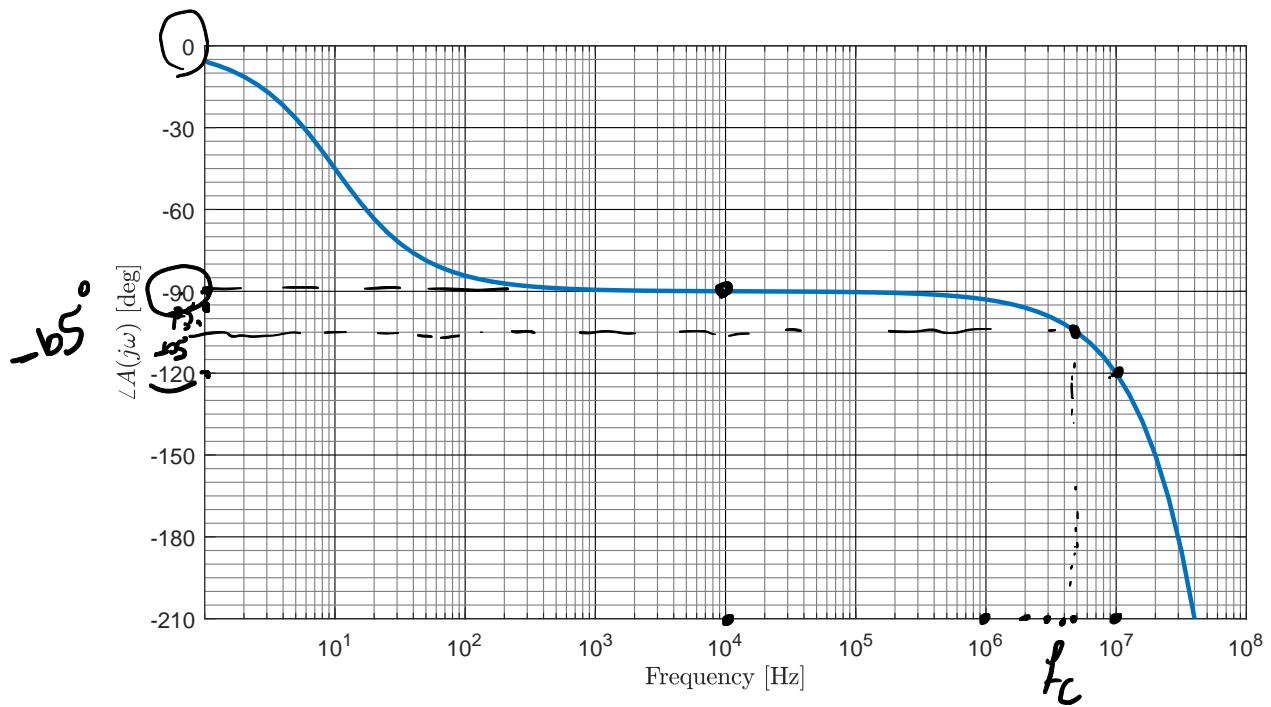
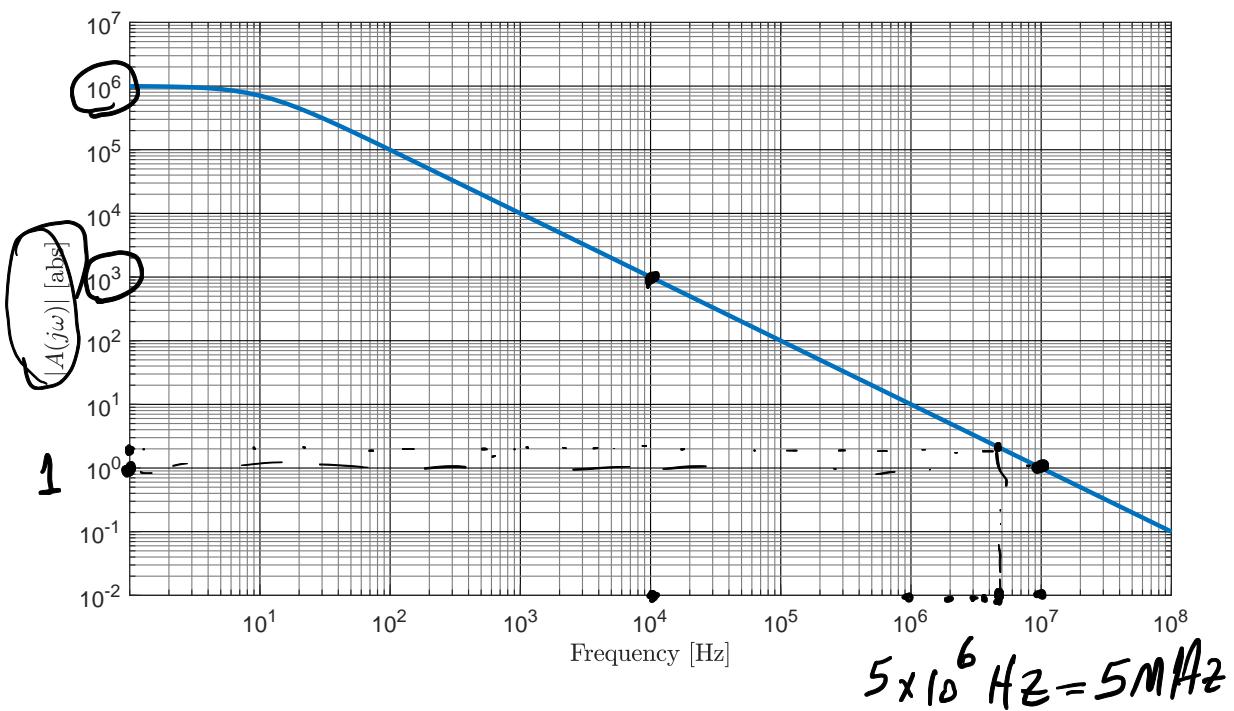


Figure 7: Bode plot of $A(s)$.