

## Lab 2 – Power Transconductance Amplifier

Pre-lab due: Feb 22, 2021  
Lab report due: Mar 12, 2021

### 1 Objectives

- Design a transconductance amplifier using a power operational amplifier.
- Measure the closed-loop step response.
- Measure the closed-loop frequency response.

### 2 Lab Description

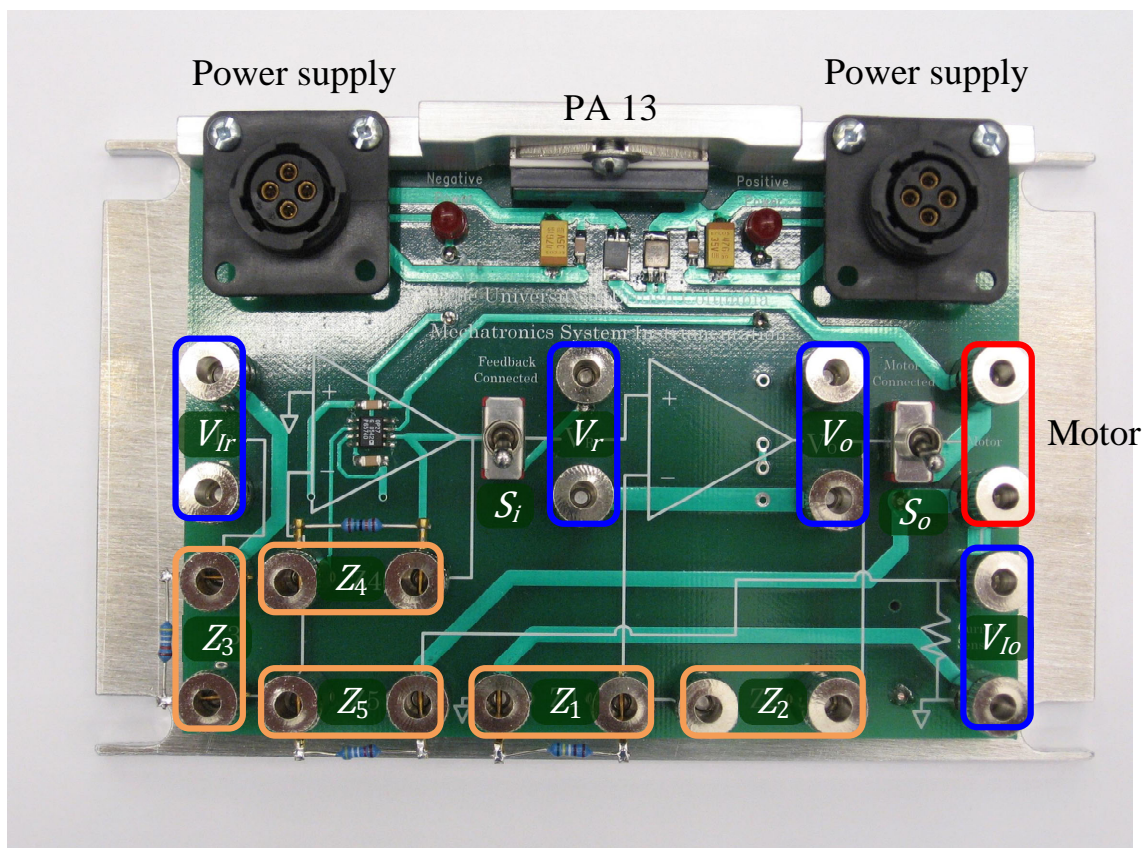


Figure 1: Picture of the power amplifier board.

Figure 1 shows a picture of the power amplifier board. Figure 2 shows a simplified circuit schematic. The board consists of two op-amp stages: a voltage stage based on a power op-amp (PA13 from Apex Microtechnology) and an analog current controller based on a precision op-amp

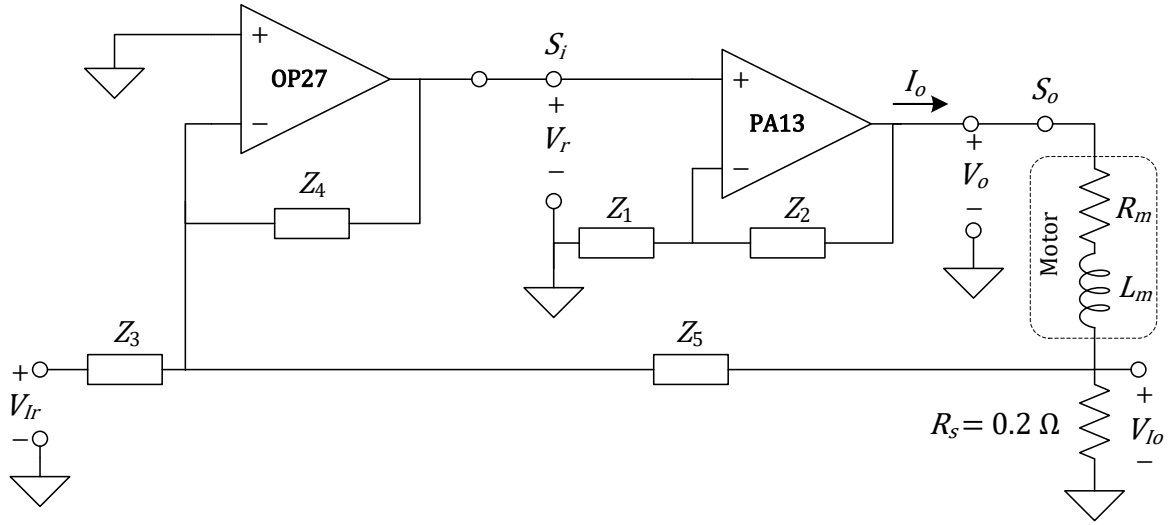


Figure 2: Power amplifier simplified schematic diagram.

(OP27 from Analog Devices). The power op-amp is attached to an aluminum heat sink and the precision op-amp is mounted on the printed circuit board. On the back side of the board, there is a shunt resistor  $R_s = 0.2\Omega$  to measure the current through the motor winding.

The sockets labeled as  $Z_1$ - $Z_5$  are to configure impedances that program the amplifier board. The sockets labeled as  $Z_1$  and  $Z_2$  are for two resistors that set the gain and bandwidth of the voltage stage. Select  $Z_1 = 2.2\text{ k}\Omega$  and  $Z_2 = 22\text{ k}\Omega$  so that the DC gain of the voltage stage becomes  $V_o/V_r = 11$ . The sockets labeled as  $Z_3$ ,  $Z_4$ , and  $Z_5$  are for impedances that implement feedback current control. In this lab, we will select appropriate impedances  $Z_3$ ,  $Z_4$ , and  $Z_5$  to implement analog current control based on the design specifications.

The sockets labeled as **Motor** are for the DC motor. Do not measure the voltage across these sockets with an oscilloscope, as neither of them are grounded. This may irreversibly damage the power amplifier board or the oscilloscope.

The board provides dedicated sockets for voltage measurements:  $V_{Ir}$ ,  $V_r$ ,  $V_o$ , and  $V_{Io}$ . Here,  $V_{Ir}$  is the current-reference voltage,  $V_r$  is the voltage stage input voltage,  $V_o$  is the voltage stage output voltage, and  $V_{Io}$  is the current-sensing voltage. Please do not use any other sockets for measurement. Also, make sure that the banana connector's ground terminal is oriented toward the bottom side of the board.

There are two switches  $S_i$  and  $S_o$  at the input and output of the power op-amp. The input switch  $S_i$  connects/disconnects the current controller. The output switch  $S_o$  connects/disconnects the DC motor load. In this lab, we will switch  $S_i$  to **Feedback Connected** side to connect the current controller and switch  $S_o$  to **Motor Connected** side to connect the motor.

### 3 Pre-lab Assignment

1. For  $Z_1 = 2.2\text{ k}\Omega$  and  $Z_2 = 22\text{ k}\Omega$ , draw a block diagram of the voltage stage that shows the relation between the input voltage  $V_r$  and output voltage  $V_o$ .
2. Draw a block diagram of the whole system that shows the relation between the current-reference voltage  $V_{Ir}$  and current-sensing voltage  $V_{Io}$ .
3. Current controller design: select appropriate values for  $Z_3$ ,  $Z_4$ , and  $Z_5$  to design a current controller that meets the following specifications.
  - $Z_3$ ,  $Z_4$ , and  $Z_5$  consist of resistors and/or capacitors. The resistors in stock are from  $10\text{ }\Omega$  to  $1\text{ M}\Omega$  in standard increments. The capacitors are from  $100\text{ pF}$  to  $4.7\text{ }\mu\text{F}$ .
  - The DC gain of  $V_{Io}/V_{Ir}$  is  $0.2\text{ V/V}$  (or, the DC transconductance of  $I_o/V_{Ir}$  is  $1\text{ A/V}$ ).
  - The closed-loop bandwidth of  $V_{Io}/V_{Ir}$  should be greater than  $5\text{ kHz}$ .
  - The step response of  $V_{Io}/V_{Ir}$  should have zero steady state error.
  - The loop should have a phase margin of at least  $60^\circ$ .
4. Based on your selected  $Z_3$ ,  $Z_4$ , and  $Z_5$ , draw the Bode plot and step response of  $V_{Io}/V_{Ir}$ .

**Note:** The Bode plots must be appropriately labeled with DC gain, relevant break frequencies, and slopes. The Bode plots must include the phase plot as well as magnitude. The step responses should have the correct initial slope (based on the system order), labeled time constant, 10%-90% rise time, steady-state value, and percentage overshoot (if any).

## 4 Lab Assignment

In this lab, we will connect the voltage stage to the current controller and motor by turning on the switches  $S_i$  and  $S_o$ . Make sure that  $S_i$  is toward the **Feedback Connected** and  $S_o$  is toward the **Motor Connected**.

### 4.1 Set the impedances $Z_1$ - $Z_5$

With the power supplies turned off, set  $Z_1 = 2.2\text{ k}\Omega$  and  $Z_2 = 22\text{ k}\Omega$ , and populate  $Z_3$ ,  $Z_4$ , and  $Z_5$  based on the pre-lab design.

### 4.2 Step responses

Apply a current-reference voltage  $V_{Ir}$  using a signal generator and measure the current-sensing voltage  $V_{Io}$  as well as  $V_{Ir}$  using an oscilloscope. Make sure that nothing is connected for  $V_r$ .

Set  $V_{Ir}$  to be a 10-Hz square wave with different amplitudes ( $0.1 V_{\text{pk-pk}}$ ,  $0.2 V_{\text{pk-pk}}$ ,  $0.5 V_{\text{pk-pk}}$ , and  $1.0 V_{\text{pk-pk}}$ ), and measure  $V_{Io}$  for each amplitude. Record the four step responses, and calculate the rise time (from 10% to 90%) and the percentage overshoot. Compare the results with the pre-lab predictions.

### 4.3 Frequency responses

Set  $V_{Ir}$  to be a sine wave with  $0.1 V_{\text{pk-pk}}$  amplitude. Measure the frequency response of  $V_{Io}/V_{Ir}$  at more than 20 frequency points from 50 Hz to  $5 \times \omega_h$ , where  $\omega_h$  is the designed closed-loop bandwidth. The frequency points should be nearly equally spaced in log scale. Take more data points around the break frequencies and interesting features. (Tip: initially sweep the frequencies quickly to identify the break frequencies and interesting features based on the phase difference between  $V_{Ir}$  and  $V_{Io}$ . Then, decide on the appropriate frequency points and proceed with the actual measurements.)

Record the amplitudes of  $V_{Ir}$  and  $V_{Io}$  and their phase difference. Calculate the -3 dB bandwidth of the closed loop response and compare with the pre-lab prediction. During the experiment, monitor both the current sensing voltage  $V_{Io}$  and the power stage output voltage  $V_o$ . If there is significant distortion on either of them, reduce the signal generator amplitude to ensure both  $V_{Io}$  and  $V_o$  remain sinusoidal.

### 4.4 Destabilize the current controller

This experiment is designed for you to understand sources of instability of the system. Keep  $Z_3$  and  $Z_5$  the same, but remove the resistor from  $Z_4$  and leave the capacitor only. This will convert the current controller from a PI controller to a pure integrator. Set  $V_{Ir}$  to be a 10 Hz square wave with  $0.2 V_{\text{pk-pk}}$  amplitude.

1. Measure the step response of  $V_{Io}/V_{Ir}$ . Record the step response using a camera and corresponding values of  $Z_3$ ,  $Z_4$ , and  $Z_5$ . Does the system become unstable?
2. If the above system remains stable, then decrease the  $Z_4$  capacitor value by a factor of two until the system becomes unstable. Be sure to record each step response and corresponding values of  $Z_3$ ,  $Z_4$ , and  $Z_5$ .
3. Explain why the system becomes unstable.