
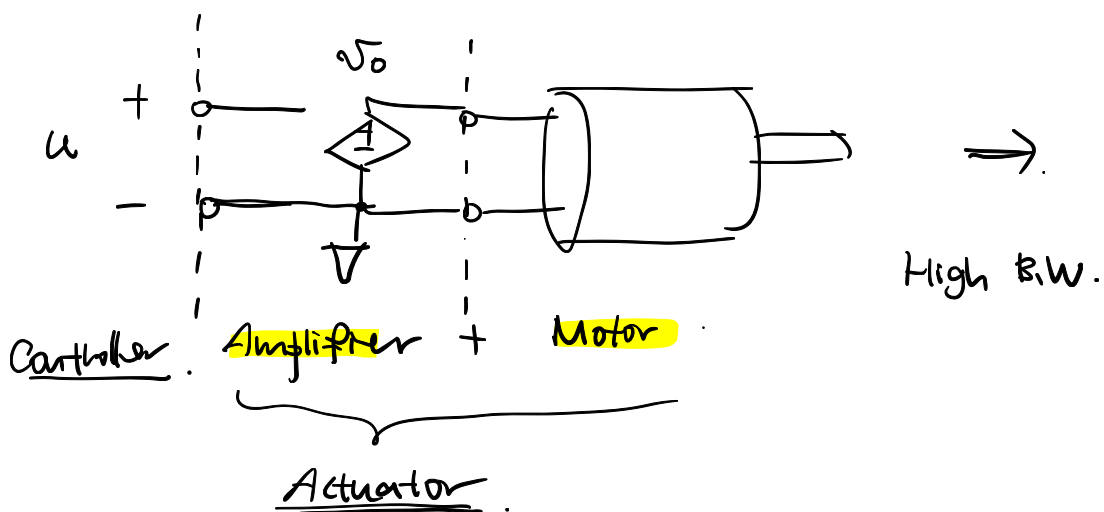


L9 – Current-controlled DC Motor

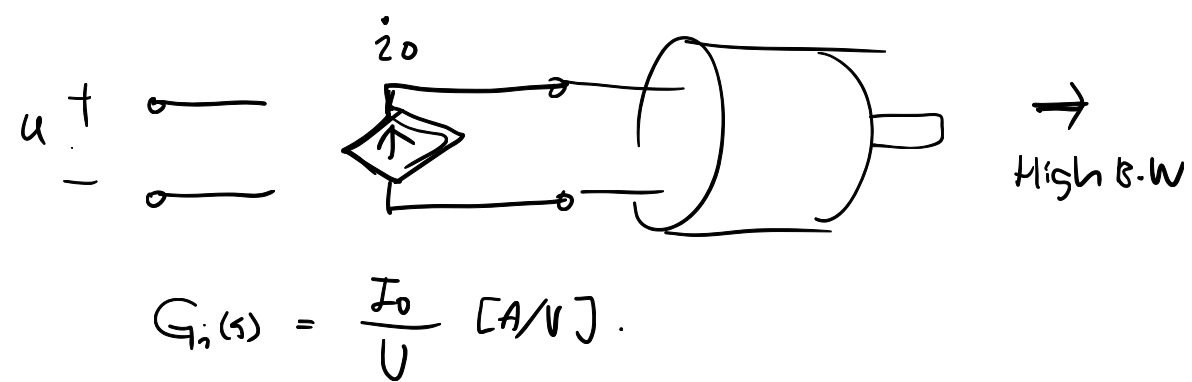


$G_v(s) = \frac{V_0}{U} \text{ [V/V]}.$

• What if




$G_i(s) = \frac{I_0}{U} \text{ [A/V]}.$

"Transconductance Am" : VCCS.

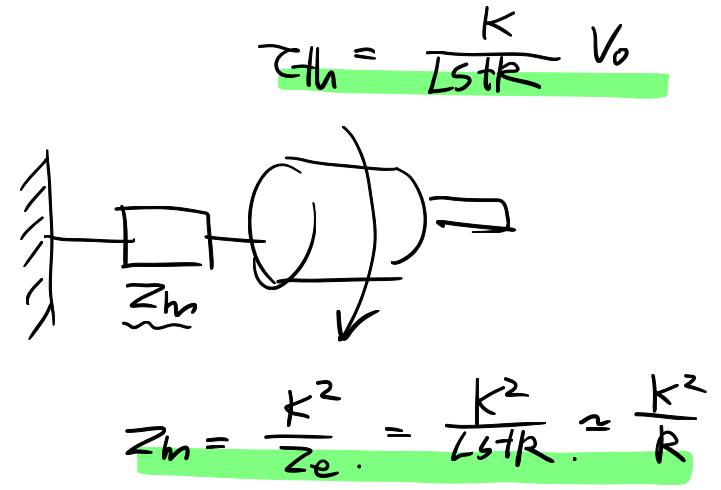

$Z_{th} = \frac{K}{Ls + R} V_0$


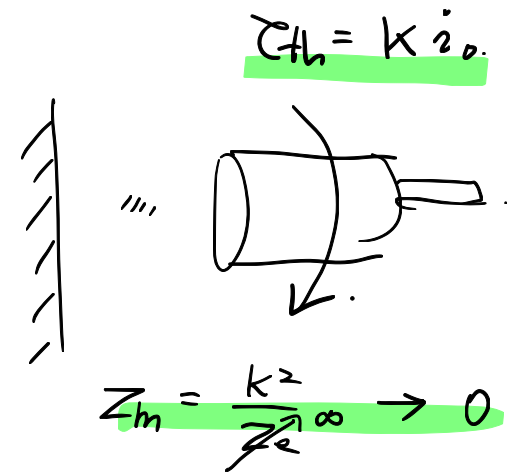
$Z_m = \frac{K^2}{Z_e} = \frac{K^2}{Ls + R} \approx \frac{K^2}{R}$




$Z_{th} = K i_0.$

$Z_m = \frac{K^2}{Z_e} \rightarrow 0$

- ① Fast torque resp | $\tau = K \cdot i$ } \Rightarrow Ideal torque source (force).
- ② Low output impedance.

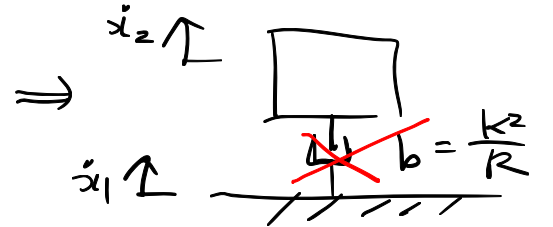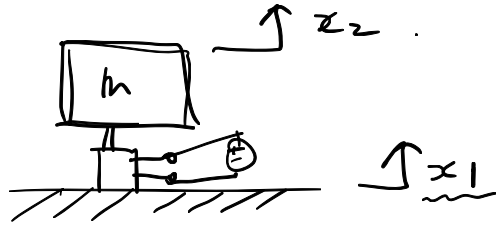


"Seismic short"

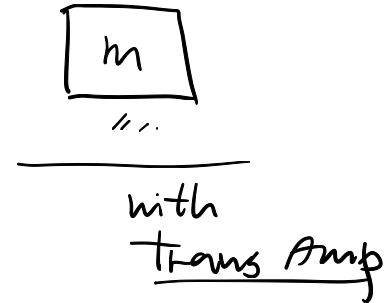

- power Amp
- Trans cond
- Motor drive
- Current drive

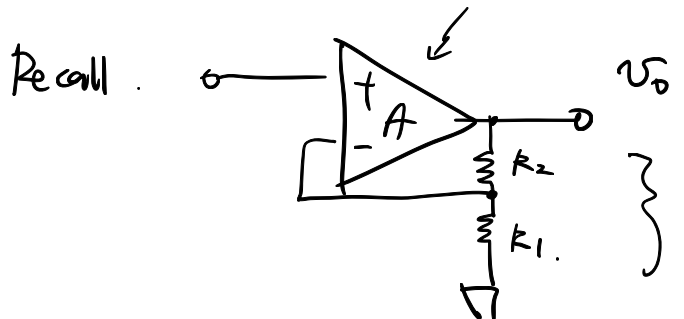Q. How can we make a controlled current source - ?



"To measure v_0 "


"Measurand"

R_2 & R_1 high enough.

\Rightarrow do not affect measurand.

{ • Measure Z_o .
 { • Feed it back.
"Strategy"

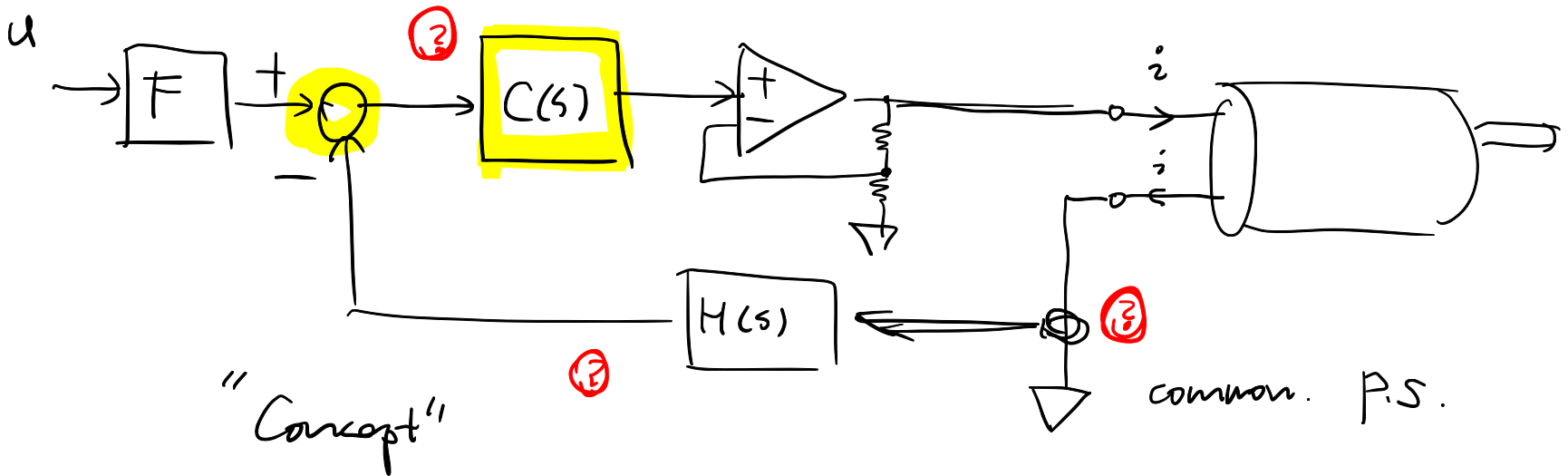
"Design question" { ① How to measure Z_o ?
 { ② How to design a feedback cont?
 { ③ How to implement a controller?



①. Current sensing . .

1. Minimally affect I_0 . $\rightarrow R_s \ll R_m$.
2. High bandwidth. \rightarrow ✓
3. Low noise. \rightarrow ✓
4. Low interference. \rightarrow
5. Low cost

trade-off.

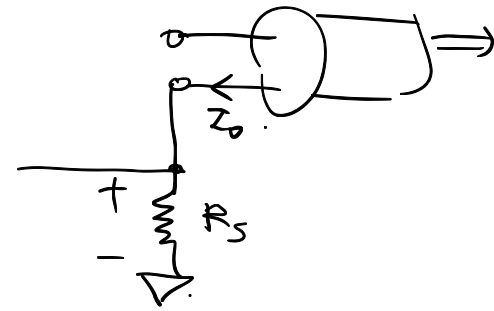




two common solutions

- ①. (Current-sensing) shunt resistor.
- ②. Hall effect sensor.

• T.C.R [K⁻¹] $\triangleq \frac{dR}{dT} \frac{1}{R}$


• $P_{max} = R_s I_{max}^2$

< Equivalent Circuit Model >

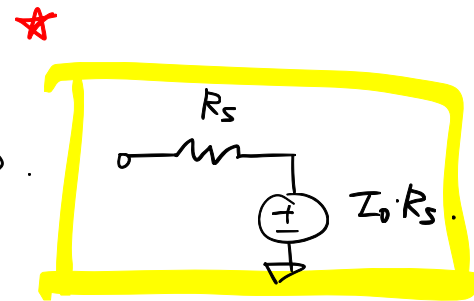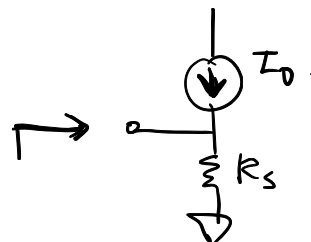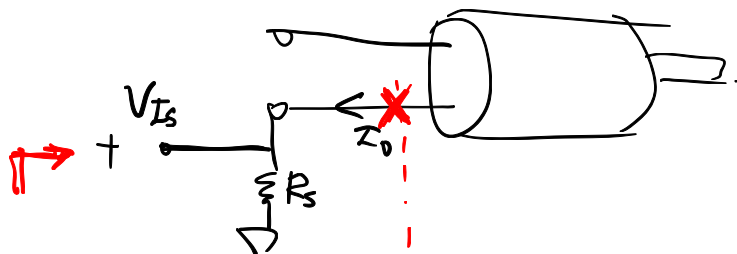

① Controller Implementation.

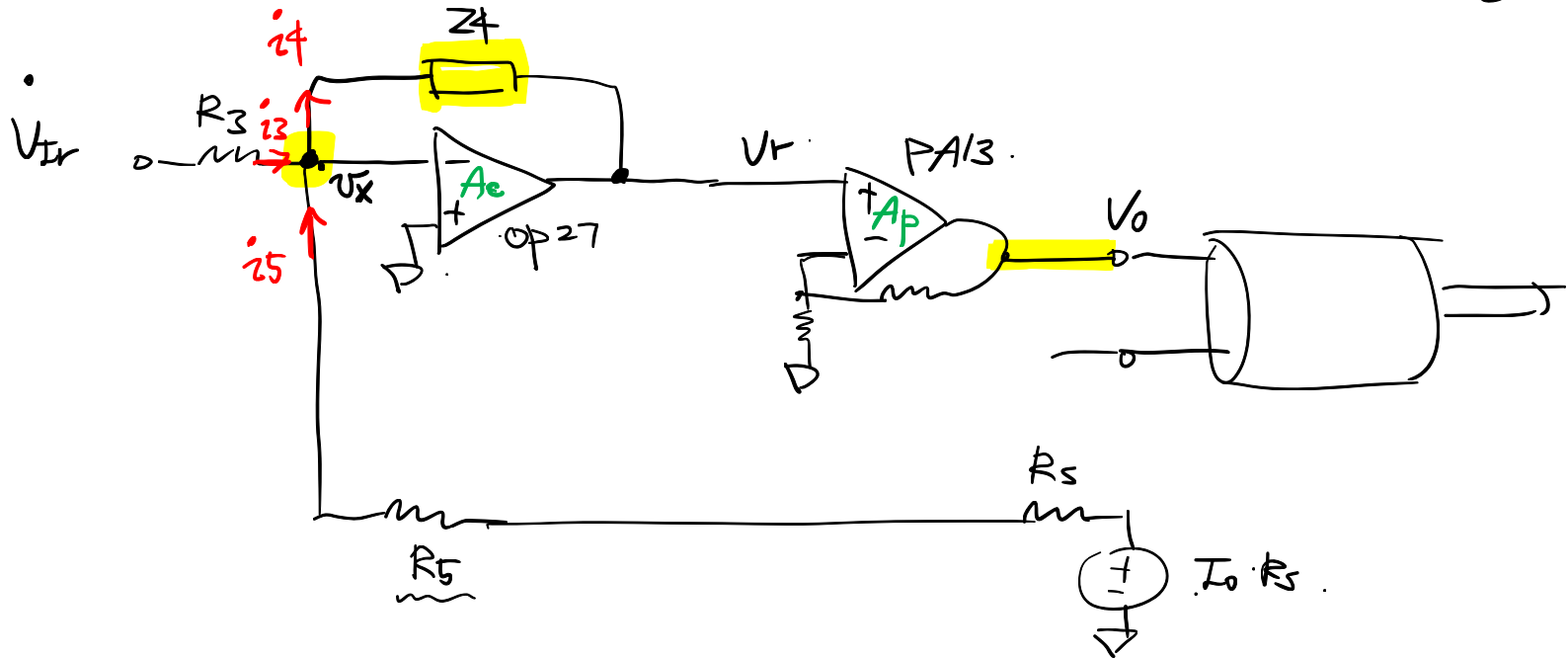- Analog circuits. — Higher B.W. vs. Digital implementation
- Lower noise. (MCU & switching electronics)



Key ideas

- Summing junction: KCL at * $\Rightarrow \underline{i_4 = i_3 + i_5}$
- Controller t.f.: $Z_4(s)$.

Virtual short approx : $v_x \approx 0$

$$V_r \approx -Z_4 i_4$$

$$= -Z_4 (i_3 + i_5)$$

Virtual short



KCL.

$$= -Z_4 \left(\frac{1}{R_3} V_{Tr} + \frac{1}{R_6 + R_5} R_5 I_o \right)$$

$$\approx -Z_4 \left(\frac{1}{R_3} V_{Tr} + \frac{R_5}{R_6} I_o \right)$$

$$\frac{R_5 \ll R_6}{\uparrow \quad \uparrow}$$

$$\ll 1 \Omega \quad R_6$$

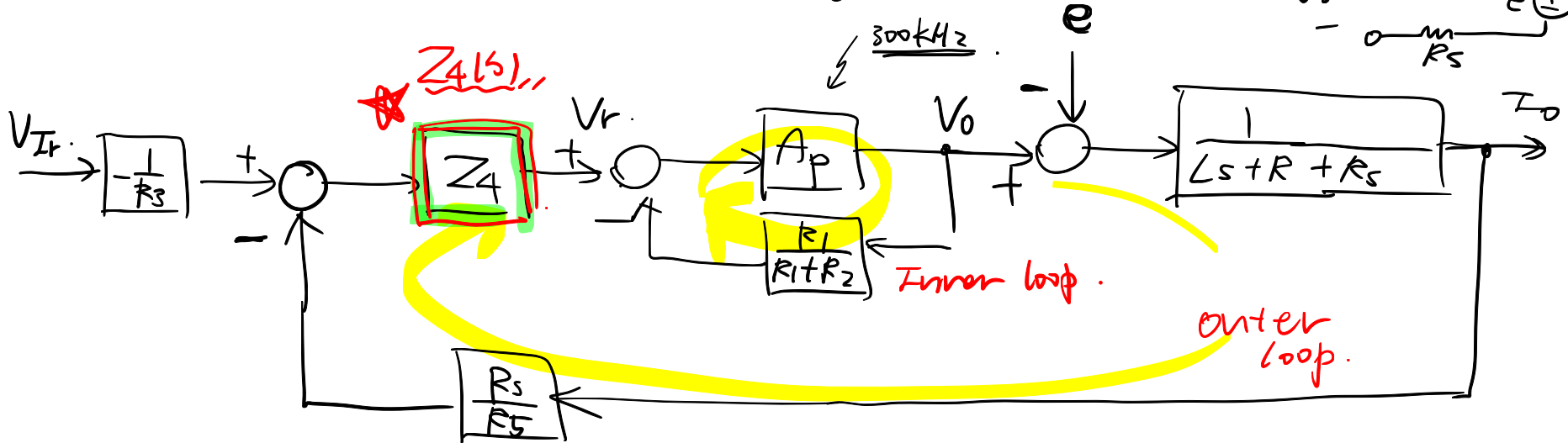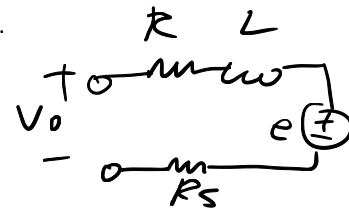

• Back - enf e : disturbance

• "Nested Loop" : Outer loop B.W. < Inner loop B.W. ,,

