

## Homework 2 – Solution

Assigned: Jan 22, 2021

Due: Jan 29, 2021

Let us consider a non-inverting amplifier shown in Fig. 1. We assume that the op-amp input impedance  $R_i$  is **infinite**, the output impedance  $R_o$  is **non-zero**, and the open-loop gain  $A$  is a **finite constant**. There is a disturbance current  $I_o$  injected into the amplifier output terminal.

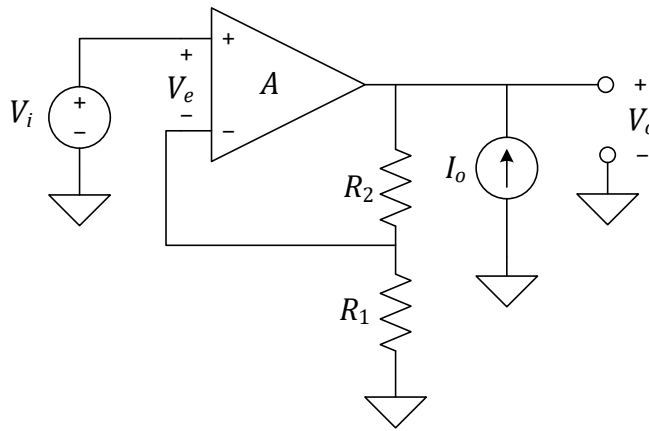


Figure 1: Schematic of a non-inverting amplifier.

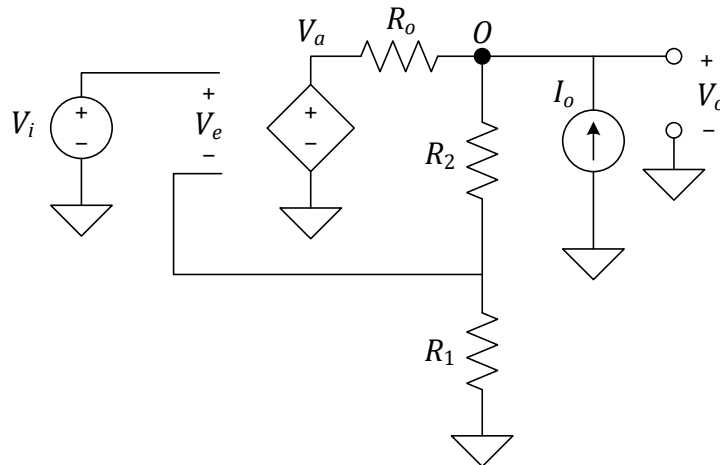


Figure 2: Equivalent circuit model.

Fig. 2 shows the equivalent circuit model. Here, the output stage of the op-amp is modeled as a dependent voltage source with a series output impedance  $R_o$ . The output from

the dependent voltage source is  $V_a = AV_e$ , where  $V_e$  is the differential voltage applied to the op-amp input signal port. Note that the amplifier output voltage  $V_o$  is not equal to  $V_a$  because  $R_o \neq 0$ .

### Problem 1

- (a) Find an expression for  $V_o$  in terms of  $V_a$  and  $I_o$  as the input variables.

**Answer:** Apply KCL at the node marked with  $O$  in Fig. 1. Since the voltage at the node  $O$  is  $V_o$ , KCL states that

$$\frac{V_o - V_a}{R_o} + \frac{V_o}{R_1 + R_2} = I_o.$$

Re-arranging the above equation for  $V_o$  leads to

$$V_o = \frac{R_1 + R_2}{R_o + R_1 + R_2} V_a + \frac{R_o + R_1 + R_2}{R_o(R_1 + R_2)} I_o$$

Alternatively, one can derive the same equation using the superposition method, i.e, find the portions of the voltage due to  $V_a$  and  $I_o$  separately and sum them up.

- (b) Find an expression for  $V_e$  in terms of  $V_i$  and  $V_o$  as the input variables.

**Answer:** The feedback voltage  $V_f$ , i.e., the voltage at the node between  $R_1$  and  $R_2$ , can be obtained by applying the voltage divider rule to  $V_o$ .

$$V_f = \frac{R_1}{R_1 + R_2} V_o.$$

Therefore, the differential voltage  $V_e$  becomes

$$V_e = V_i - \frac{R_1}{R_1 + R_2} V_o.$$

- (c) Complete the block diagram in Fig. 3.

**Answer:**

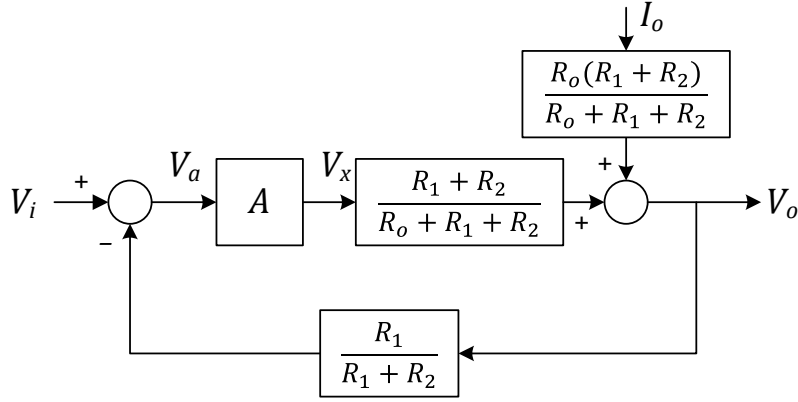


Figure 3: Block diagram.

### Problem 2

For  $R_o = 50 \Omega$ ,  $R_1 = 1 \text{ k}\Omega$ , and  $R_2 = 9 \text{ k}\Omega$ , find the amplifier gain  $V_o/V_i$  when

(a)  $A = 10^5$

**Answer:** Break the loop right before the summing junction and identify the loop transmission

$$L.T. = -A \left( \frac{R_1 + R_2}{R_o + R_1 + R_2} \right) \left( \frac{R_1}{R_1 + R_2} \right).$$

Apply the Black's formula from  $V_i$  to  $V_o$ :

$$\frac{V_o}{V_i} = \frac{\text{Forward gain}}{1 - L.T.} = \frac{A \left( \frac{R_1 + R_2}{R_o + R_1 + R_2} \right)}{1 + A \left( \frac{R_1 + R_2}{R_o + R_1 + R_2} \right) \left( \frac{R_1}{R_1 + R_2} \right)}.$$

Substituting  $R_o = 50 \Omega$ ,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 9 \text{ k}\Omega$ , and  $A = 10^5$  into the above leads to

$$\boxed{\frac{V_o}{V_i} = 9.999}$$

(b)  $A \rightarrow \infty$

**Answer:** When  $A \rightarrow \infty$ , the above analytic expression for  $V_o/V_i$  simplifies to

$$\frac{V_o}{V_i} = \frac{R_1 + R_2}{R_1}$$

Substituting  $R_1 = 1 \text{ k}\Omega$  and  $R_2 = 9 \text{ k}\Omega$  into the above leads to

$$\boxed{\frac{V_o}{V_i} = 10}$$

Note that  $R_o$  does not affect the amplifier gain when  $A \rightarrow \infty$ .

### Problem 3

For  $R_o = 50 \Omega$ ,  $R_1 = 1 \text{ k}\Omega$ , and  $R_2 = 9 \text{ k}\Omega$ , find the amplifier output impedance  $V_o/I_o$  when

(a)  $A = 10^5$

**Answer:** Apply the Black's formula from  $I_o$  to  $V_o$

$$\frac{V_o}{I_o} = \frac{\text{Forward gain}}{1 - L.T.} = \frac{\frac{R_o(R_1+R_2)}{R_o+R_1+R_2}}{1 + A \left( \frac{R_1+R_2}{R_o+R_1+R_2} \right) \left( \frac{R_1}{R_1+R_2} \right)}$$

Substituting  $R_o = 50 \Omega$ ,  $R_1 = 1 \text{ k}\Omega$ ,  $R_2 = 9 \text{ k}\Omega$ , and  $A = 10^5$  into the above leads to

$$\boxed{\frac{V_o}{I_o} = 0.005 \Omega}$$

(b)  $A \rightarrow \infty$

**Answer:** When  $A \rightarrow \infty$ , the above analytic expression converges to zero. Therefore,

$$\boxed{\frac{V_o}{I_o} = 0 \Omega}$$

#### Problem 4

Let us consider an op-amp circuit shown in Figure 4. We assume that the op-amp is **ideal**, i.e., the input impedance  $R_i$  is infinite, the output impedance  $R_o$  is zero, and the open-loop gain  $A$  is infinite.

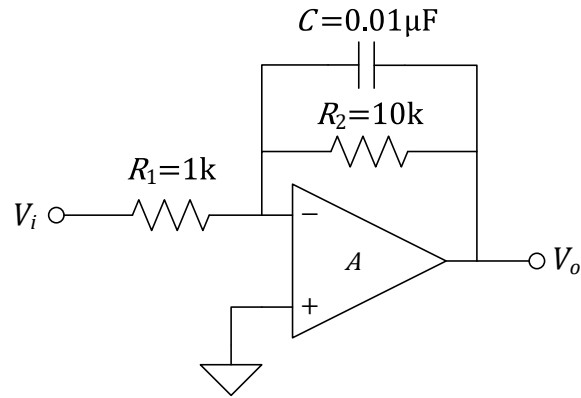


Figure 4: Schematic of a non-inverting amplifier.

- (a) Derive the transfer function  $V_o(s)/V_i(s)$

**Answer:**


$$\frac{V_o}{V_i} = -\frac{Z_2}{Z_1} = -\frac{1}{R_1} \left( \frac{1}{C s} \parallel R_2 \right) = -\frac{R_2}{R_1} \left( \frac{1}{R_2 C s + 1} \right)$$

Therefore,

$$\boxed{\frac{V_o}{V_i} = -10 \left( \frac{1}{0.0001s + 1} \right)}$$

- (b) Plot the Bode plot and the step response.

**Answer:**

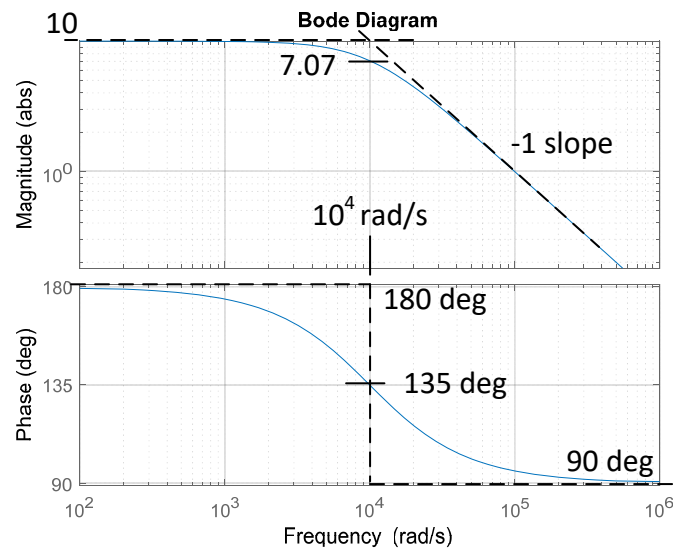

Note that the op-amp circuit behaves as a constant gain at low frequencies and as an integrator at high frequencies. The transition occurs at a frequency (break frequency) determined by  $C$  and  $R_2$ . Below this frequency the parallel branch consisting of  $C$  and  $R_2$  looks like a resistor, whereas above this frequency the parallel branch looks like a capacitor.

