
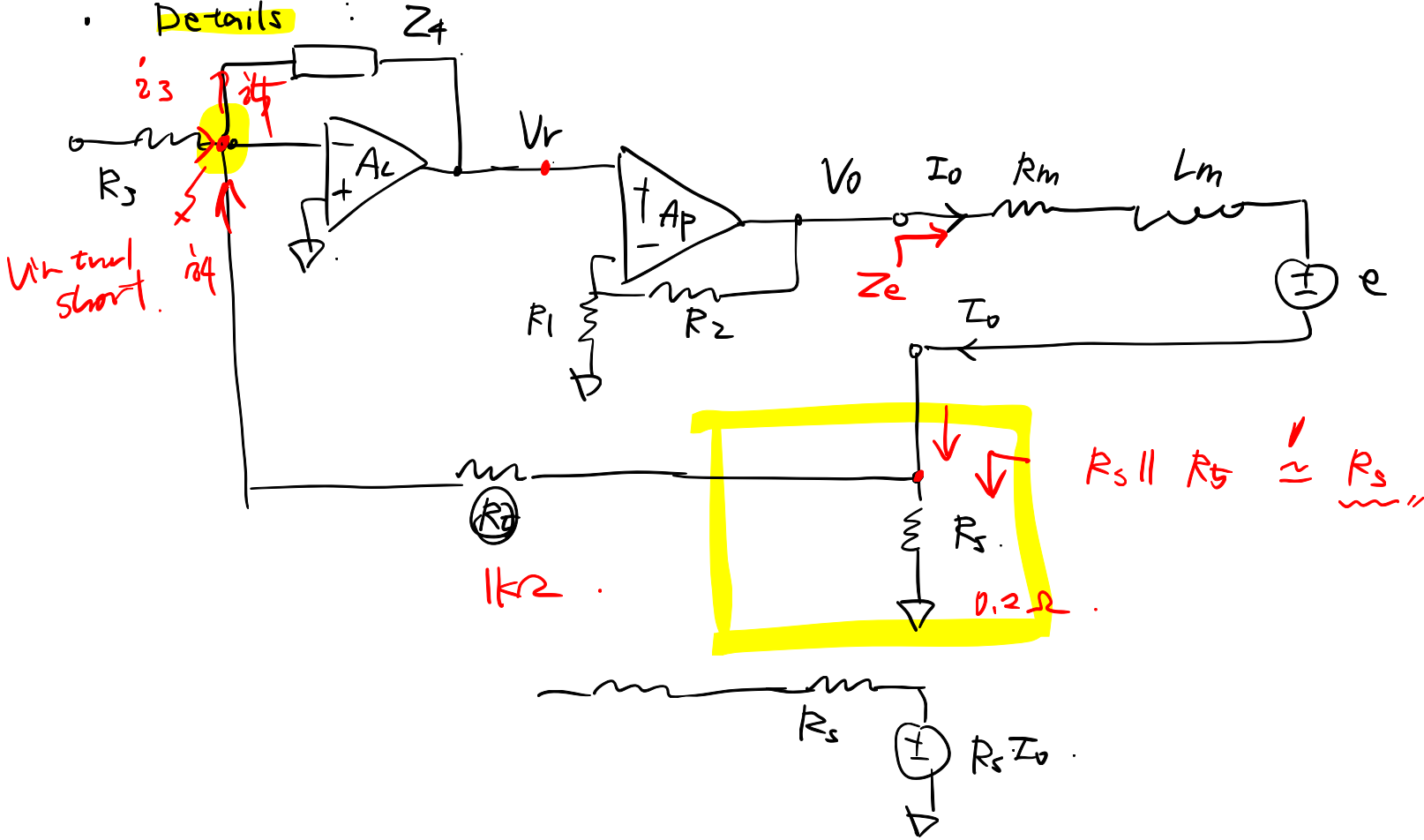


L10 – Transconductance Amplifier Design

Design process : "Coarse to Fine"

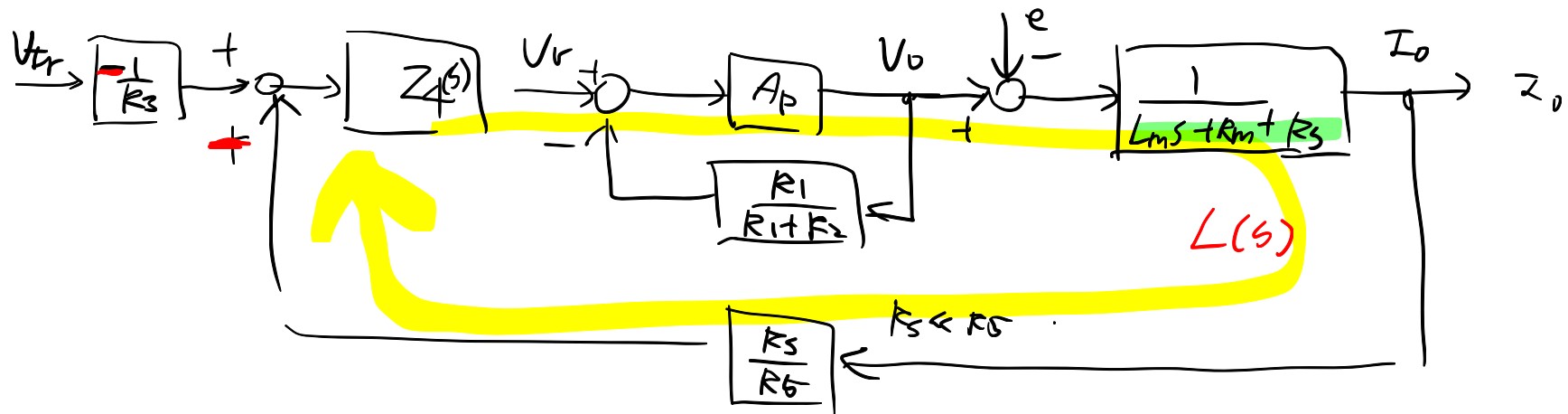- Strategy : current sensing + feedback .
- Concept : analog implementation .
- Details :






Need to select "Design parameters" to meet "Design Specs" "Detail"

< Design Spec >

I { • DC Gain

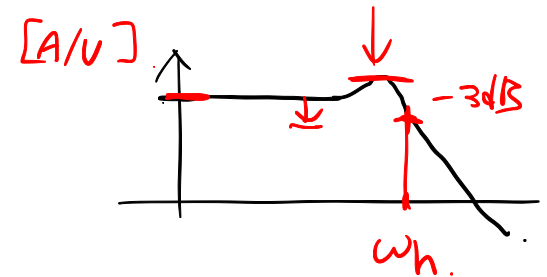
II { • Bandwidth  $\longleftrightarrow \omega_c$   
• Resonance peak  $\longleftrightarrow \phi_m$  } Loop shaping.


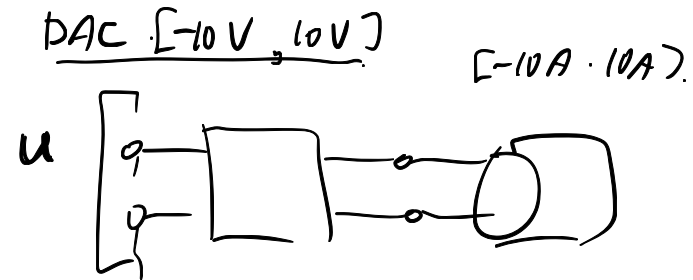
# I. bc gain design.

- $-1$  [A/V].


- { Max current. of motor.  
DAC output range



- Assume  $\left. L(j\omega) \right|_{\omega \rightarrow 0} \rightarrow \infty$ ,  $\left. \frac{I_o}{V_{Zr}} \right|_{\omega=0} = - \frac{1}{R_s} \cdot \frac{R_o}{R_s} = -1$

- $I_f$   $\star$   $R_s = 0.2 \Omega$   $\rightarrow$  { Pick  $R_5$  such that  $R_5 \gg R_s$  :  $R_5 = 1k\Omega$   
Pick  $R_3 \rightarrow \frac{1}{k_3} \frac{k_5}{R_s} : 1 \rightarrow$   $R_3 = 5k\Omega$

## V. Loop Shaping.


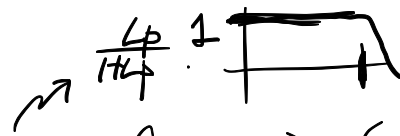


$$L(s) = \underbrace{Z_f(s)}_{C(s)} \cdot \underbrace{T_p(s) \left( \frac{K_1 + R_2}{R_1} \right) \left( \frac{1}{L_m s + R_m + R_5} \right) \left( \frac{R_5}{R_5} \right)}_{P(s)}$$



- Design  $C(s) = Z_f(s)$  such that  $L(s) = C \cdot P$  achieves a "desired loop shape"

- $C(s)$  "Compensator"   
 Compensates ( $L(s)$ ) for  $\begin{pmatrix} \text{mag} \\ \text{diff} \\ \text{phase} \end{pmatrix}$

- o Desired Loop shape

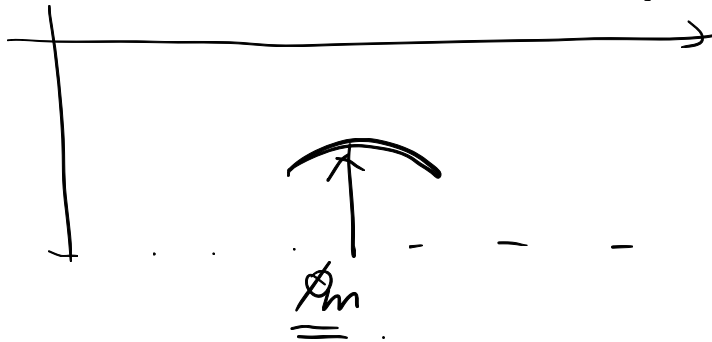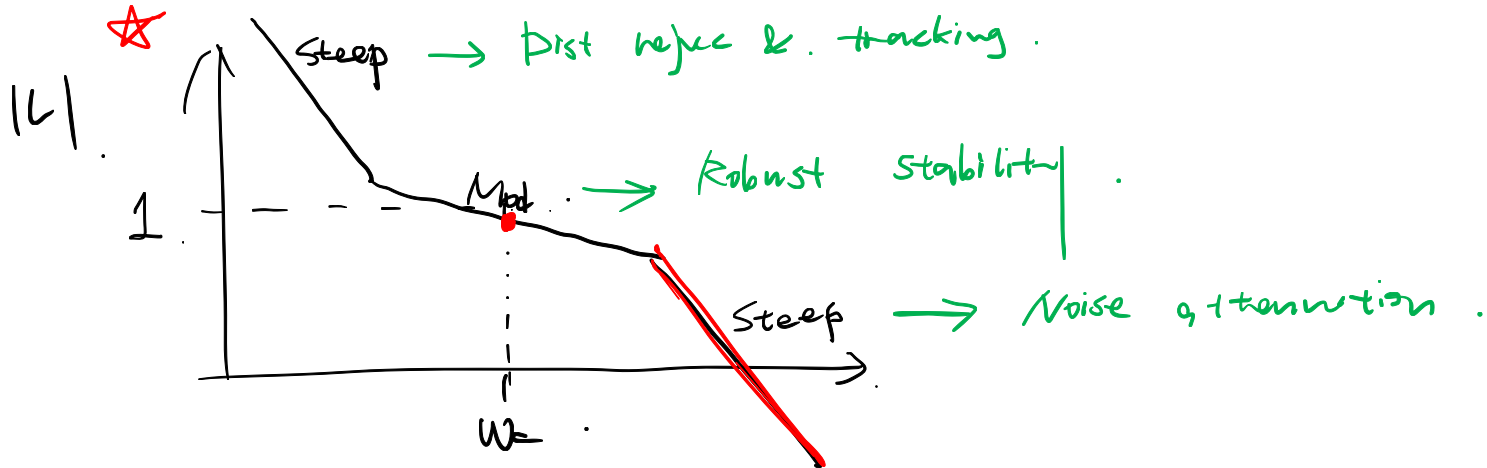

$$\phi \approx 90^\circ \cdot n$$

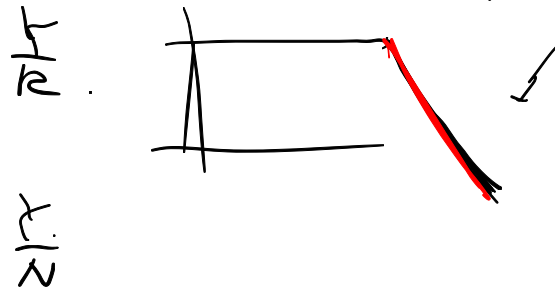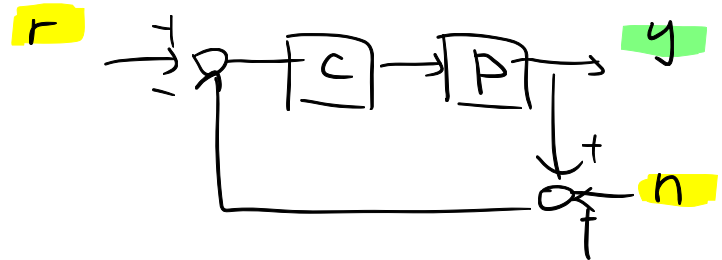


- Loop shape before comp.

$$p(s) = T_p(s) \frac{R_1 R_2}{R} \left( \frac{1}{L_m s + R_m + R_5} \right) \cdot \frac{R_5}{R_6}$$

$$\begin{aligned} L_m &= 1 \text{ mH} \\ R_m &= 6 \Omega \\ R_1 &= 1 \text{ k}\Omega \\ R_2 &= 9 \text{ k}\Omega \\ R_5 &= 0.2 \Omega \\ R_6 &= 1 \text{ k}\Omega \end{aligned}$$
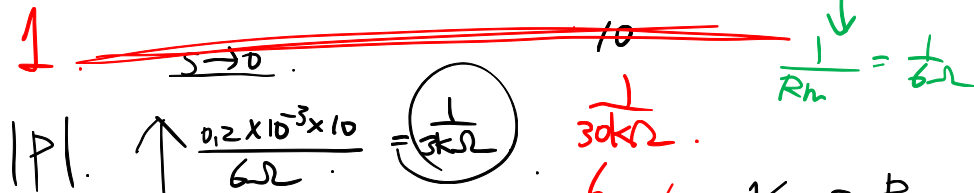
$$\frac{0.2 \Omega}{1 \text{ k}\Omega} = 0.2 \times 10^{-3}$$




$$K_p = P_4$$

$$2\pi \approx 6$$

"

$$\frac{6 \times 10^3 \text{ rad/s}}{1 \text{ mH}} \approx \frac{6 \Omega}{1 \text{ mH}} = \frac{R_m}{L_m} \approx 1 \text{ kHz}$$

$$300 \text{ kHz}$$

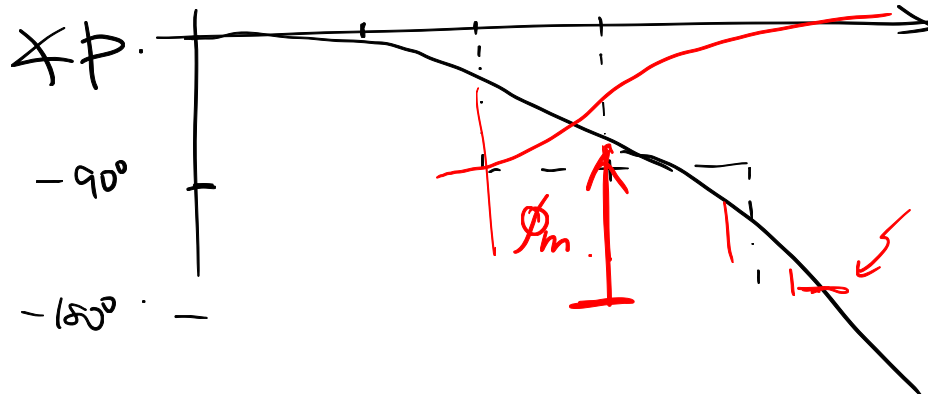


## Di FRiciencies


- Low loop gain.
  - Flat dc loop gain
- want "steep" slope

< Loop shaping steps >.
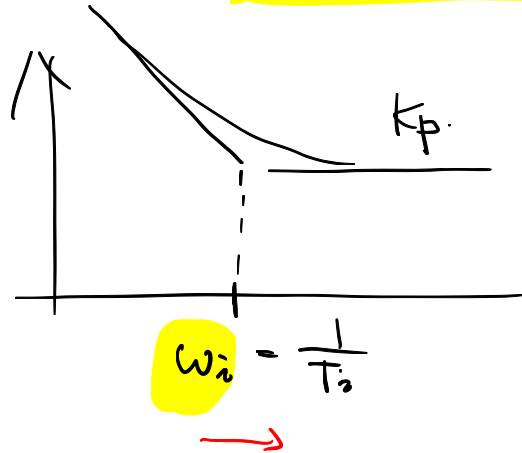
$$\textcircled{1} \quad C(s) = K_p \left( 1 + \frac{1}{T_i s} \right) = K_p \left( 1 + \frac{\omega_i}{s} \right) = Z_4(s).$$



$\Rightarrow$

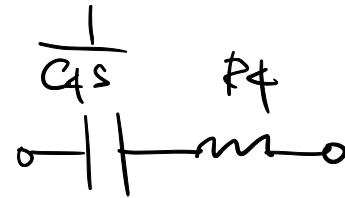


$$Z_4(s) = K_p \left( 1 + \frac{1}{R_4 C_i s} \right)$$

$\textcircled{3}$  Select  $\omega_c$  by considering  $\phi_m$


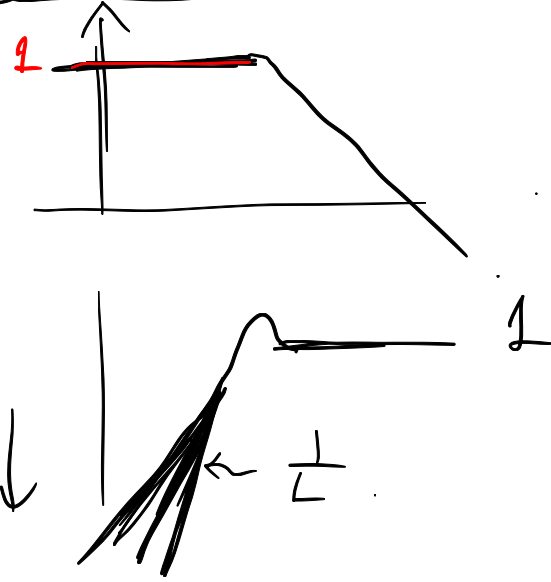
$$L(s) \quad \begin{cases} T. = \frac{L}{1+L} \\ S = \frac{1}{1+L} \end{cases}$$



e.g.) set  $\phi_m > 60^\circ$  .  $30^\circ$  .

$$\omega_c = 10 \text{ kHz} \rightarrow \phi_m = 90^\circ .$$

③ . Raise  $k_p$  .  $|L(j\omega)| = 1$  at  $\omega = \omega_c$  .


$$\frac{R_f}{30 \text{ k}\Omega} = 1 \Rightarrow \underline{R_f = 30 \text{ k}\Omega}$$

④ . Introduce the integrator . by selecting  $(W_i)$

e.g.  $\frac{1}{R_f C_f} \approx \underline{1 \text{ kHz}}$  .  $(\frac{1}{5})$



10 kHz .
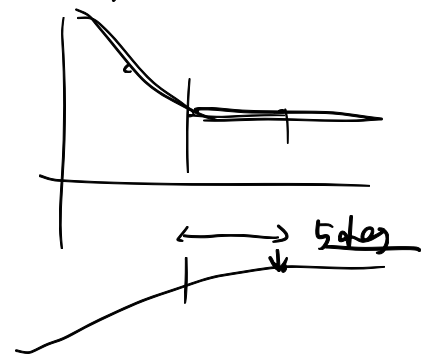
$$\Rightarrow \boxed{C_f \approx 5.5 \text{ nF}}$$



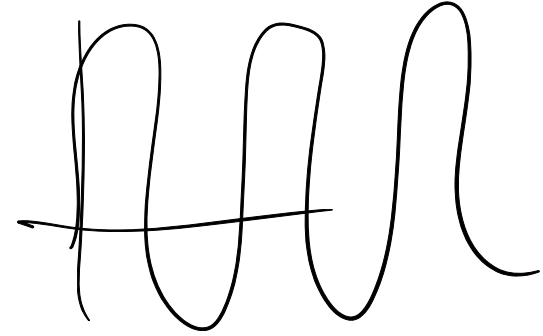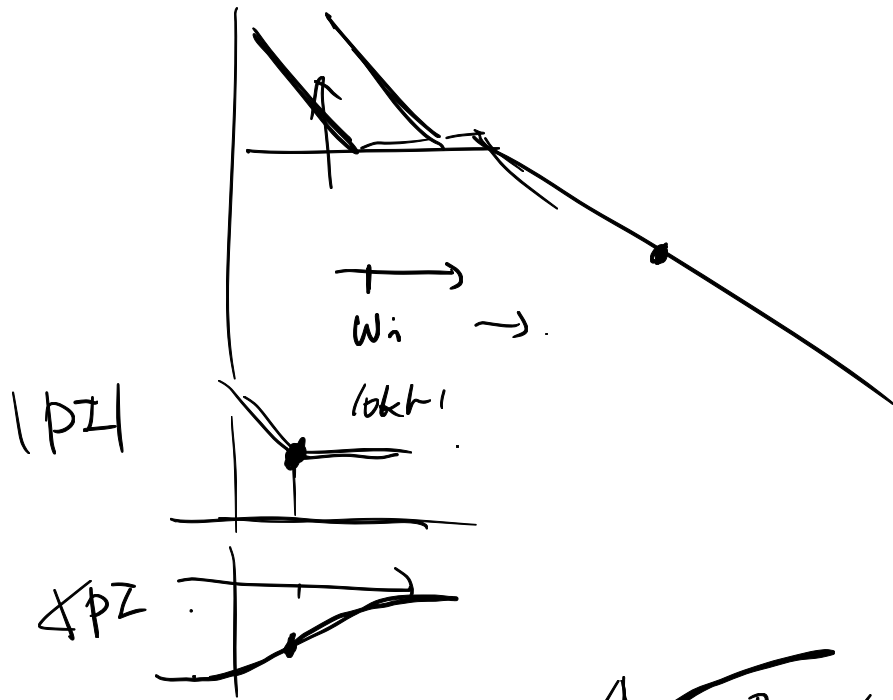"Trade-off" { low  $W_i \rightarrow$  weak dist reject  
band tracking .  
Low  $W_i \rightarrow$  sacrifices  $\phi_m$





$\uparrow$   
 $\underline{90^\circ} = \phi_m$  .  $\downarrow$   $\underline{45^\circ \text{ dec}}$  .  $\downarrow$   $\underline{0 \text{ deg}}$