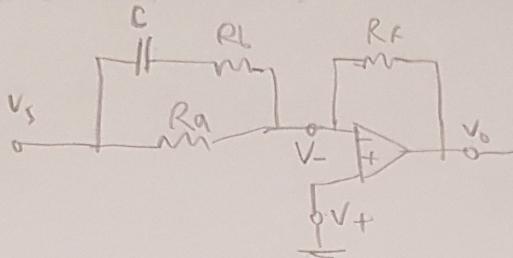


Q1

Rathnayake Pratip
#63205165

$$V_+ = V_- = 0 \text{ V}$$

$$\text{Total: } 82 + 12 = 94$$

$$\frac{V_o}{R_f} + \frac{V_s}{R_a} + C \frac{dV_c}{dt} = 0 \quad \text{Node current rule}$$

$$V_s = V_c + \frac{dV_c}{dt} C R_b \rightarrow V_c = V_s - \frac{dV_c}{dt} C R_b$$

$$\text{for } G(s) \rightarrow Z_C = \frac{1}{sC}$$


$$\frac{V_o}{R_f} + \frac{V_s}{\left(\frac{1}{R_a} + \frac{1}{Z_C + R_b}\right)} = 0 \rightarrow V_o = \frac{-R_f V_s}{\left(\frac{1}{R_a} + \frac{1}{Z_C + R_b}\right)}$$

$$G(s) = \frac{V_o}{V_s} = -R_f \left(\frac{R_a + Z_C + R_b}{R_a (Z_C + R_b)} \right) \left(\frac{sC}{sC} \right)$$

$$= -R_f \left(\frac{sC(R_a + R_b) + 1}{R_a(sCR_b + 1)} \right)$$

$$= -\frac{R_f}{R_a} \times \left(\frac{sC(R_a + R_b) + 1}{sCR_b + 1} \right) \times \frac{1}{sCR_b + 1}$$

P67

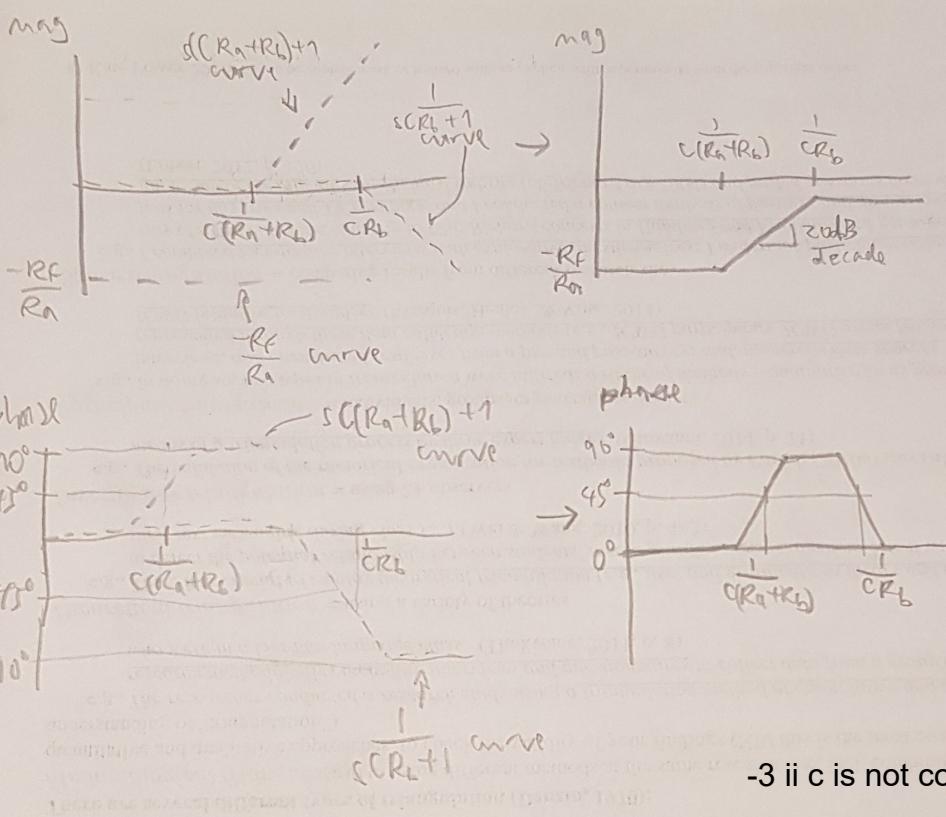

-3 ii c is not correct

ii a) SS gain $\approx \lim_{s \rightarrow 0} G(s)$

$$\approx -\frac{R_f}{R_a}$$

b) $\text{Im } G(j\omega) \approx -\frac{R_f}{R_a} + 20\text{dB} \left(\log \left(\frac{1}{CR_b} - \frac{1}{C(R_a+k_b)} \right) \right)$ [from plot]

c) lead $= 0^\circ \text{ or } 0 \text{ rad}$

d) $\frac{1}{C(R_a+R_b)} \text{ & } \frac{1}{CR_b}$

PG 2

At low frequency, acts like inverting amplifier

At mid frequency, acts like measurement tool (16) proportional to ω)

At high frequency, acts like inverting amp again

-5 iii a: the result is not correct

a)

at $\omega = 100 \frac{1}{s}$, $V_s = \frac{V_{max} \omega}{\omega_{max}}$, $V_o = 6V$, find R_f

$$V_o = -R_f (sC(R_a + R_b)H)$$

$$V_s = R_a (sC R_b + 1)$$

$$R_f = \frac{R_a V_o}{V_s} = \frac{s C R_b + 1}{s C (R_a + R_b) + 1} \rightarrow s = j\omega$$

$$= 10K \left(\frac{1}{j100} \right) \left(j100 (2 \times 10^{-6}) 2000 + 1 \right) = j$$

$$= \frac{1}{j(100)(2 \times 10^{-6})(12 \times 10^3)} + 1$$

Sensitivity $\propto \frac{\partial V_o}{\partial V_s}$

$$\frac{\partial V_o}{\partial V_s} = \frac{1}{s C (R_a + R_b)}$$

$$\text{at } \omega = 0 \rightarrow 0 \sim 41.67 \frac{\text{rad}}{\text{s}} \text{ low freq}$$

$$\frac{1}{s C (R_a + R_b)} \sim \frac{1}{s C R_L} \rightarrow 41.67 \frac{\text{rad}}{\text{s}} \approx 250 \frac{\text{rad}}{\text{s}} \text{ mid freq}$$

$$\frac{1}{s R_b} \sim \infty \rightarrow 250 \sim \infty \frac{\text{rad}}{\text{s}} \text{ high freq}$$

From Nyquist frequency rule, $f_{c2} = f_s$, or
sampling rate has to be double of operating frequency PS3

So for low freq $\rightarrow f_S = 83 \text{ rad/s}$

$$\text{mid freq} \rightarrow f = 500 \text{ rad/s}$$

hi freq \rightarrow $f_3 = \text{double set frequency at operation}$

Q2


$$\text{i) } R \propto R_0 e^{(\beta(\frac{1}{T} - \frac{1}{T_0}))}$$

$$R(T_0) = R_0 e^{(\beta(\frac{1}{T_0} - \frac{1}{T_0}))}$$

$$\Rightarrow R_0 e^{\beta 0}$$

$$\Rightarrow R_0 (1)$$

$$\Rightarrow R_0$$

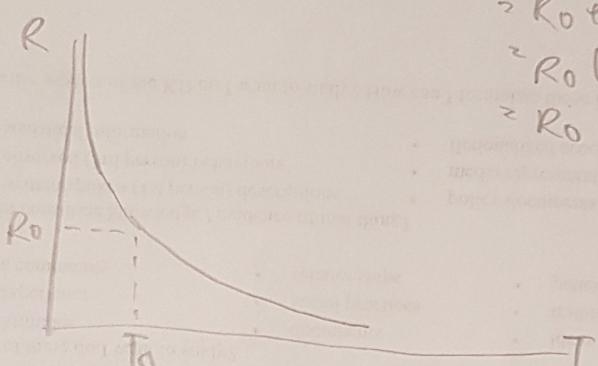

-5 ii a: the final equation is wrong

-5 ii b: the result is wrong

C iii)

$$\frac{R}{R_0} = e^{\beta(\frac{1}{T} - \frac{1}{T_0})}$$

a)

$$\ln R - \ln R_0 = \beta \left(\frac{1}{T} - \frac{1}{T_0} \right) = \beta \left(T^{-1} - T_0^{-1} \right)$$


$$\frac{\partial R}{R} = \frac{8R_0}{R} = \beta \left(-\frac{8T}{T^2} \right)$$

$$e_T - e_{R_0} = \beta \frac{e_T}{T}$$

$$e_T^2 \frac{I}{\beta} (e_{R_0} - e_R)$$

for large T, small e_T and e_R

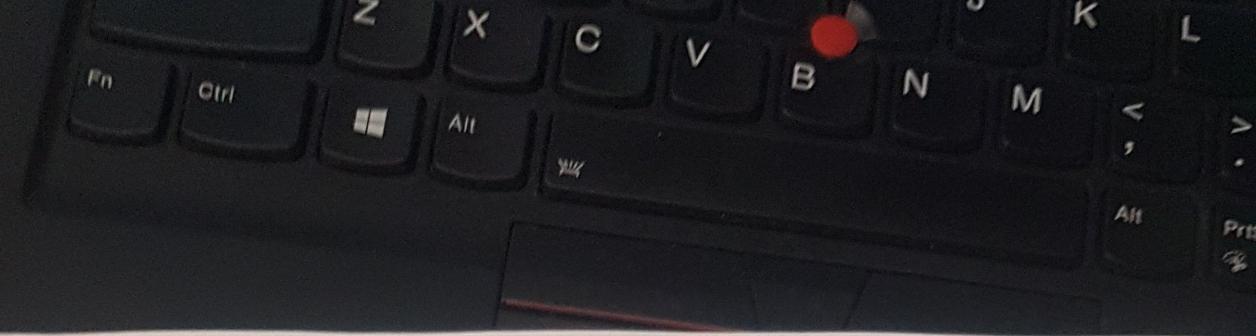$\delta I \propto T$ \Rightarrow larger T result in larger e_T



9.11.2)

$$e_T = \frac{(400\text{K})}{(4200\text{K})} (0.02 - 0.01)$$

$$\approx \pm 9.52 \times 10^{-4}$$