

Let us consider an op-amp circuit in Figure 1. We assume that the op-amp has infinite input impedance, zero output impedance, and open-loop transfer function  $A(s)$ . Figure 3 shows the Bode plot of  $A(s)$ .

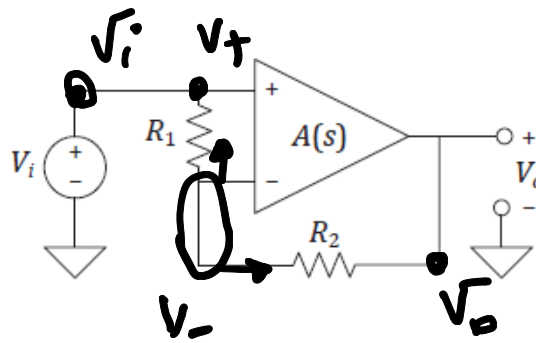


Figure 1: Op-amp circuit for Problem1.

- (a) (20 pt.) Draw a block diagram that shows the feedback relation between the input voltage  $V_i(s)$  and output voltage  $V_o(s)$ .

$$\text{KCL: } \frac{V_+ - V_-}{R_1} + \frac{V_- - V_o}{R_2} = 0$$

$V_+ = V_i$

$$\xrightarrow{R_1 R_2} R_2 (V_- - V_i) + R_1 (V_- - V_o) = 0$$

$$R_2 V_- - R_2 V_i + R_1 V_- - R_1 V_o = 0$$

$$\Rightarrow (R_2 + R_1) V_- = R_2 V_i + R_1 V_o$$


$$V_- = \frac{R_2}{R_2 + R_1} V_i + \frac{R_1}{R_1 + R_2} V_o$$

$$V_o = A(s) (\underbrace{V_+}_{V_i} - \underbrace{V_-}_{V_o})$$

$$V_o = A(s) \left( V_i - \underbrace{\frac{R_2}{R_2 + R_1} V_i - \frac{R_1}{R_1 + R_2} V_o}_{\text{feedback}} \right)$$

$$V_o = A(s) \left( \underbrace{\frac{R_1}{R_1 + R_2}}_{\text{forward}} V_i - \underbrace{\frac{R_1}{R_1 + R_2}}_{\text{feedback}} V_o \right)$$
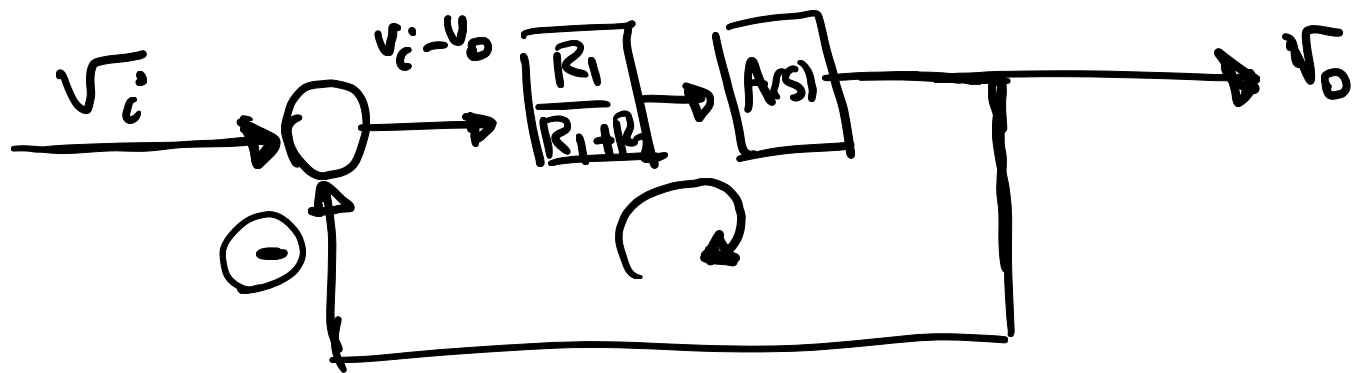
$$V_o = A(s) \left( \frac{R_1}{R_1 + R_2} \right) (V_i - V_o)$$



(b) (10 pt.) Find the expression for the loop transfer function  $L(s)$  in terms of  $R_1$ ,  $R_2$ , and  $A(s)$ .

loop transfer function = - L.T.

$$= - \left( - \frac{R_1}{R_1 + R_2} \times A(s) \right) \Rightarrow$$

$$L(s) = \frac{R_1}{R_1 + R_2} A(s)$$

(c) (20 pt.) For  $R_1 \rightarrow \infty$ ,  $R_2 = 1 \text{ k}\Omega$ , and  $A(s)$  given in Figure 3, find the gain crossover frequency  $\omega_c$  and phase margin  $\phi_m$  of  $L(s)$ .

$$|L(j\omega)|_{\omega=\omega_c} = 1$$

$$R_1 \rightarrow \infty \Rightarrow \frac{R_1}{R_1 + R_2} \simeq 1 \Rightarrow \underline{L(s) = A(s)}$$

$$\underline{|A(j\omega)|_{\omega=\omega_c} = 1} \xrightarrow{\text{Fig 3}} \omega_c = 10^7 \text{ Hz}$$

$$\phi_m = \angle L(j\omega) + 180^\circ$$

$$\angle L(j\omega_c) = -110^\circ \xrightarrow{\text{Fig 3.}} \phi_m = -110 + 180 = 70^\circ$$

(d) (30 pt.) For  $R_1 = 1 \text{ k}\Omega$  and  $A(s)$  given in Figure 3, find the resistance value  $R_2$  that makes the closed-loop transfer function  $G(s) = V_o(s)/V_i(s)$  achieve a -3 dB bandwidth of 100 kHz.

-3dB bandwidth

$\omega_h$

closed-loop transfer function

$G(s)$

crossover frequency

$\omega_c$

loop transfer function

$L(s)$

if  $\phi_m = 90^\circ \Rightarrow \omega_h = \omega_c$

①

$\omega_h \approx \omega_c$

$$G(s) = \frac{\left( \frac{R_1}{R_1 + R_2} \right) A(s)}{1 + \frac{R_1}{R_1 + R_2} A(s)} = \frac{f A(s)}{1 + f A(s)}$$

$R_2 \rightarrow ?$

$$\omega_h = \underline{100 \text{ kHz}} = \underline{\omega_c}$$

$$|L(j\omega)|_{\omega = 100 \text{ kHz}} = 1$$

$$\left| \frac{R_1}{R_1 + R_2} A(j\omega) \right|_{\omega = 100 \text{ kHz}} = 1$$

$$\frac{R_1}{R_1 + R_2} |A(j\omega)|_{\omega=100\text{kHz}} = 1$$

$$|A(j\omega)|_{\omega=100\text{kHz}} = 10^5 = 100$$

$$\Rightarrow \frac{R_1}{R_1 + R_2} (100) = 1 \Rightarrow \frac{R_1}{R_1 + R_2} = \frac{1}{100}$$

$$\frac{1}{1 + R_2} = \frac{1}{100}$$

$$\Rightarrow R_2 = 99\text{k}\Omega$$

②  $|G(j\omega)|_{\omega=100\text{kHz}} = -3\text{dB} = \frac{1}{\sqrt{2}}$  ✓

$$\left| \frac{A(j\omega)}{1 + A(j\omega)} \right|_{\omega=100\text{kHz}} = \frac{1}{\sqrt{2}}$$

$$A(j\omega) = A(10^5 j) = 100 \angle -90^\circ = 100 e^{-\frac{\pi}{2}j} = -100j$$

$$\left| \frac{-100fj}{1-100fj} \right| = \frac{1}{\sqrt{2}}$$

$$\left| \frac{-100fj(1+100fj)}{(1-100fj)(1+100fj)} \right| = \left| \frac{-100fj + 10^4 f^2}{1+10^4 f^2} \right| = \frac{1}{\sqrt{2}}$$

$$\sqrt{\left(\frac{100f}{1+10^4 f^2}\right)^2 + \left(\frac{10^4 f^2}{1+10^4 f^2}\right)^2} = \frac{\sqrt{(100f)^2 + (10^4 f^2)^2}}{1+10^4 f^2} = \frac{\sqrt{2}}{2}$$

$$\frac{\sqrt{10^8 f^2 + 10^8 f^4}}{1+10^4 f^2} = \frac{\sqrt{10^8 f^2(1+10^4 f^2)}}{1+10^4 f^2}$$

$$= \frac{10^2 f \sqrt{1+10^4 f^2}}{1+10^4 f^2} = \frac{\sqrt{2}}{2}$$

$$\Rightarrow 10^2 f = 1 \Rightarrow f = \frac{1}{100}$$

$$1+10^4 f^2 = 2 \Rightarrow 10^4 f^2 = 1 \Rightarrow \boxed{f = \frac{1}{100}}$$

(e) (20 pt.) What is the dc gain of  $G(s)$  designed in part (d)?

$$R_1 = 1 \text{ k}\Omega, R_2 = 99 \text{ k}\Omega, f = \frac{R_1}{R_1 + R_2} = \frac{1}{100}$$

$$|G(j\omega)|_{\omega=0} = \frac{f A(j\omega)}{1 + f A(j\omega)}$$

$$= \left| \frac{0.01 \underline{A(0)}}{1 + 0.01 \underline{A(0)}} \right| = \frac{0.01 \times 10^6}{1 + (0.01 \times 10^6)} = \frac{10^4}{1 + 10^4}$$

$$\approx \underline{1} = 0.9999$$


(f) (30 pt.) Suppose  $G(s)$  designed in part (d) is excited with an input voltage

$$V_i(t) = 0.1 \cos(2\pi \times 10^5 t)$$

which is a persistent sinusoid defined for all time including  $t < 0$ . Find the magnitude  $M_o$  and phase  $\phi_o$  of the output voltage

$$V_o(t) = M_o \cos(2\pi \times 10^5 t + \phi_o)$$
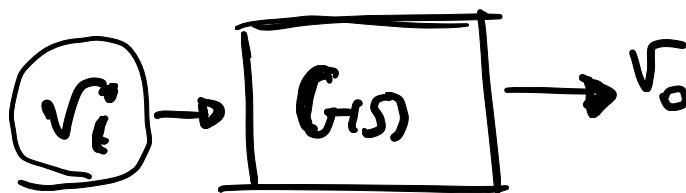
$$G(s) = \frac{0.01 A(s)}{1 + 0.01 A(s)}$$



$$A \cos(2\pi f t + \phi)$$

$$A |G(s)|_{\omega=f} \cos(2\pi f t + \phi + \angle G(s)_{\omega=f})$$

$$|G(j\omega)|_{\omega=2\pi \times 10^5 \text{ rad/s} = 10^5 \text{ Hz}}$$

$$= \left| \frac{0.01 A(j\omega)}{1 + 0.01 A(j\omega)} \right|_{\omega=10^5 \text{ Hz}} = \left| \frac{(0.01)(-100j)}{1 + (0.01)(-100j)} \right|$$

$$A(j\omega)_{\omega=10^5 \text{ Hz}} = 100 \angle -90^\circ = -100j$$

$$= \left| \frac{-j}{1-j} \right| = \left| \frac{-j(1+j)}{(1-j)(1+j)} \right| = \left| \frac{-j+1}{1+1} \right| = \left| \frac{-j+1}{2} \right|$$



$$= \sqrt{\left(\frac{1}{2}R\right)^2 + \left(\frac{1}{2}\right)^2} = \frac{1}{\sqrt{2}}$$

$$\angle \frac{-j}{1-j} = \arctan\left(\frac{-\frac{1}{2}}{\frac{1}{2}}\right) = -45^\circ$$

$$V_o = \frac{1}{\sqrt{2}} \cos(2\pi \times 10^5 t - 45^\circ)$$

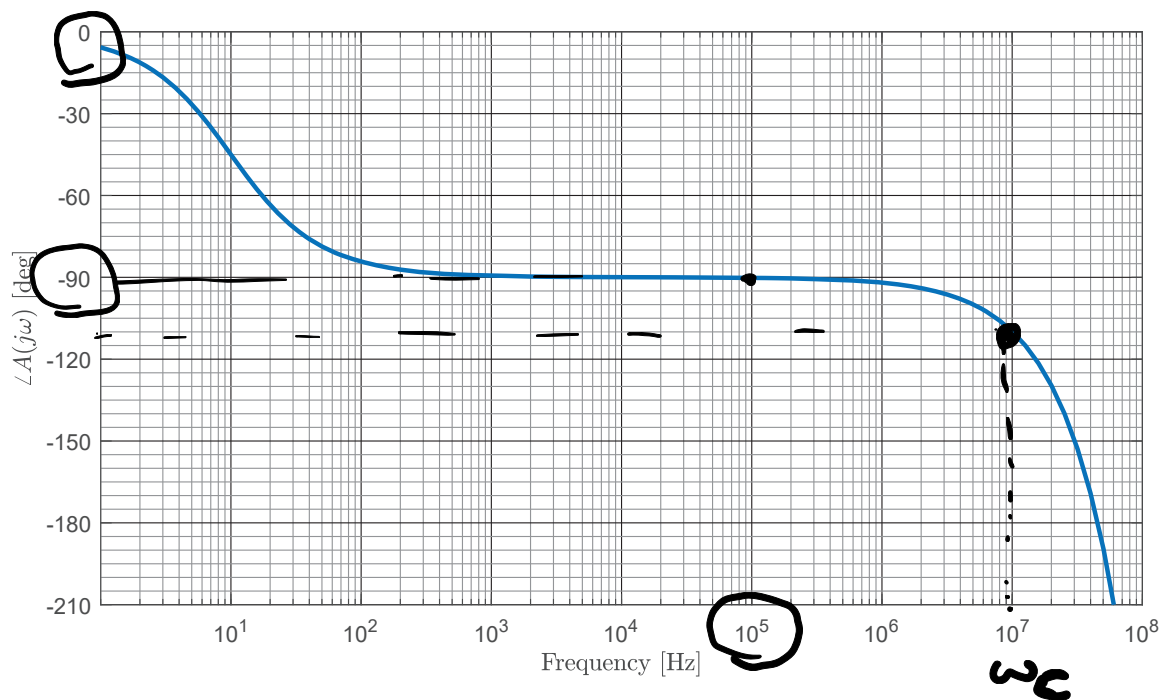
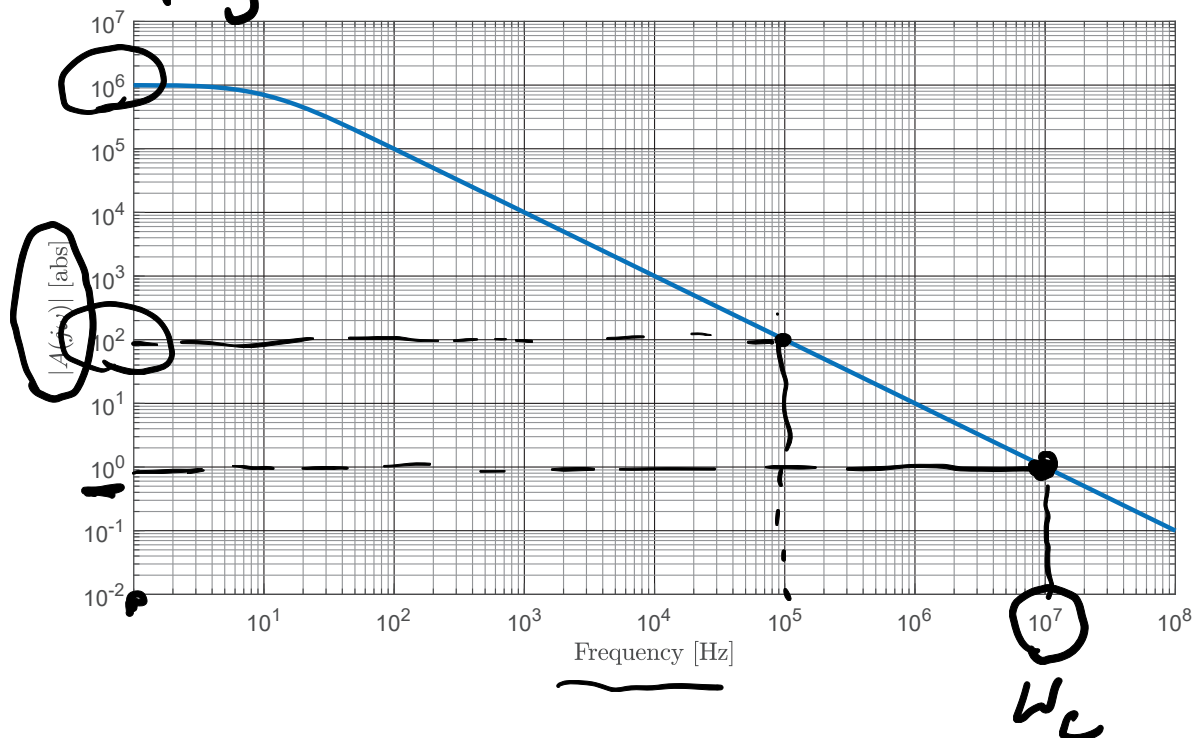


Figure 3: Bode plot of  $A(s)$ .