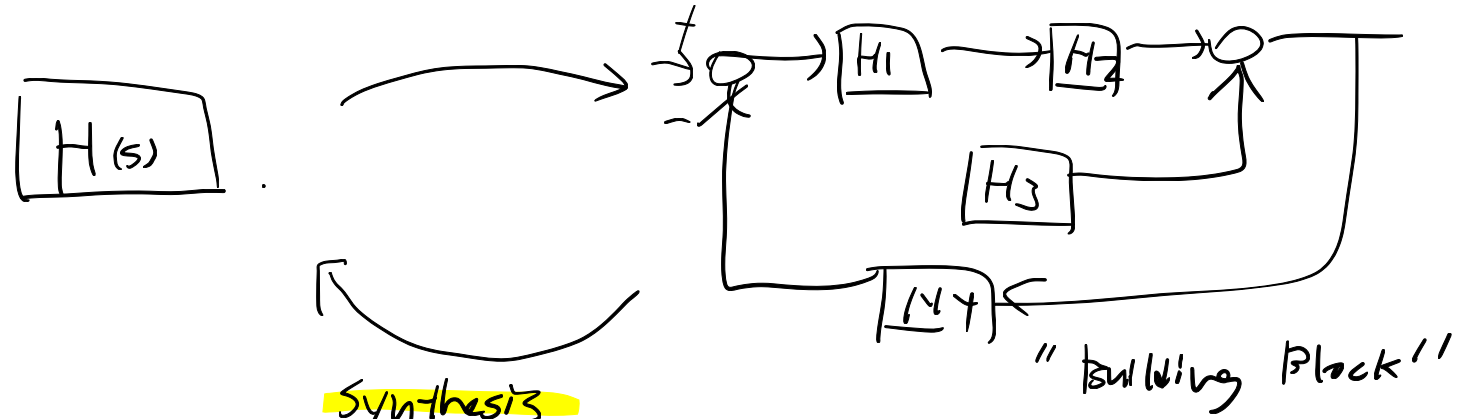


L4 – Operational Amplifier

Control = "Design" of the system dynamics.

Analysis { Decompose: "+"
Factorization: "x"






Synthesis
(design)

time { Imp
step. sinusoid.




Freq. { pole
zero.
 $H(s)$

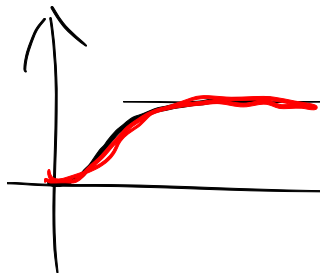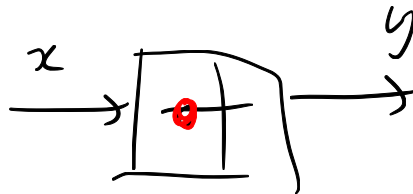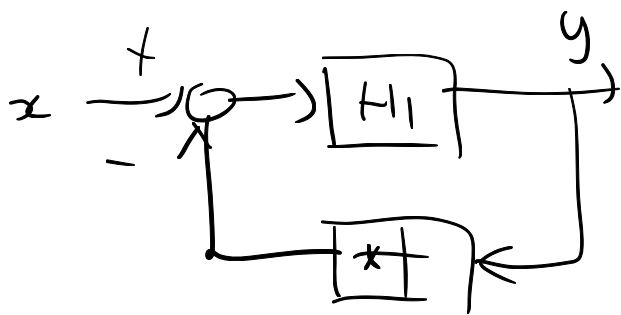

$$G_1 = \frac{1}{s^2 + 20s + 100}$$

$$= \frac{1}{(s+10)^2}$$




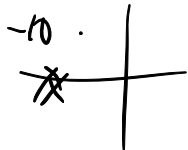


$$G_2 = \frac{1+s}{s^2 + 20s + 100}$$

AMP & ZV


$$G_3 = \frac{1-s}{s^2 + 20s + 100}$$
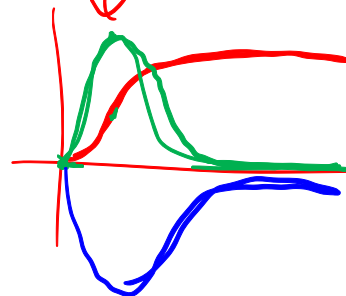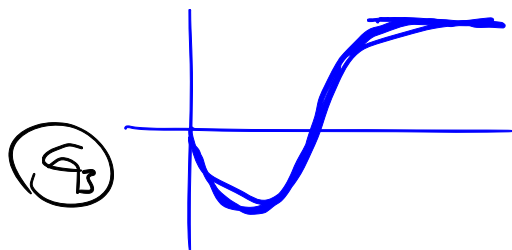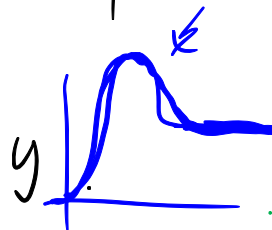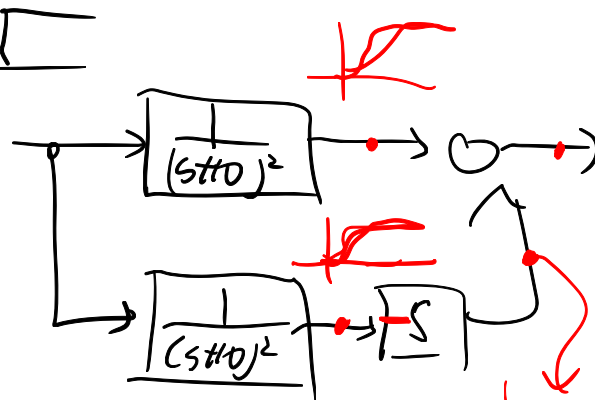
$$G_2 = \frac{1}{(s+10)^2} + \frac{s}{(s+10)^2}$$



Input. $\{$

"Object"

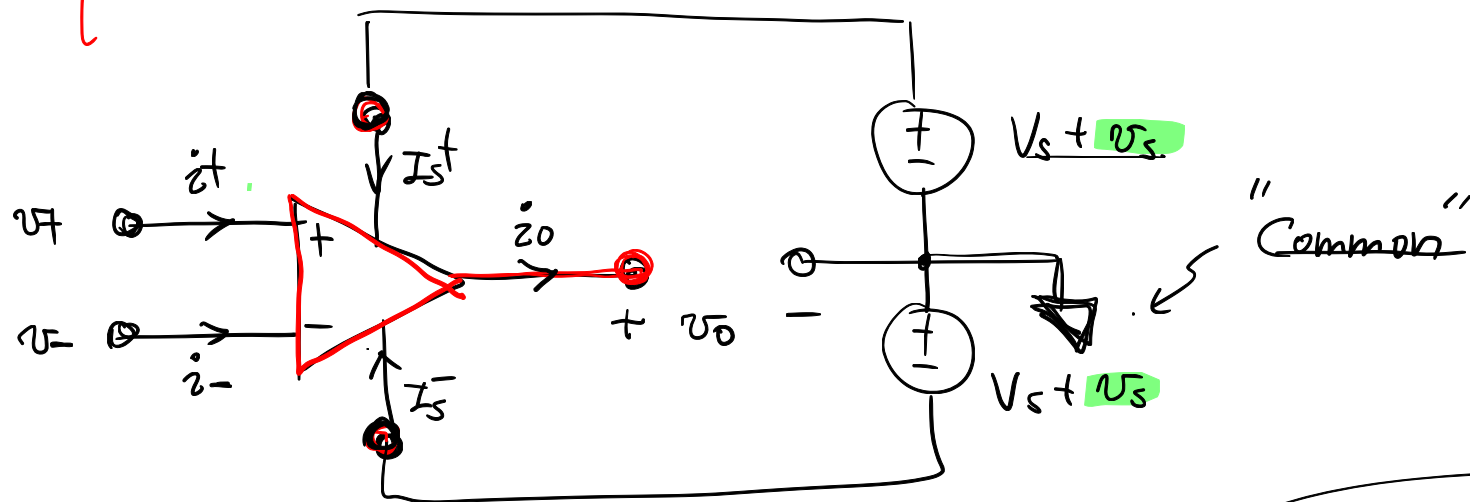

trans. cap. res. . . .

Terminal Variables

Terminal Relations

- 5 terminals
- 3 ports.

Current : $\underline{i_o} = \underline{I_s^+} + \underline{I_s^-} + \underline{i_+} + \underline{i_-}$ (KCL)

Voltage : $v_o = A(\underbrace{v_+ - v_-}_{v_d}) + A_c \left(\underbrace{\frac{v_+ + v_-}{2}}_{v_{cm}} \right) + A_s \overset{\downarrow}{v_s} - Z_o i_o$



$\left\{ \begin{array}{l} A: \text{open-loop (voltage) gain.} \\ A_c: \text{Common-mode gain.} \\ A_s: \end{array} \right.$

$$\underline{\underline{CMRR}} \triangleq \frac{A}{A_c}$$

$$\Rightarrow \underline{\underline{PSRR}} \triangleq \frac{A}{A_s}$$



$\left\{ \begin{array}{l} \text{Input } Z: Z_i \\ \text{Output } Z: Z_o \end{array} \right.$

① Circuit Model.

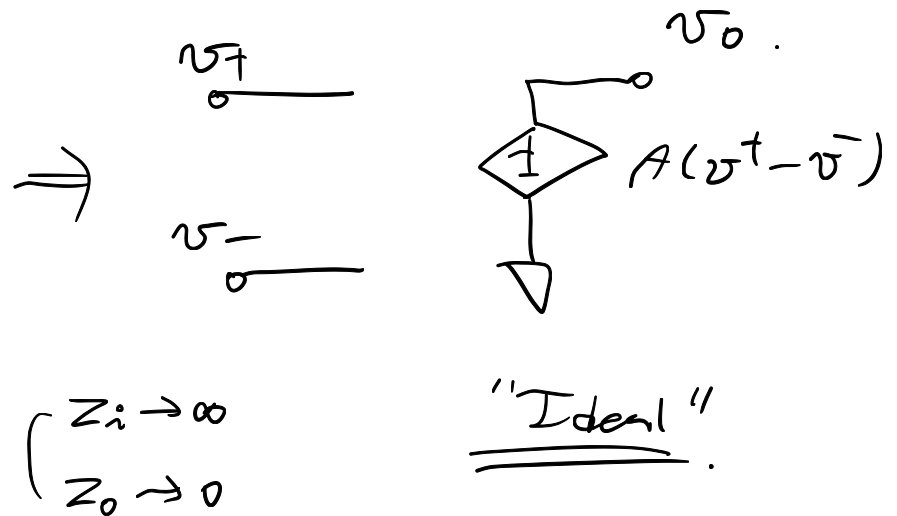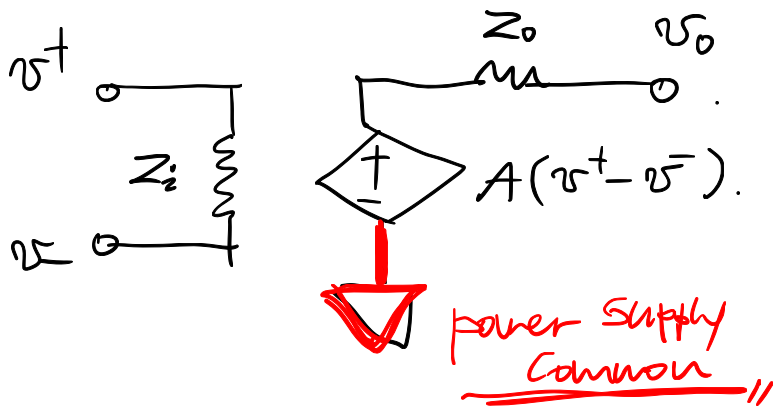

$$\left\{ \begin{array}{l} Z_i \rightarrow \infty \\ Z_o \rightarrow 0 \end{array} \right.$$

② Block diagram

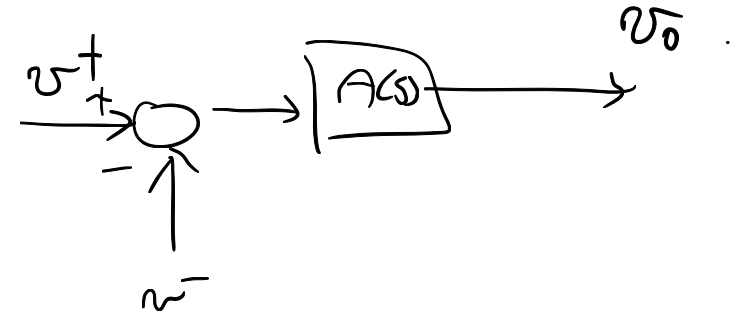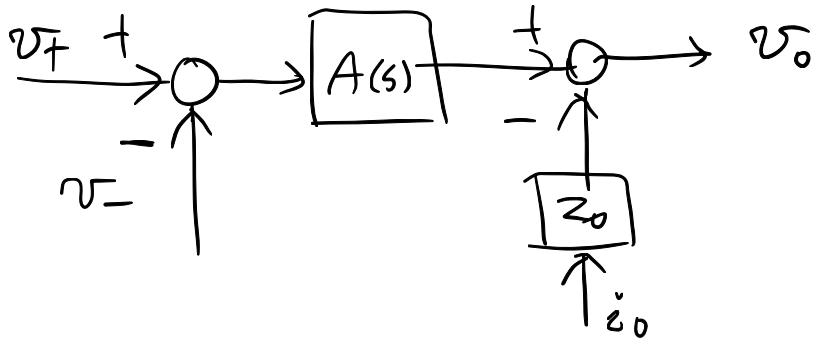


- Σ
- (1) $A = \text{const}$
 - (2) $A \rightarrow \infty$
 - (3) $A(s) = \frac{\omega_0}{s}$
 - (4) $A(j\omega)$ in datasheet.




$$A [V/V] = [-]$$

< Non-inverting Amp >

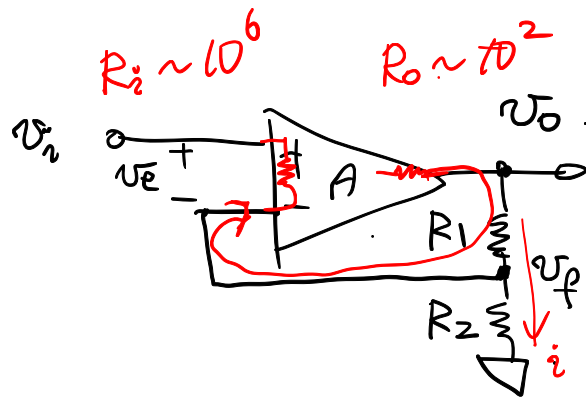

10^4 10kΩ

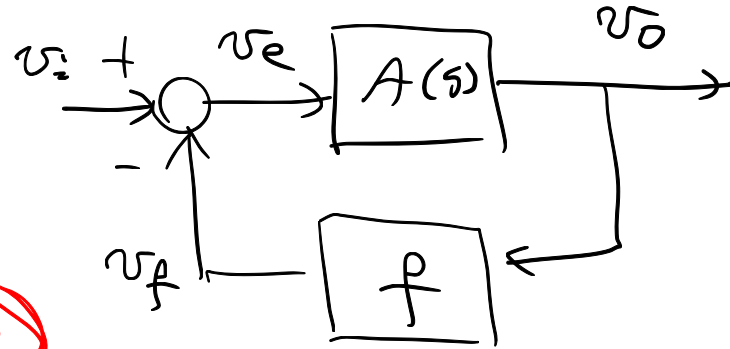

Q. "A" } hard to make it precise.
easy to make it "Large"

$\times 1000$

Q. A → How make precise amp? → "Feed back"

$$f = \frac{v_f}{v_o}$$

$$v_f = \frac{R_2}{R_1 + R_2} \cdot v_o$$

$$f = \frac{R_2}{R_1 + R_2}$$

Black's Formula

$v_i \rightarrow v_o$

$$\frac{A(s)}{1 + \underline{L(s)}} =$$

$$\frac{A(s)}{1 + \underline{A(s) \cdot f}}$$

$$\frac{1/2}{1/2 + 9/2} = \frac{1}{10}$$

$$\frac{1k\Omega}{1k\Omega + 9k\Omega} \approx \frac{1}{10}$$

$$G = \frac{A}{1+A\beta}$$

$$\begin{array}{l} 1k\Omega = R_1 \\ 9k\Omega = R_2 \end{array} \Rightarrow \beta = \frac{1}{10}$$

$$\text{As } A\beta \rightarrow \infty \quad G \approx \frac{A}{\cancel{1+A\beta}} = \frac{A}{A\beta} = \frac{1}{\beta} \quad R (0.005\%)$$

