

## Homework 3

Assigned: Feb 5, 2021

Due: Feb 12, 2021

### Problem 1

Let us consider an op-amp circuit in Figure 1. We assume that the op-amp input impedance is infinite, the output impedance is  $R_o$ , and the open-loop gain is  $A(s)$ . Note that the output impedance  $R_o$  is pulled out of the op-amp.

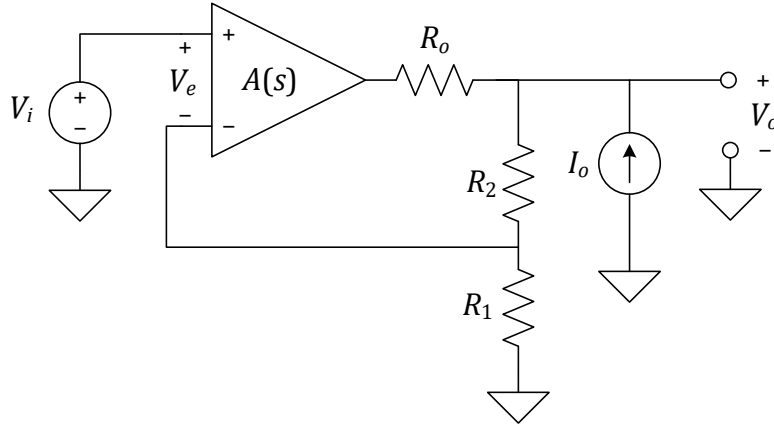


Figure 1: Schematic of a non-inverting amplifier.

- Draw a block diagram that shows the relation between the input voltage  $V_i$ , disturbance current  $I_o$ , and the output voltage  $V_o$ . The block diagram should show a feedback loop around  $A(s)$ .
- Find the expression for the loop transfer function  $L(s)$ . Also, find the expression for the output impedance  $Z_o(s) = V_o/I_o$  in terms of  $L(s)$ ,  $R_o$ ,  $R_1$ , and  $R_2$ .
- Assuming the op-amp high-frequency open-loop gain is zero, i.e.,  $A(j\omega)|_{\omega \rightarrow \infty} = 0$ , find the expression for the high-frequency output impedance  $Z_o(j\omega)|_{\omega \rightarrow \infty}$  in terms of  $R_o$ ,  $R_1$ , and  $R_2$ . Also, find the expression for the output impedance normalized to the high-frequency value, i.e.,

$$\hat{Z}(s) \equiv \frac{Z_o(s)}{Z_o(j\omega)|_{\omega \rightarrow \infty}}$$

in terms of  $L(s)$ .

(d) Using MATLAB, draw the Bode plots of  $L(s)$  and  $\hat{Z}(s)$  for

$$R_o = 50 \Omega \quad R_1 = 1 \text{ k}\Omega \quad R_2 = 1 \text{ k}\Omega \quad A(s) = \frac{10^4}{(s+1)(0.001s+1)}$$

on the same graph. Find the gain crossover frequency  $\omega_c$  and phase margin  $\phi_m$  of  $L(s)$ , and also find the cutoff frequency  $\omega_l$  where  $|\hat{Z}(j\omega_l)| = 0.7071 (-3 \text{ dB})$ . Discuss how the shapes of  $|L(j\omega)|$  and  $|\hat{Z}(j\omega)|$  are related at frequencies below  $\omega_c$ .

(e) Find the output dc impedance  $Z_o(j\omega)|_{\omega=0}$

## Problem 2

Let us consider a brushed dc motor driven by a voltage amplifier shown in Figure 2. Here,  $L_m$  is the winding inductance,  $R_m$  is the winding resistance,  $J_m$  is the rotor rotational inertia, and  $K_t$  is the motor torque constant. There is a wheel mounted on the motor shaft, whose rotational inertia is  $J_w$ . On the current return path, there is a shunt resistor  $R_s$  to measure the current through the motor winding.

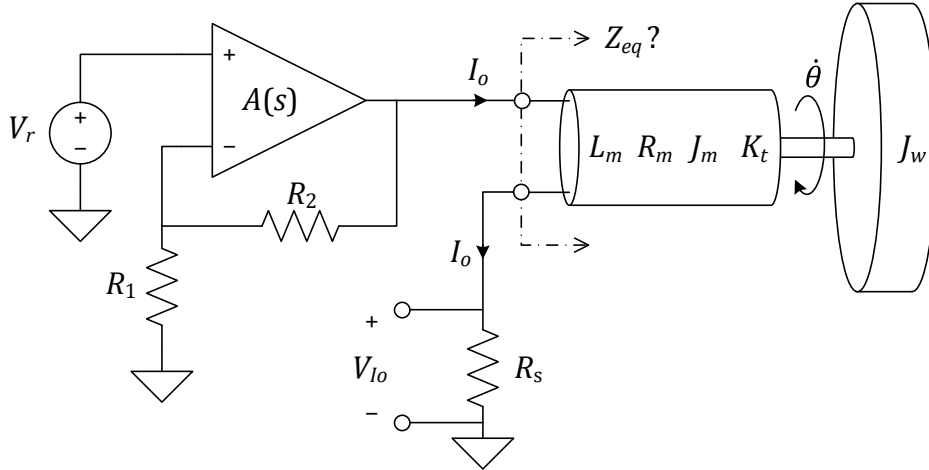


Figure 2: Brushed dc motor driven by an op-amp circuit.

- Find the electrical impedance  $Z_{eq}(s)$  looking into the electrical port of the motor.
- Draw an equivalent circuit diagram where all mechanical elements are referred to the electrical domain as passive electrical elements. Find the parameter(s) of the equivalent circuit element(s) in terms of  $L_m$ ,  $R_m$ ,  $J_m$ ,  $K_t$ , and  $J_w$ .

- (c) Find the analytic expression for the transconductance from  $V_r(s)$  to  $I_o(s)$ . Then, draw the Bode plot of  $I_o(s)/V_r(s)$  using MATLAB for

$$\begin{array}{lll}
 A(s) = \frac{10^7}{s} & R_1 = 1 \text{ k}\Omega & R_2 = 9 \text{ k}\Omega \\
 R_m = 4.8 \Omega & L_m = 1 \text{ mH} & R_s = 0.2 \Omega \\
 K_t = 250 \text{ mNm/A} & J_m = 1 \text{ kg} \cdot \text{cm}^2 & J_w = 9 \text{ kg} \cdot \text{cm}^2
 \end{array}$$

- (d) Let us assume that the shunt resistor  $R_s$  is rated for 1 W power. That is, the resistor fails when it dissipates more than 1 W. What is the maximum rms current  $I_{o,\text{rms}}$  allowed for the shunt resistor?
- (e) Let the input voltage  $V_r$  be sinusoidal at 50 Hz. What is the maximum rms voltage  $V_{r,\text{rms}}$  that the shunt resistor can accommodate for its power rating?