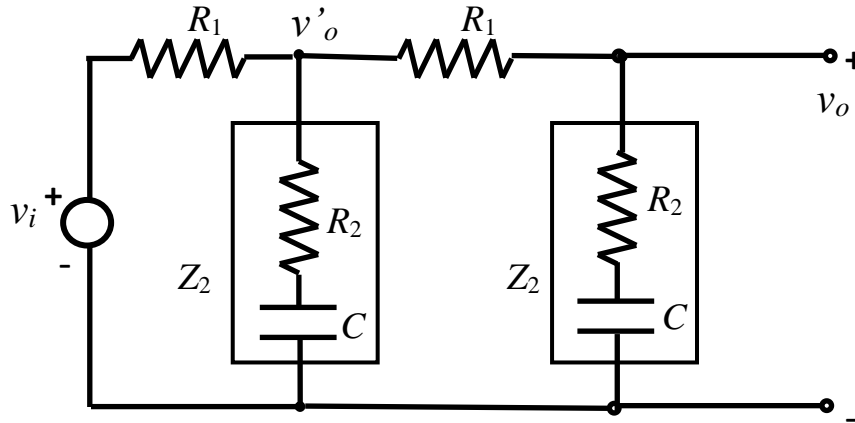


**Example 3.1**


Consider the cascaded lag network shown in Figure 3.1. Determine the input impedance and the output impedance of the circuit.



**Figure 3.1: Cascaded lag network.**

**Solution**

An equivalent circuit of the given cascaded circuit is shown in Figure S3.1(a).

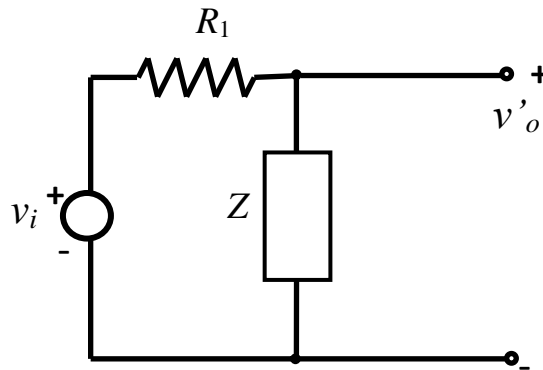

**Figure S3.1(a): An equivalent circuit of the cascaded circuit.**

**Input Impedance:**

Since  $Z$  is formed by connecting  $Z_2$  and  $(R_1 + Z_2)$  in parallel (see Figure 3.1), we have

$$\frac{1}{Z} = \frac{1}{Z_2} + \frac{1}{R_1 + Z_2} \quad (i)$$

The input current from the source is

$$i = \frac{v_i}{R_1 + Z}$$

Hence, the input impedance is

$$Z_i = \frac{v_i}{i} = R_1 + Z$$

where,  $Z$  is given by (ii).

### Output Impedance:

Voltage drop across  $Z$  is (from Figure S3.1(a))

$$v_o' = \frac{Z}{R_1 + Z} v_i \quad (\text{ii})$$


The output, open-circuit voltage is (see Figure 3.1)

$$v_o = \frac{Z_2}{R_1 + Z_2} v_o'$$

Substitute (ii) into this equation. We get

$$v_o = \frac{Z_2}{(R_1 + Z_2)} \frac{Z}{(R_1 + Z)} v_i \quad (\text{iii})$$

To get the short-circuit current, short the output of Figure 3.1. We get the circuit in Figure S3.1(b).

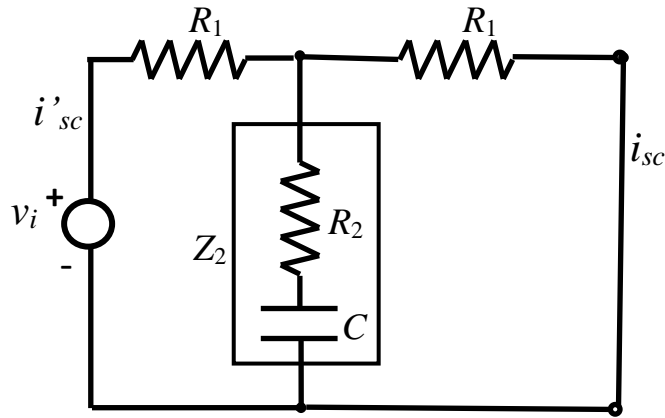

**Figure S3.1(b): Circuit with output short-circuited.**

The equivalent impedance of the second stage (consisting of  $Z_2$  and  $R_1$  in parallel) of this circuit  $Z'$  is given by

$$\frac{1}{Z'} = \frac{1}{Z_2} + \frac{1}{R_1} \text{ or } Z' = \frac{R_1 Z_2}{R_1 + Z_2} \quad (\text{iv})$$

Hence, the current at the source under short-circuit conditions is

$$i_{sc}' = \frac{v_i}{R_1 + Z'} \quad (\text{v})$$

Since the current is divided proportional to inverse of impedance among parallel branches, the short-circuit current (at the output) is (see Figure S3.1(b))

$$i_{sc} = \frac{Z_2}{R_1 + Z_2} i_{sc}' = \frac{Z_2}{R_1 + Z_2} \frac{v_i}{R_1 + Z'} \quad (\text{vi})$$

The output impedance (by definition) is (from (iii) and (vi))

$$Z_o = \frac{v_o}{i_{sc}} = \frac{\frac{Z_2}{(R_1 + Z_2)} \frac{Z}{(R_1 + Z)} v_i}{\frac{Z_2}{(R_1 + Z_2)} \frac{v_i}{(R_1 + Z)}} = \frac{Z(R_1 + Z')}{R_1 + Z} = \frac{(R_1 + Z')}{R_1 / Z + 1}$$

Substitute (i) and (iv):

$$Z_o = \frac{\left( R_1 + \frac{R_1 Z_2}{R_1 + Z_2} \right)}{\left( \frac{R_1}{Z_2} + \frac{R_1}{R_1 + Z_2} + 1 \right)} = \frac{R_1 Z_2 (R_1 + Z_2 + Z_2)}{R_1 (R_1 + Z_2) + R_1 Z_2 + Z_2 (R_1 + Z_2)}$$

Or,

$$Z_o = \frac{R_1 Z_2 (R_1 + 2Z_2)}{R_1^2 + 3R_1 Z_2 + Z_2^2} = \frac{(R_1 + 2Z_2)}{R_1 / Z_2 + 3 + Z_2 / R_1}$$

Think of ways to make this small (to reduce loading).