

Solutions to Assignment 2

Sol-Problem 1 (Problem 2.4 from Textbook)

In open circuit, the voltage at the output port is given simply by the voltage-divider equation (in the frequency domain):

$$v_{oc} = \frac{\left[R_2 + \frac{1}{j\omega C} \right]}{\left[R_1 + R_2 + j\omega L + \frac{1}{j\omega C} \right]} v = v_{eq} \quad (i)$$

Note: Equivalent source v_{eq} is expressed here as a function of frequency. Its corresponding time function $v_{eq}(t)$ is obtained by using inverse Fourier transform. Alternatively, first replace $j\omega$ by

the Laplace variable s : $v_{eq}(s) = \frac{\left[R_2 + \frac{1}{sC} \right]}{\left[R_1 + R_2 + sL + \frac{1}{sC} \right]} v(s)$. Then obtain the inverse Laplace

transform, for a given $v(s)$, using Laplace transform tables.

Now, in order to determine Z_{eq} , note from Figure P2.4(c) that when the voltage source is shorted, the resulting circuit has the two branches of impedance $(R_1 + j\omega L)$ and $\left[R_2 + \frac{1}{j\omega C} \right]$ in parallel. Their equivalent impedance is given by: $\frac{1}{Z_{eq}} = \frac{1}{(R_1 + j\omega L)} + \frac{1}{\left[R_2 + \frac{1}{j\omega C} \right]}$

Or,

$$Z_{eq} = \frac{\left[R_2 + \frac{1}{j\omega C} \right] [R_1 + j\omega L]}{\left[R_1 + R_2 + j\omega L + \frac{1}{j\omega C} \right]}$$

Sol-Problem 2 (Problem 2.7 from Textbook)

(a) The input impedance of the amplifier = 500 MΩ.

$$\text{Estimated error} = \frac{10}{(500+10)} \times 100\% = 2\%$$

(b) Impedance of the speaker = 4 Ω .

$$\text{Estimated error} = \frac{0.1}{(4 + 0.1)} \times 100\% = 2.4\%$$

Sol-Problem 3 (Problem 2.10 from Textbook)

For the given system, $\omega_n = \sqrt{\frac{1 \times 10^6}{100}}$ rad/s = 100 rad/s and $\omega \geq 200$ rad/s. Hence, we have the frequency ratio $r \geq 2.0$.

For $r = 2.0$ and $|T_f| = 0.5$ we have $0.5 = \sqrt{\frac{1 + 16\zeta^2}{9 + 16\zeta^2}}$ or, $\zeta = \sqrt{\frac{5}{48}}$. Hence,

$$b = 2\zeta\omega_n m = 2\sqrt{\frac{5}{48}} \times 100 \times 100 \text{ N.s/m} \rightarrow b = 6.455 \times 10^3 \text{ N.s/m}.$$

With this damping constant, for $r \geq 2$, we will have $|T_f| \leq 0.5$. Decreasing b will decrease $|T_f|$ in this frequency range.

To plot the Bode diagram using MATLAB, first note that:

$$2\zeta\omega_n = b / m = 6.455 \times 10^3 / 100 = 64.55 \text{ rad/s and } \omega_n^2 = 10^4 \text{ (rad/s)}^2$$

The corresponding transmissibility function is $T_f = \frac{64.55s + 10^4}{s^2 + 64.55s + 10^4}$ with $s = j\omega$

The following MATLAB script will plot the required Bode diagram:

```
% Plotting of transmissibility function
clear;
m=100.0;
k=1.0e6;
b=6.455e3;
sys=tf([b/m k/m],[1 b/m k/m]);
bode(sys);
```

The resulting Bode diagram is shown in Figure S2.10. A transmissibility magnitude of 0.5 corresponds to $20\log_{10} 0.5 \text{ dB} = -6.02 \text{ dB}$.

Note from the Bode magnitude curve in Figure S2.10.4 that at the frequency 200 rad/s the transmissibility magnitude is less than -6 dB and it decreases continuously for higher frequencies. This confirms that the designed system meets the design specification.

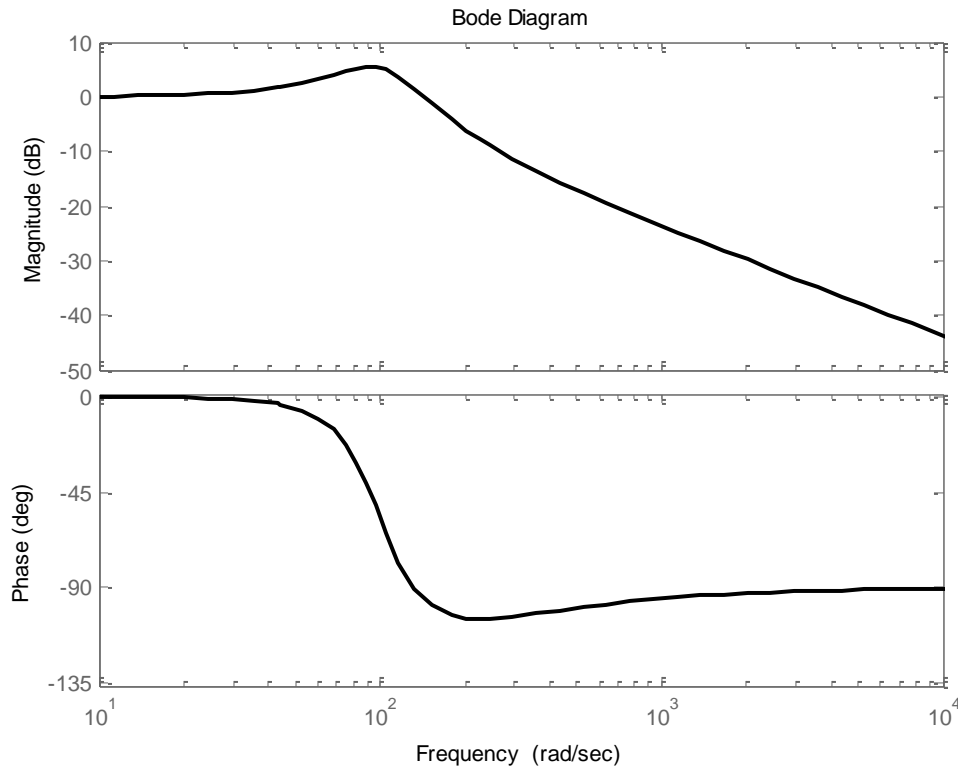


Figure S2.10: Transmissibility magnitude and phase curves of the designed system.

Sol-Problem 4 (Problem 2.17 from Textbook)

Slew rate: $s = 2\pi f_b a$ (i)

where, a = output amplitude, f_b = bandwidth (Hz).

The rise time T_r is inversely proportional to f_b . Hence, $f_b = \frac{k}{T_r}$ where, k = constant.

Substitution gives: $s = \frac{2\pi k a}{T_r}$ (ii)

From (i): For constant s , bandwidth decreases as a is increased.

For a sine signal, substitute the given values in (i): $f_b = \frac{0.5}{2\pi \times 2.5} \text{ MHz} = 31.8 \text{ kHz}$

Next, for a step input, use $s = \frac{\Delta y}{\Delta t}$

where, Δy = final output value, Δt = time to reach the final output value

Substitute numerical values: $\Delta t = \frac{\Delta y}{s} = \frac{5.0}{0.5} \mu\text{s} = 10 \mu\text{s}$.

Sol-Problem 5 (Problem 2.25 from Textbook)

(a)

Op-amp properties: 1. Voltages at input leads are equal; 2. Currents through input leads = 0

Op-amp property:

$$v_B = v_P = v_o \quad (i)$$

$$\text{Current Balance at Node A: } \frac{(v_i - v_A)}{Z_c} = \frac{(v_A - v_B)}{Z_c} + \frac{(v_A - v_P)}{R} \quad (ii)$$

$$\text{Current Balance at Node B: } \frac{(v_A - v_B)}{Z_c} = \frac{v_B}{R} \quad (iii)$$

Note: $Z_c = \frac{1}{Cs}$ = impedance of capacitor

$$\text{Substitute (i) and (iii) in (ii): } \frac{(v_i - v_A)}{Z_c} = \frac{v_o}{R} + \frac{(v_A - v_o)}{R} = \frac{v_A}{R} \rightarrow v_i = (1 + \frac{1}{\tau s})v_A \quad (iv)$$

$$\text{Substitute (i) in (iii): } \frac{(v_A - v_o)}{Z_c} = \frac{v_o}{R} \rightarrow v_A = (1 + \frac{1}{\tau s})v_o \quad (v)$$

Note: $\tau = RC$ = time constant

$$\text{Substitute (iv) in (v): } G(s) = \frac{v_o}{v_i} = \frac{(\tau s)^2}{(\tau s + 1)^2}$$

This is a 2nd order transfer function \rightarrow 2-pole filter

(b)

$$\text{With } s = j\omega \text{ in } G(s), \text{ we have } G(j\omega) = \frac{-\tau^2 \omega^2}{(1 + \tau j\omega)^2}$$

$$\text{Filter magnitude } |G(j\omega)| = \frac{\tau^2 \omega^2}{(1 + \tau^2 \omega^2)}$$

The magnitude of the filter transfer function is sketched in Figure S2.25. This represents a high-pass filter.

(c)

$$\text{When, } \omega \ll \frac{1}{\tau}: |G(j\omega)| \cong \tau^2 \omega^2$$

$$\text{When, } \omega \gg \frac{1}{\tau}: |G(j\omega)| \cong \frac{\tau^2 \omega^2}{\tau^2 \omega^2} = 1$$

Hence, we may use $\omega_c = \frac{1}{\tau}$ as the cutoff frequency.

Note: $|G(j\omega)| \rightarrow 1$ as $\omega \rightarrow \infty$

For small ω : Roll-up slope of $|G(j\omega)|$ curve is $= 20\log_{10}(\omega^2) = 40 \text{ dB/decade}$

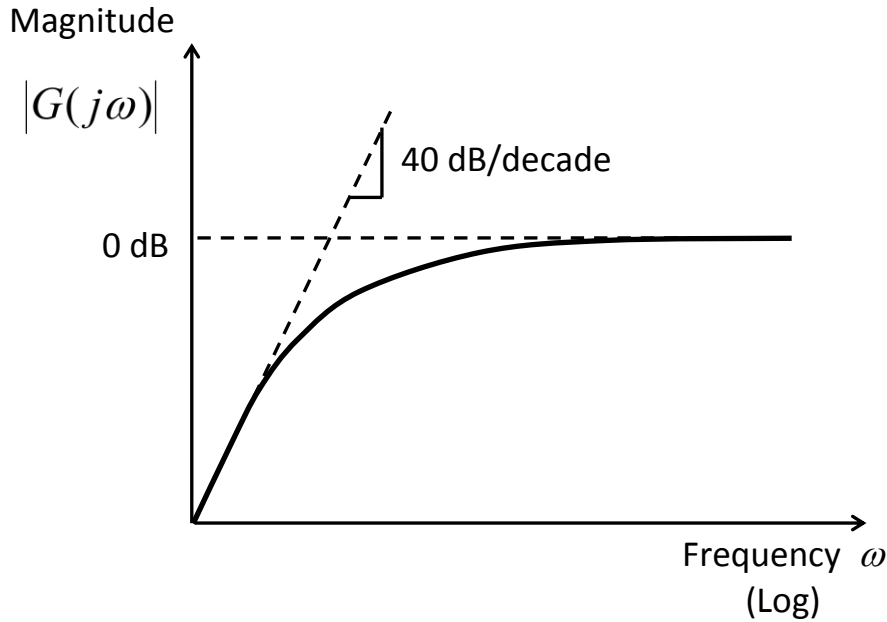


Figure S2.25: Filter transfer function magnitude.

Sol-Problem 6 (Problem 2.40 from Textbook)

From equation (2.80) we get $\delta v_o = \frac{[(R + \delta R)R - R(R - \delta R)]}{(R + \delta R + R)(R - \delta R + R)} v_{ref} - 0$

This simplifies to $\frac{\delta v_o}{v_{ref}} = \frac{2\delta R / R}{4 - (\delta R / R)^2}$ which is nonlinear.

Similarly, it can be shown from equation (2.80) that the pair of changes: $R_2 \rightarrow R + \delta R$ and $R_4 \rightarrow R - \delta R$ will result in a nonlinear relation that is the same as before, except for the change in sign:

$$\frac{\delta v_o}{v_{ref}} = \frac{-2\delta R / R}{4 - (\delta R / R)^2}$$

Sol-Problem 7 (Problem 2.41 from Textbook)

From equation (2.87) we get $\delta v_o = \frac{[(R + \delta R)R - (R - \delta R)R]}{(R + \delta R + R - \delta R + R + R)} i_{ref} - 0$

On simplification we get the linear relation: $\frac{\delta v_o}{R i_{ref}} = \frac{\delta R / R}{2}$

If R_4 and R_3 are the active elements, with R_4 in tension and R_3 in compression, it is clear from equation (2.87) that we get an identical linear result (not even a sign change).

Sol-Problem 8 (Problem 2.48 from Textbook)

From the bridge circuit we have: $v_o = \left[\frac{R_1}{(R_1 + R_2)} - \frac{R_3}{(R_3 + R_4)} \right] v_{ref}$ (neglect load current)

If R_1 is changed to $R_1 + \delta R_1$ we have

$$\begin{aligned}\delta v_o &= \left[\frac{R_1 + \delta R_1}{(R_1 + \delta R_1 + R_2)} - \frac{R_3}{(R_3 + R_4)} - \frac{R_1}{(R_1 + R_2)} + \frac{R_3}{(R_3 + R_4)} \right] v_{ref} \\ &= \left[\frac{R_1 + \delta R_1}{(R_1 + R_2 + \delta R_1)} - \frac{R_1}{(R_1 + R_2)} \right] v_{ref} = \left[\frac{R + \delta R}{2R + \delta R} - \frac{1}{2} \right] v_{ref} \quad \{R_1 = R_2 = R\}\end{aligned}$$

$$\text{Hence, } \delta v_o = \frac{\delta R}{2(2R + \delta R)} v_{ref}$$

We can write this in Taylor series expansion as:

$$\delta v_o = \frac{\delta R}{4R \left(1 + \frac{\delta R}{2R}\right)} v_{ref} = \frac{\delta R}{4R} v_{ref} \left(1 + \frac{\delta R}{2R}\right)^{-1} = \frac{\delta R}{4R} v_{ref} \left(1 - \frac{\delta R}{2R} + O(2)\right)$$

If we neglect $O(2)$ terms, which are small compared to $\frac{\delta R}{2R}$, we have: $\delta v'_o = \frac{\delta R}{4R} v_{ref}$

$$\begin{aligned}\rightarrow \quad \% \text{ error} &= \frac{(\delta v'_o - \delta v_o)}{\delta v_o} \times 100 = \frac{\left[\frac{\delta R}{4R} - \frac{\delta R}{2(2R + \delta R)} \right]}{\frac{\delta R}{2(2R + \delta R)}} \times 100 \\ &= \left[\frac{4R + 2\delta R}{4R} - 1 \right] \times 100 = \frac{\delta R}{2R} \times 100\end{aligned}$$

$$\text{For } \frac{\delta R}{R} = 0.05: \% \text{ error} = \frac{0.05}{2} \times 100\% = 2.5\%$$