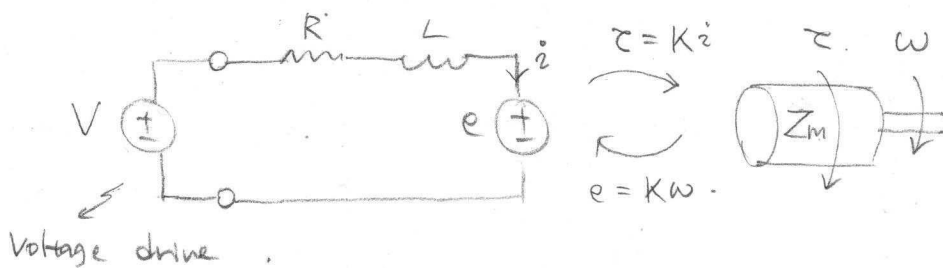


< Voltage-controlled Brushed DC Motor >

Objective


- Understand the dynamics of voltage-controlled dc motors.
- Open-loop speed & torque response.

① Lumped-parameter Model.




	Through	Across
Flow	i	v, w
Effort	f, τ	V

② Block Diagram

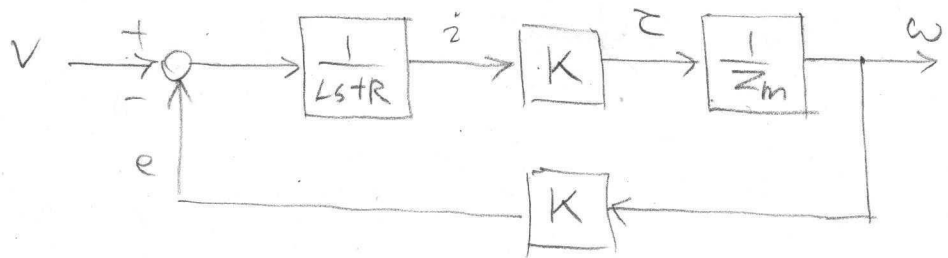

③ Equivalent Mechanical Model

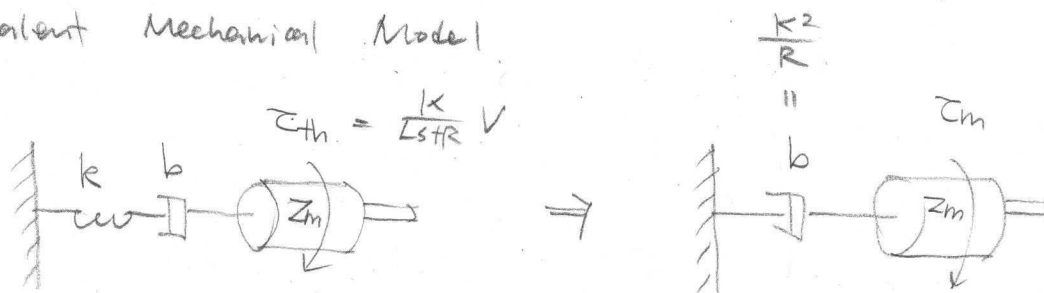

Let's study the dynamics of voltage-controlled dc motors.

$$L(s) = \frac{K^2}{Z_m Z_e} \Rightarrow \begin{cases} \frac{w}{V} = \frac{\frac{K}{Z_m Z_e}}{1 + \frac{K^2}{Z_m Z_e}} & \text{speed resp.} \\ \frac{\tau}{V} = \frac{\frac{K}{Z_e}}{1 + \frac{K^2}{Z_m Z_e}} & \text{torque resp.} \end{cases}$$

Speed Response

$$G_w \triangleq \frac{\omega}{V} = \frac{\frac{K}{Z_m(Ls+R)}}{1 + \frac{K^2}{Z_m(Ls+R)}} = \frac{K}{Z_m(Ls+R) + K^2}$$



When $Z_m = Js$ (Free Inertia)

$$\frac{\omega}{V} = \frac{K}{Js(Ls+R) + K^2} = \frac{K}{JLs^2 + JRs + K^2}$$

$\omega_m \ll \omega_e$ in many practical cases.

$$\omega_e = \frac{R}{L} \quad \omega_m = \frac{K^2}{JR}$$

Bode Plot:

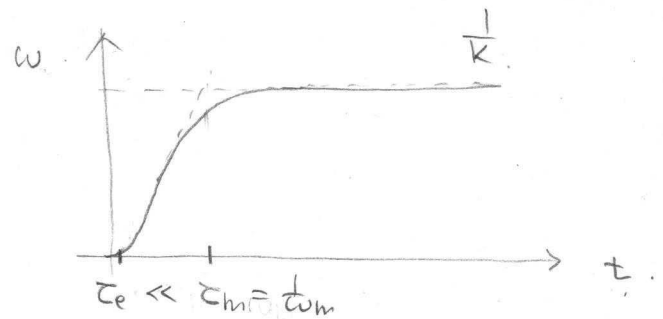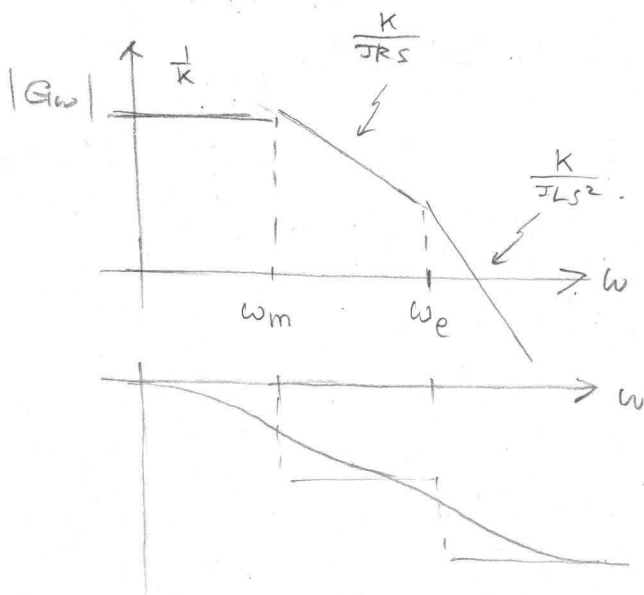


See the datasheet.

Example motor parameters

$$L = 1 \text{ mH}, \quad R = 6 \Omega, \quad K = 200 \text{ mNm/A}, \quad J = 2 \text{ kg} \cdot \text{cm}^2$$

$$\begin{cases} \omega_e \approx 1 \text{ kHz} & \tau_e = 1 \text{ ms} \\ \omega_m \approx 5 \text{ Hz} & \tau_m \approx 200 \text{ ms} \end{cases}$$

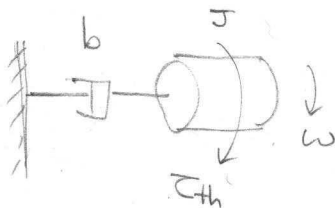
Note that the approx. mechanical model leads to ^{Almost} the same.



$$\begin{aligned} \omega &= \frac{1}{Js+b} \cdot \tau_{th} = \frac{1}{Js + \frac{K^2}{R}} \cdot \frac{K}{Ls+R} V \\ &= \frac{K}{JLs^2 + (JR + \frac{K^2}{R})s + K^2} V \\ &\approx \frac{K}{JLs^2 + JRs + K^2} V \end{aligned}$$


(If $\frac{K^2}{R} \ll JR \Leftrightarrow \omega_m \ll \omega_e$)

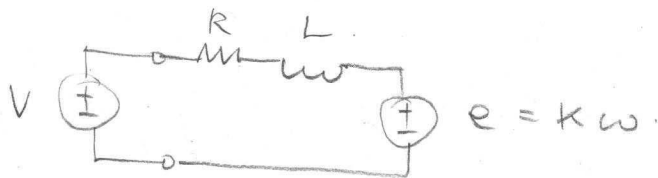- Here, the steady-state speed can be understood as the terminal velocity due to the apparent damping $b = \frac{K^2}{R}$.
- The step-response is dominated (or bottlenecked) by $\tau_m \ll \tau_e$.
- From the lumped-parameter model:



At the steady-state, $\omega = \text{const}$
 $\rightarrow \tau = 0 \rightarrow i = 0$
 \rightarrow Voltage drop across $Z_e = 0$
 $\rightarrow V = e = K\omega$
 $\therefore \underline{\underline{\omega = \frac{V}{K}}}$

- From the block diagram.

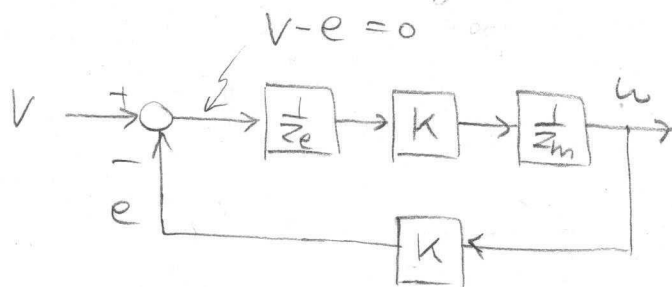

At the steady-state
the "error" signal is zero.
 $\Rightarrow V - e = 0 \rightarrow V = K \cdot \omega$

- Open-loop speed control with a "voltage drive" is common for simple tasks. (e.g. cooling fans).

• Torque Response:


For the analysis & control of mechanical systems (e.g., robots) we usually treat torques and forces as the driving variables.

High-bandwidth torque control is important in robotics.

(e.g. MIT Mini Cheetah - very light limbs)

Voltage-controlled dc motor has some issues here.
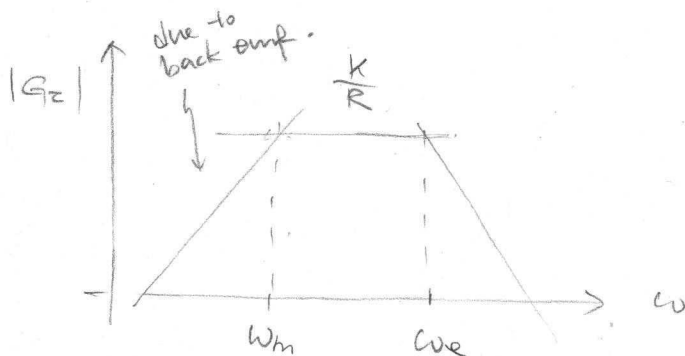
$$G_c \triangleq \frac{\tau}{V} = \frac{\frac{K}{Ls+R}}{1 + \frac{K^2}{(Ls+R)Js}} = \frac{K}{Ls + R + \frac{K^2}{Js}}$$



$$\omega_m = \frac{K^2}{JR} \quad \text{as } J \downarrow, \omega_m \uparrow \text{ even worse.}$$

Issues

① Slow response to V .

Even if we use high-bandwidth voltage amplifier, (e.g., 300 kHz), the torque response is bottlenecked by ω_c (e.g., 1 kHz).

② Back-emf effect.

Back-emf decreases the low-freq torques.

$\left\{ \begin{array}{l} \text{Mechanical view: apparent damping drags the rotor.} \\ \text{Electrical view: external low-freq disturbance voltage.} \end{array} \right.$

\Rightarrow Current-controlled dc motor can address these issues.