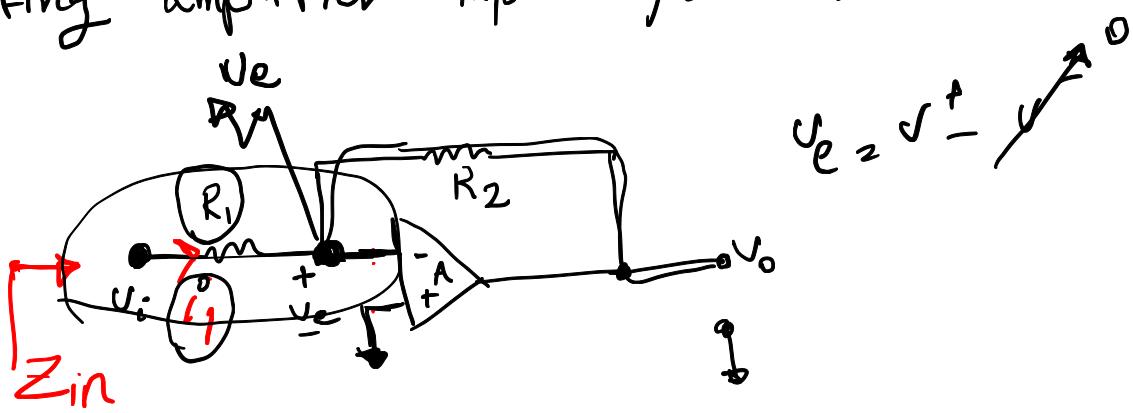


< inverting amplifier input impedance >



$$V_i \cdot = Z_{in} i_1$$

① $A \rightarrow \infty$ and $f = \frac{R_1}{R_1 + R_2} \neq 0 \Rightarrow A_f \rightarrow \infty$
 $L(s) \rightarrow \infty$

"virtual short"

$$V^+ = 0$$

$$V_e \approx 0 \quad i_1 = \frac{V_c - 0}{R_1}$$

$$\Rightarrow Z_{in} = R_1$$


② $A = A(s)$

$$\frac{V_i - V_e}{R_1} = i_1$$

$$V_i \cdot = Z_{in} i_1$$
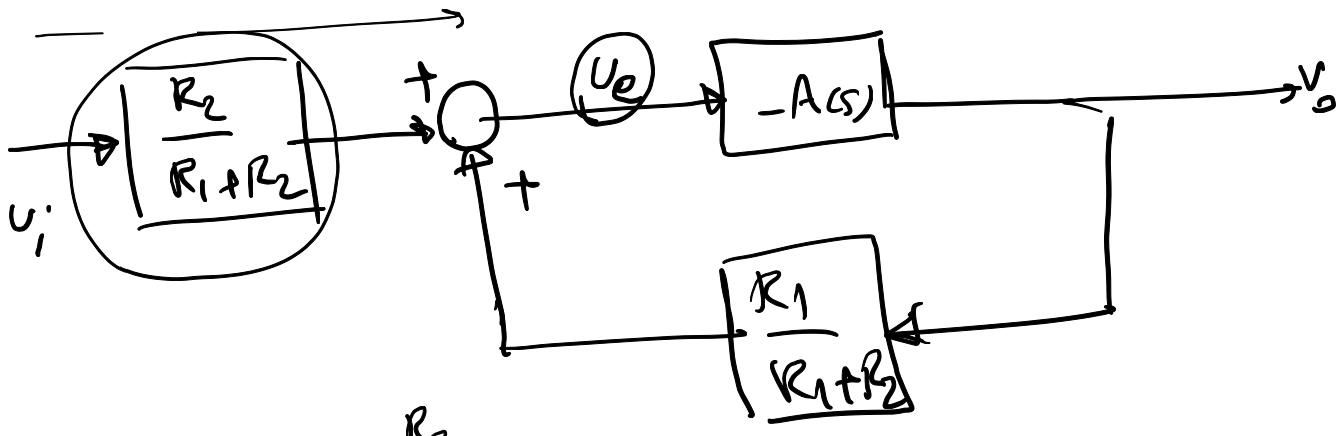
$$V_e = \frac{R_2}{R_1 + R_2} V_i + \frac{R_1}{R_1 + R_2} V_o$$





$$\frac{v_e}{v_i} = \frac{\frac{R_2}{R_1 + R_2}}{1 + L(s)}$$

Block's formula

$$\begin{aligned} i_1 &= \frac{1}{R_1} (v_i - v_e) \\ &= \frac{1}{R_1} \left(v_i - \frac{R_2 / (R_1 + R_2)}{1 + L(s)} v_i \right) \end{aligned}$$

$$i_1 = \frac{1}{R_1} \left(1 - \frac{\frac{R_2}{R_1 + R_2}}{1 + L(s)} \right) v_i$$

admittance $\gamma(s)$

$$\begin{cases} I = \gamma V \\ V = Z I \end{cases}$$

$$\gamma(s) = \frac{1}{Z(s)}$$

$$\gamma(s) = \frac{1}{R_1} \left(\frac{1 + L(s) - \frac{R_2}{R_1 + R_2}}{1 + L(s)} \right)$$

$$= \frac{1}{R_1} \left(\frac{\frac{R_1}{R_1 + R_2} + L(s)}{1 + L(s)} \right)$$

$$Y(s) = \frac{1}{R_1} \left(\frac{f + L(s)}{1 + L(s)} \right)$$

$$\hookrightarrow \frac{1}{Y(s)} = \boxed{Z(s) = R_1 \left(\frac{f + L(s)}{f + L(s)} \right)}$$

$L(s) = A(s)f$

$R_1, R_2, A(s)$

① $A \rightarrow \infty \rightsquigarrow L \rightarrow \infty \Rightarrow Z(s) = R_1$

② $A = A(s) \Rightarrow Z(s) = R_1 \left(\frac{1 + L(s)}{f + L(s)} \right)$

③ $b \rightarrow 0$ $Z(s) = R_1 \frac{1}{f} = \boxed{R_1 + R_2}$
 at high frequencies

$$\omega \gg \omega_0$$

$$A_f(s) = \frac{10^6}{s}, R_1 = 1k\Omega, R_2 = 9k\Omega$$


$|Z(s)| \uparrow$

$R_1 + R_2 = 10k\Omega$

$$f = \frac{1}{10}$$

$$L(s) = A(s) \times f = \frac{10^5}{s}$$
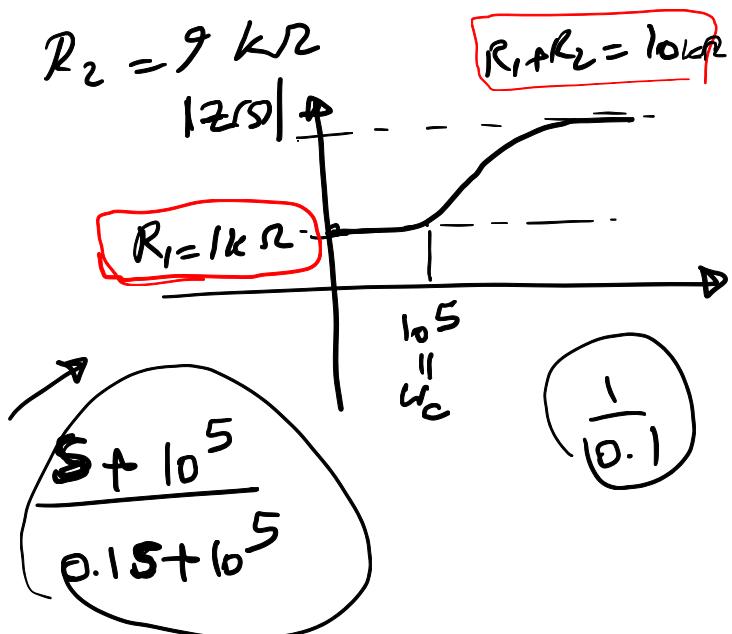
$$Z(s) = 1 \left(\frac{1 + \frac{10^5}{s}}{\frac{1}{10} + \frac{10^5}{s}} \right) =$$



< Non-inverting >

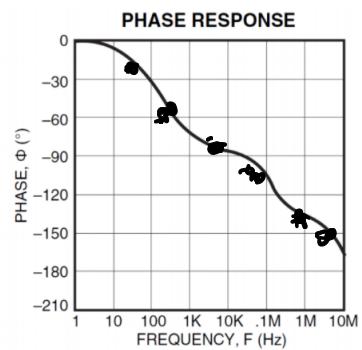
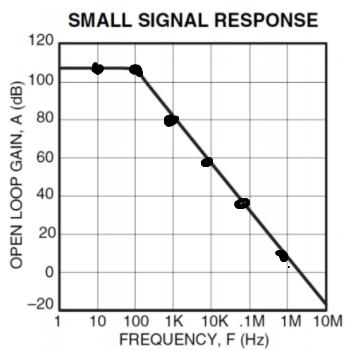
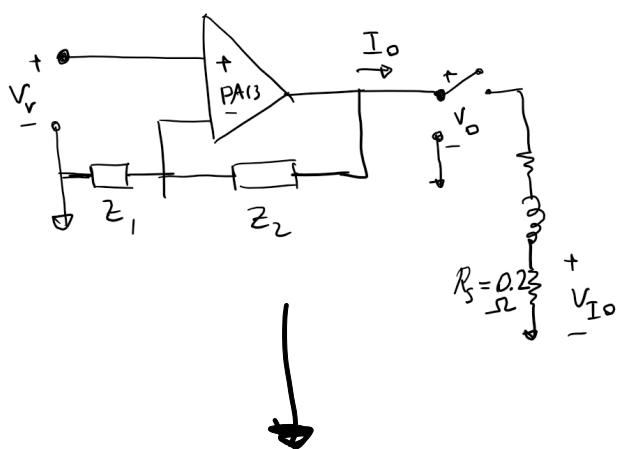


Figure 3: Open-loop frequency response of PA13.

$$f = \frac{z_1}{z_1 + z_2}$$

$$= \frac{A(s)}{s}$$

$$\frac{L(s)}{T(s)}$$

complementary

$$G(s) = \frac{A(s)f}{1 + A(s)f}$$


$$S(s) = \frac{V_e}{V_c} = \frac{1}{1 + L(s)} \rightarrow \text{dictates}$$

$$= \frac{dG/G}{dA/A}$$

$$T(s) = \frac{L(s)}{1 + L(s)} = \frac{A(s)f}{1 + A(s)f} \rightarrow \text{dictates}$$

} error dynamics
v: disturbance rejection
if $A(s)$ changes,
how much $G(s)$
is affected

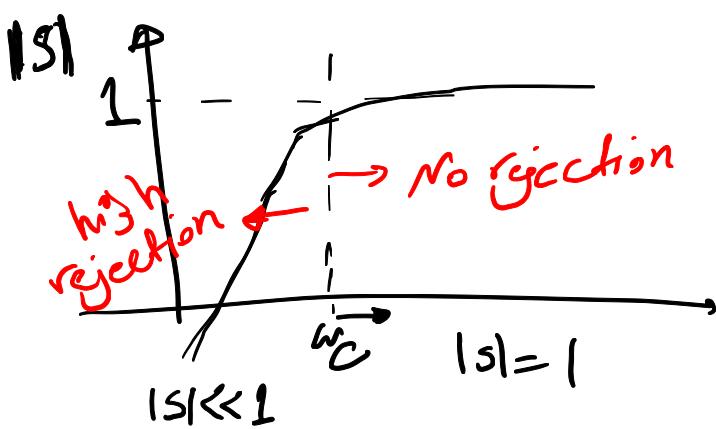} tracking
rise-time → Bandwidth
overshoot → Resonant Peak



$$S(s) = \frac{L}{1+L(s)}, \quad T(s) = \frac{L(s)}{1+L(s)}$$

$$|L| \gg 1$$

$\omega \ll \omega_c$

$$|s| \approx 0$$
$$|T| \approx 1$$

$$|L| \ll 1$$

$\omega \gg \omega_c$

$$|s| = 1$$
$$|T| = |L|$$
$$\text{and } T = L$$