

### Slide 18:

Normalized relation of  $v_o = \frac{R}{(R+R_c)} v_{ref} : \frac{v_o}{v_{ref}} = \frac{R/R_c}{(R/R_c + 1)}$

This is nonlinear. Also, see the characteristic curve.

### For small changes:

$$v_o = \frac{R}{(R+R_c)} v_{ref} \rightarrow \delta v_o = \frac{\partial v_o}{\partial R} \delta R + \frac{\partial v_o}{\partial R_c} \delta R_c \text{ (the familiar differential relation)}$$

Differentiate the original relation wrt the two parameters:

$$\frac{\partial v_o}{\partial R} = \frac{(R+R_c) - R}{(R+R_c)^2} v_{ref} = \frac{R_c}{(R+R_c)^2} v_{ref} ; \quad \frac{\partial v_o}{\partial R_c} = -\frac{R}{(R+R_c)^2} v_{ref}$$

Substitute:  $\delta v_o = \frac{R_c}{(R+R_c)^2} v_{ref} \delta R - \frac{R}{(R+R_c)^2} v_{ref} \delta R_c = \frac{v_{ref}}{(R+R_c)^2} [R_c \delta R - R \delta R_c]$

**Note:** Now, it is linear.

**Problem:** In the beginning, the circuit output is  $v_o = \frac{1}{2} v_{ref}$  if  $R_0 = R_{0c}$

→ Any associated change (e.g., noise) can completely mask the needed output change.

### Temperature Compensation:

For a temperature change of  $\Delta T$  the corresponding change in the output is

$$\delta v_o = \frac{v_{ref}}{(R_0 + R_{0c})^2} [R_{0c} R_0 (1 + \alpha \Delta T) - R_0 R_{0c} (1 + \alpha \Delta T)] = 0 \text{ where } ()_0 \text{ denotes initial values, and } \alpha$$

denotes the coefficient of thermal resistance of the material

**Note:** Since the material is assumed to be the same for the two resistors,  $\alpha$  is the same as well

Other assumption: The changes are small (O(2) terms in the Taylor series expansion are neglected.