

$$v_e = v_t - v_- = v_i - v_1$$

$$v_2 = v_o$$


v_x
only

Node current at v_2 : $\frac{v_o - Av_e}{R_2 + R_1} + \frac{v_o}{R_2} - I_o = 0$

$$v_o = \frac{R_o(R_2 + R_1)}{(R_o + R_1 + R_2)(v_x + I_o)}$$

$$v_1 = \frac{R_1}{R_1 + R_2} v_2 = \frac{R_1}{R_1 + R_2} v_o$$
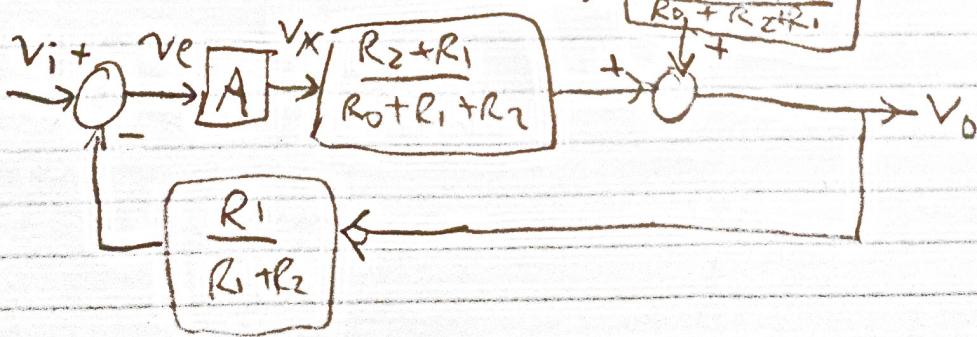
$$v_e = v_i - v_1 = v_i - \frac{R_1}{R_1 + R_2} v_o$$



B $L(s) = \text{loop return ratio}$

$$= -A \left(\frac{R_2 + R_1}{R_o + R_1 + R_2} \right) \left(\frac{R_1}{R_1 + R_2} \right)$$

$$= -A \left(\frac{R_1}{R_o + R_1 + R_2} \right)$$

$$Z_0 = \frac{V_o}{I_o} = \frac{\text{forward gain}}{1 - \text{loop ratio}} = \frac{\frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2}}{1 - \frac{1}{L}}$$


$$\frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2}$$

$$1 + A \left(\frac{R_1}{R_o + R_1 + R_2} \right)$$

TC $A|_{w \rightarrow 0} = 0 \Rightarrow L = A(\dots)|_{w \rightarrow 0} = 0(\dots) = 0$

$$\rightarrow Z_0|_{w \rightarrow 0} = \frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2} = \frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2} = \frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2}$$

$$Z(s) = \frac{Z_0(s)}{Z_0(j\omega)|_{w \rightarrow 0}} = \frac{\frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2} / (1 - \frac{1}{L})}{\frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2}} = \frac{1}{1 - \frac{1}{L(s)}}$$

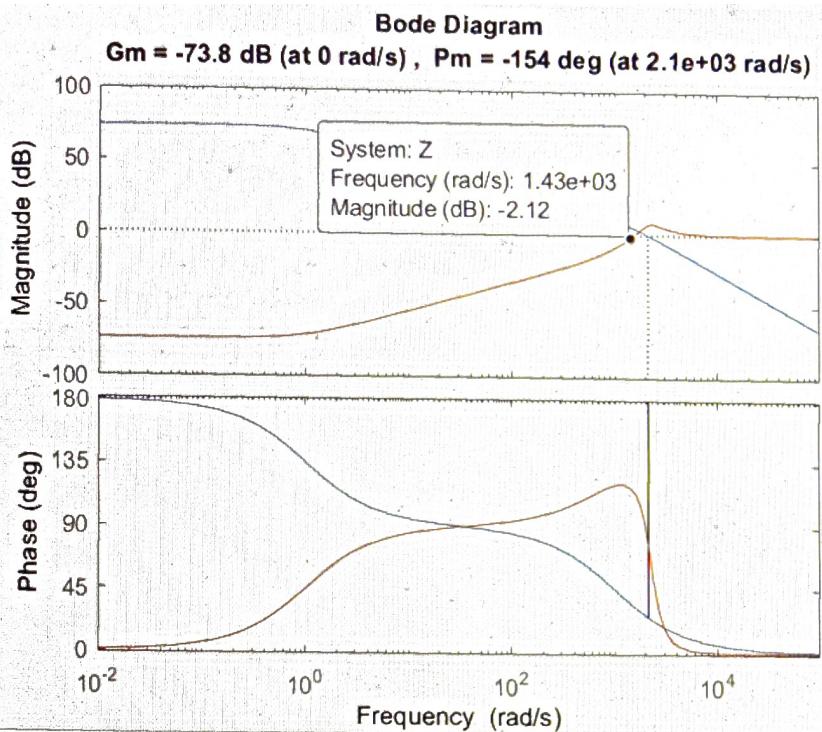

```
r0 = 50;
r1 = 1000;
r2 = 1000;
A = tf([10000], [.001 1.001 1]);
L = -(r1/(r0+r1+r2))*A;
Z = 1/(1-L);
figure(1);
hold on;
margin(L);
bode(Z);
hold off;
[Gm,Pm,Wcg,Wcp] = margin(L);
cutoffFreq = bandwidth(Z);
disp(Wcg);
disp(Pm);
disp(L);
disp(Z);
```


w_c = 0
pm = -154 deg
w_t = 1.43e3 rad/s

Shape of $|L(j\omega)|$ and $|Z(j\omega)|$ are approximately symmetric along 0dB line.

Q1e.


$$Z_0(j\omega)|_{W=0} = \frac{R_0(R_f+R_d)}{R_0+R_f+R_d} \times \frac{s_0(1k\text{mK})}{s_0+1k\text{mK}} = \frac{100000}{2050} = 48.78$$


2a

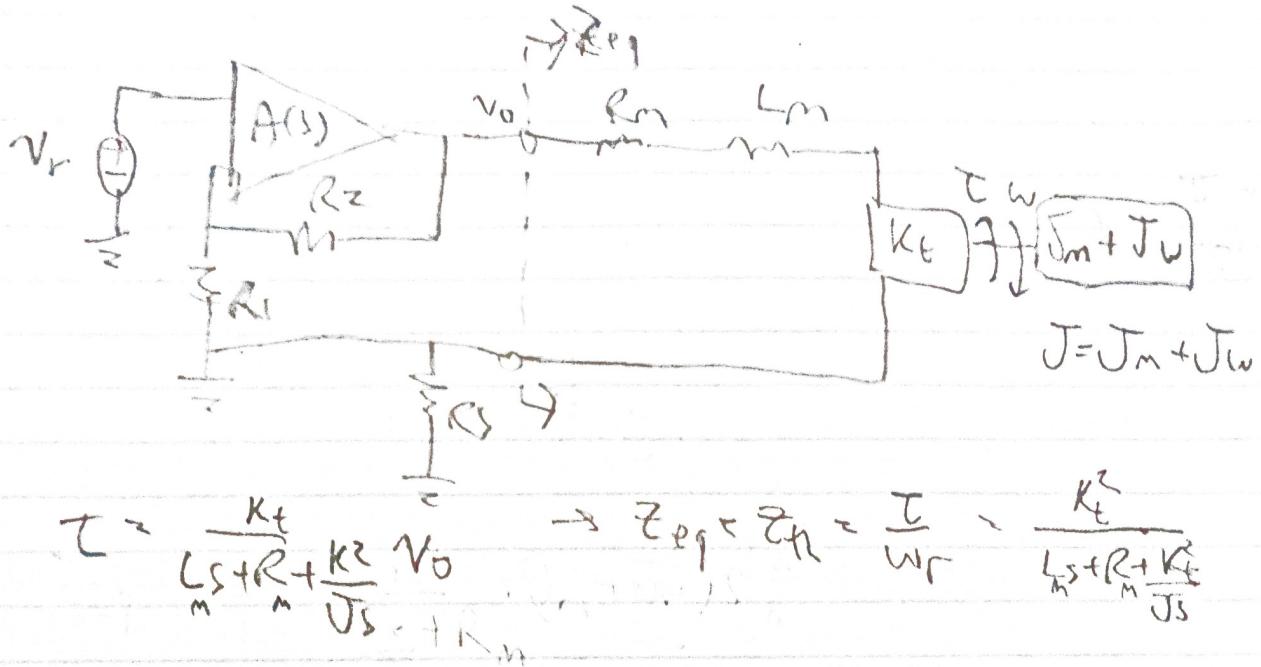

$$T = \frac{K_t}{L_s + R_m + K_t} \frac{V_o}{J_s} \rightarrow Z_{eq} = Z_R = \frac{T}{\omega_r} = \frac{K_t^2}{L_s + R_m + K_t}$$

2b

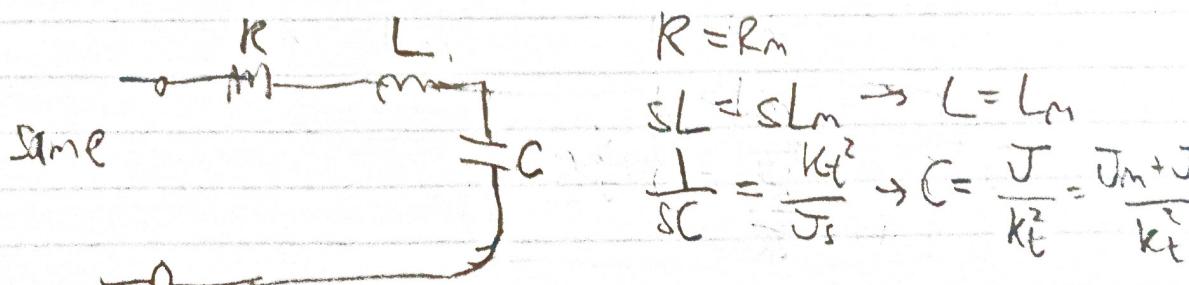

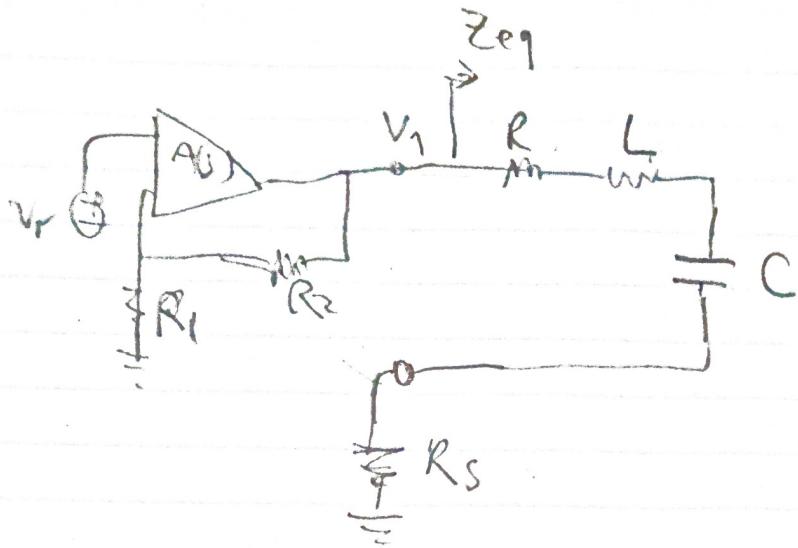

$$\frac{V_1}{V_r} = \frac{A}{1+A} \quad f = \frac{R_2}{R_1 + R_2}$$

$$V_1 = I_o(z_{eq} + R_s)$$


$$\frac{I_o}{V_r} = (z_{eq} + R_s)$$

$$\frac{I_o}{V_r} = \frac{I_o}{V_r} \left(\frac{V_1}{V_r} \right) = (z_{eq} + R_s) \left(\frac{A}{1+A} \right)$$

$$= \left(\frac{k^2}{L_m s + R_m + k^2} + R_s \right) \left(\frac{A}{1+A \left(\frac{R_2}{R_1 + R_2} \right)} \right)$$

$$= \left(\left(\frac{k^2}{(L_m s + R_m) J_s + k^2} \right) + R_s \right) \left(\frac{A}{1+A \left(\frac{R_2}{R_1 + R_2} \right)} \right)$$

2C.

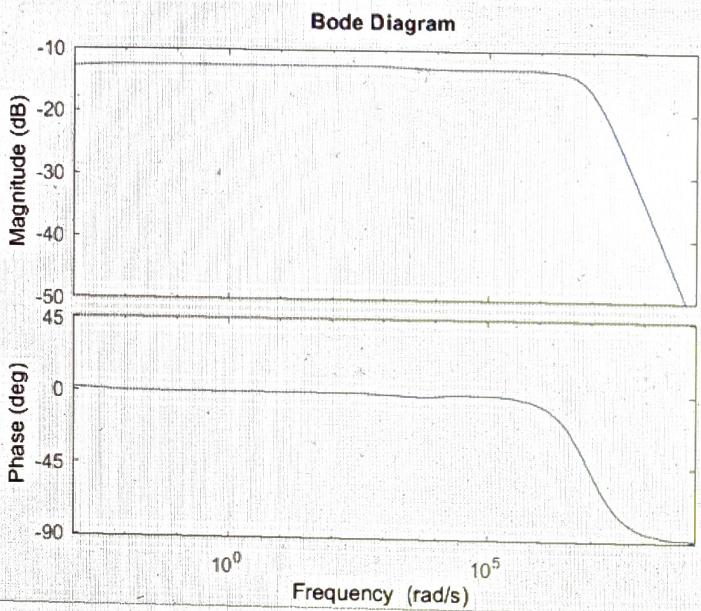

```
q2_vars.m X hw2_1.m X hw2_2.m X + . . .
1 - A = tf([10000000], [1 0]);
2 - r1 = 1000;
3 - r2 = 9000;
4 - rm = 4.8;
5 - Lm = .001;
6 - rs = .2;
7 - Kt = .25;
8 - Jm = 1;
9 - Jw = 9;
10 - %Jm = 1*0.0001; % use SI
11 - %Jw = 9*0.0001;
12 - J = Jm + Jw;
13 - Zeq = tf([Kt*Kt*J 0], [J*Lm J*rm Kt*Kt]);
14 - I_V = (Zeq+rs)*(A/(1+A*(r2/(r1+r2)))); 
15 - bode(I_V);

Command Window
New to MATLAB? See resources for Getting Started.
```

Q11

$$P = I^2 R$$

$$P_{max} = I_{max} R_S$$

$$I_{max} \cdot P_{max} = \frac{1W}{R_S} = 5A$$

$$I_{0, rms} = \frac{I_{max}}{\sqrt{2}} = 3.536A$$

B.

$$50\pi/2 = 314.6 \text{ rad/s}$$

$$\frac{Z_0}{V_t} = -12.5 \text{ dB} = 0.237 \frac{A}{V}$$

$\omega = 314.6 \text{ rad/s}$ (from Bode plot)

$$V_{t, rms} = I_{0, rms} \left(\frac{V_t}{Z_0} \right) = 3.536 (0.237)^{-1} = 14.9 V$$