
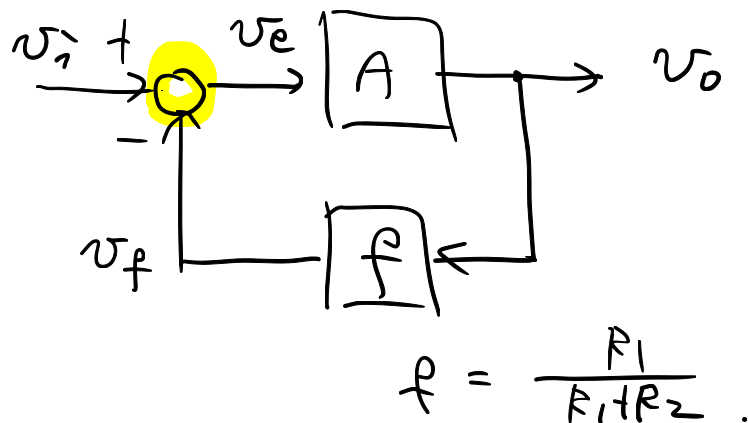


L5 - Op-Amp (Statics)

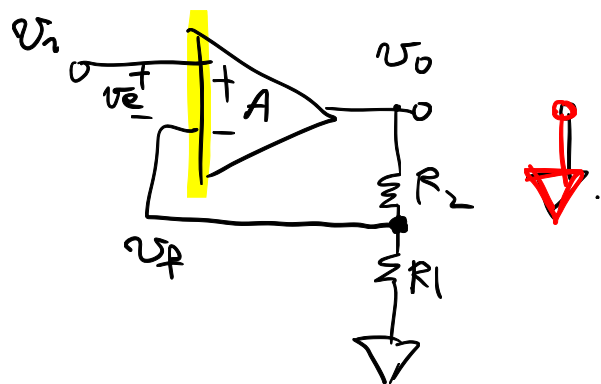

$$\frac{v_o}{v_i} \triangleq G = \frac{A}{1 + Af}$$


① $Af \rightarrow \infty \Rightarrow G = \frac{A}{1 + Af} \approx \frac{A}{Af} = \frac{1}{f}$. \underline{G} is not affected by A .

② $Af \not\rightarrow \infty$. $A = \text{constant}$. Op27. $|A(j\omega)|_{\omega \rightarrow 0} \approx \underline{125 \text{ dB}}$

$$10^{\frac{125 \text{ dB}}{20 \text{ dB}}} = 10^{6.25} \approx \boxed{10^6}$$

How to quantify $\frac{dA}{A} \approx 10\% \rightarrow \frac{dG}{G} ?$

"Gain sensitivity"

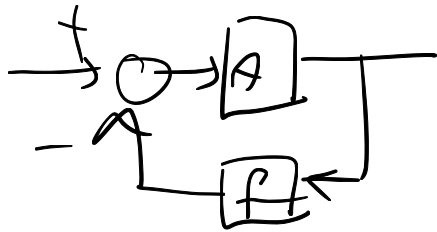

① $f=0 \Rightarrow \underline{dA = dG}$

$\frac{dG}{G} = \frac{dA}{A} = \underline{10\%}$ ↙

② $f \neq 0 \Rightarrow G = \frac{A}{1+Af}$

$$dG = \frac{dA(1+Af) - A(dA \cdot f)}{(1+Af)^2}$$

$$= \frac{dA + \cancel{dA}Af - A\cancel{dA}f}{(1+Af)^2}$$

$$= \frac{dA}{(1+Af)^2}$$



$$G = \frac{A}{1+Af} \quad \frac{dG}{G} = \frac{1+Af}{A} \cdot \frac{dA}{(1+Af)^2} = \underbrace{\left(\frac{1}{1+Af} \right)}_{\cong S} \frac{dA}{A} \quad \downarrow 10\%..$$

Op27 : $A \approx 10^6$, $f = \frac{1}{10}$

$$Af \approx 10^5 \rightarrow \frac{1}{1+Af} = \frac{1}{1+10^5} = \frac{10^{-5}}{10^{-5}+1} \approx 10^{-5}$$

• Sensitivity function : $S(s) \stackrel{D}{=} \frac{1}{1+L(s)}$

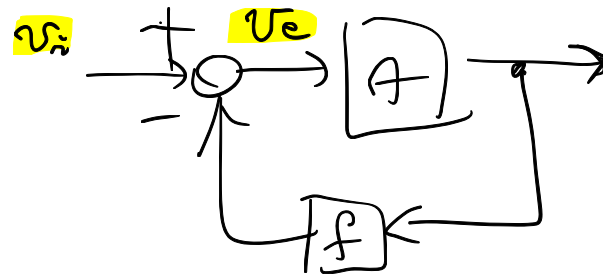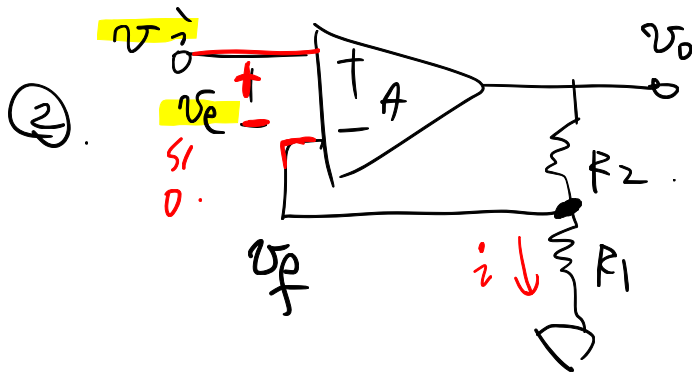① - Feedback makes the system "Insensitive" to change in A .



$$\frac{v_e}{v_i} = \frac{1}{1 + Af} = S(s).$$

When $Af = L \rightarrow \infty$. $S \rightarrow 0$.

~~$v_e = S \cdot v_i$~~


"Feedback syst. reject dist."

As $Af \rightarrow \infty$.


As long as $Af \gg 1$, $v_e \approx 0$ "virtual short"

Example As $Af \rightarrow \infty$, $v_f \approx v_i$ $v_o = v_f \frac{1}{R_1} (R_1 R_2)$

$$\approx v_i \frac{1}{R_1} (R_1 R_2)$$

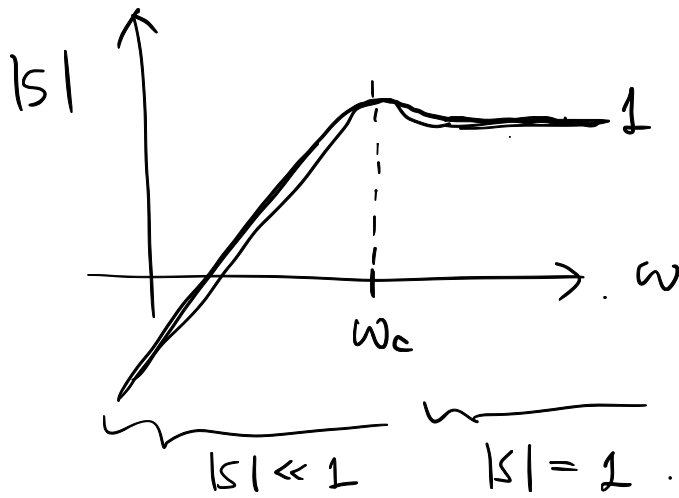

$$v_o \approx \frac{R_1 R_2}{R_1} v_i$$

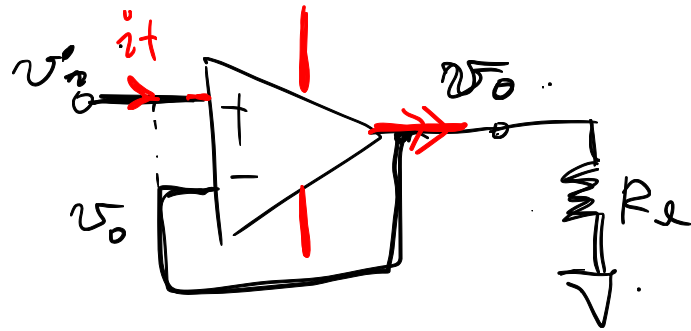

$$\boxed{v_o \approx v_i} \quad G = 1$$

Q. Amplifier?

A. Yes.


Q. What does it amplify?

A. Power.


{ $P_{in} = v_i i_i \approx 0$

$P_{out} = v_o i_o = \frac{v_o^2}{R} \quad \underline{\underline{100W!}}$



"Power Amplifier"

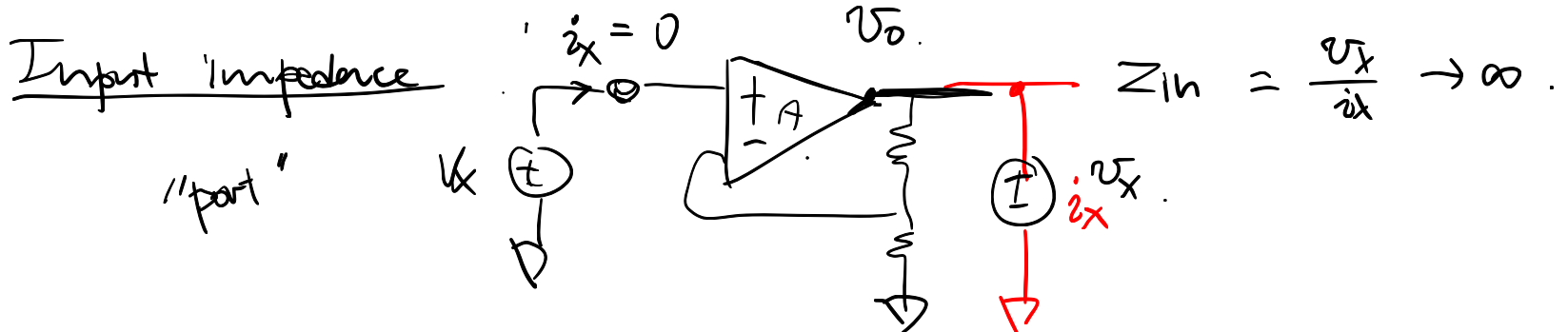

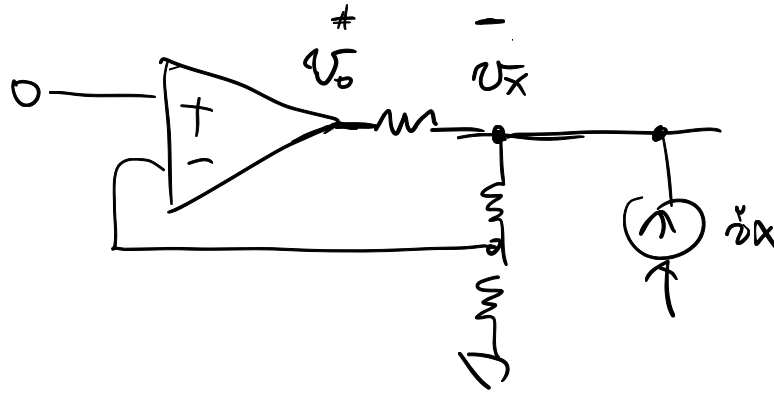Output Z . $Z_{out} = \frac{v_x}{i_x} \approx 0$.



Inverting Amp

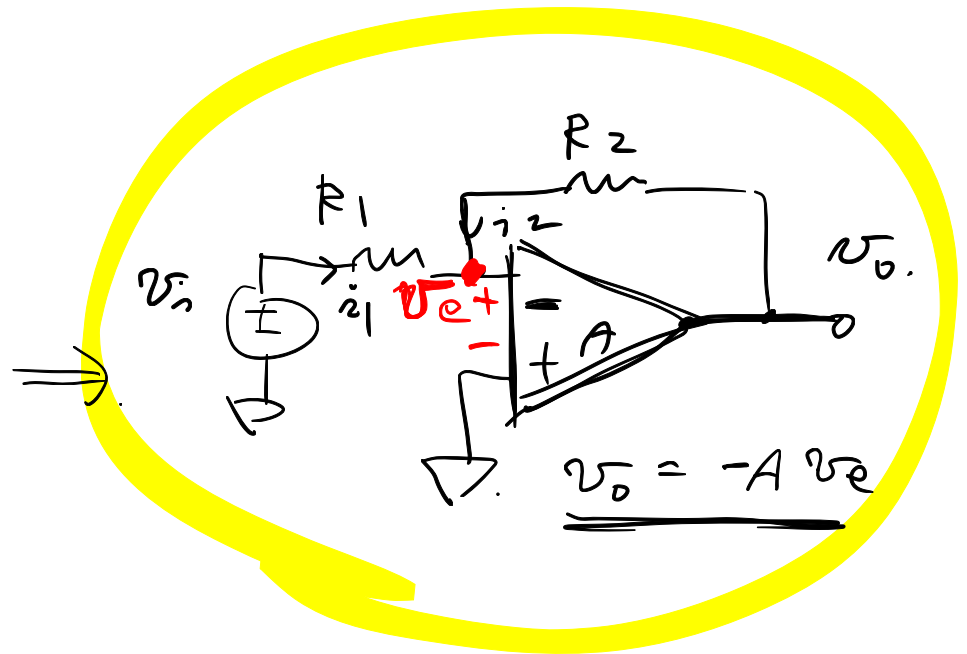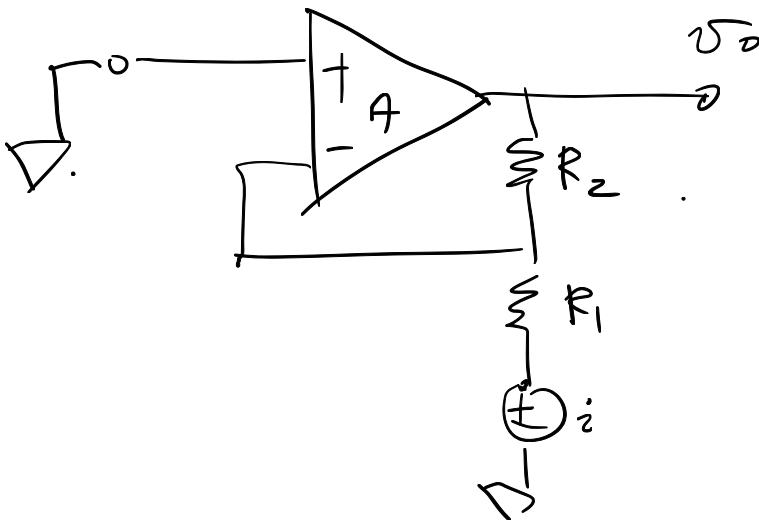

$A \rightarrow \infty$. $v_e \approx 0$.

KCL: $i_1 + i_2 = 0 \Rightarrow v_i \rightarrow \boxed{\frac{1}{R_1}} \xrightarrow{i_1} \boxed{-1} \xrightarrow{i_2} \boxed{R_2} \rightarrow v_o$.

$A = \text{const}$


$\frac{v_o}{v_i} = -\frac{R_2}{R_1}$

① Node Method

I Apply KCL: $\sum i = 0$.

$\frac{v_e - v_i}{R_1} + \frac{v_e - v_o}{R_2} = 0$

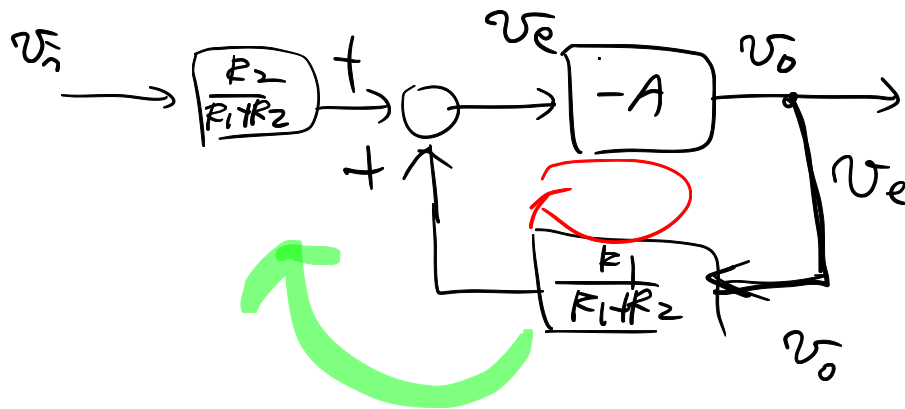$v_e \left(\frac{1}{R_1} + \frac{1}{R_2} \right) = + \frac{1}{R_1} v_i + \frac{1}{R_2} v_o$





$$= \left(\frac{\frac{1}{R_1}}{\frac{1}{R_1} + \frac{1}{R_2}} \right) v_i + \left(\frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} \right) v_o$$

$$= \left(\frac{R_2}{R_1 + R_2} \right) v_i + \left(\frac{R_1}{R_1 + R_2} \right) v_o$$

II $v_o = -A v_e$


$L(s) = ?$

$A \cdot \frac{R_1}{R_1 + R_2}$ AP

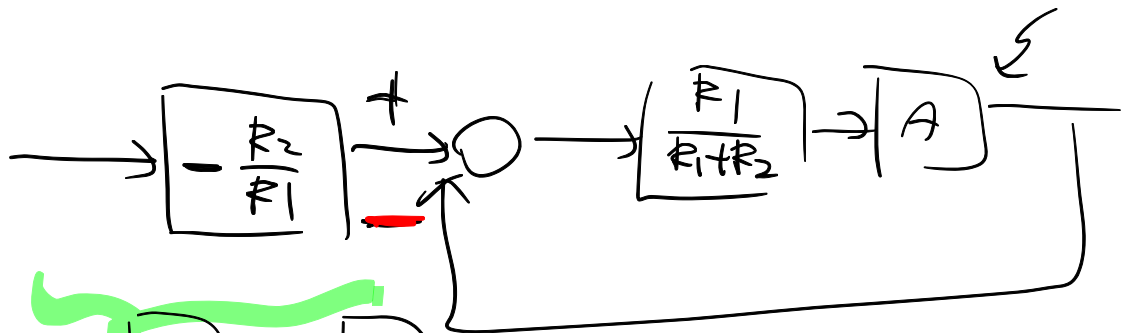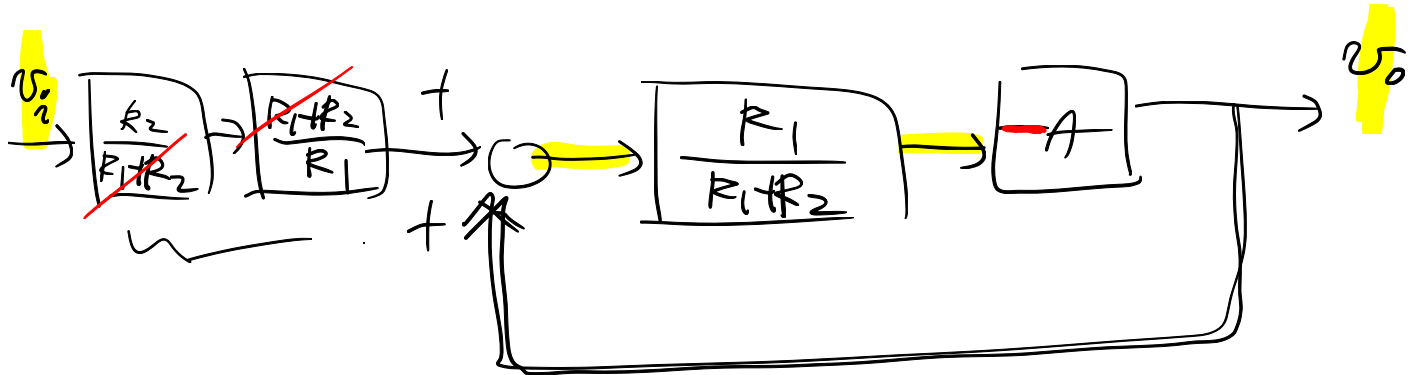

① $A(s) = \frac{\omega_0}{s}$

② $A(j\omega)$

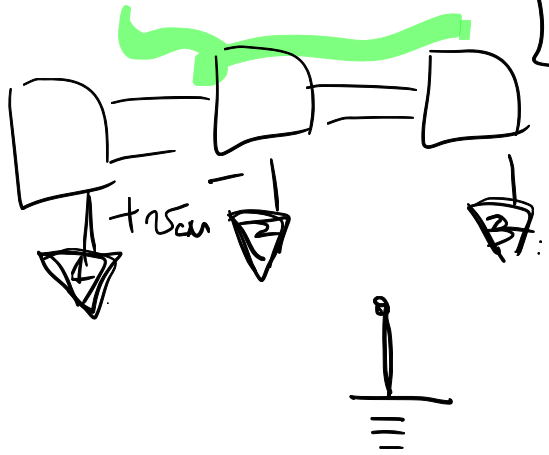

Low Impedance

V

