

The following questions are centered on the electrical circuit shown in Figure 1. In the following questions, assuming OP27 is an ideal Op-Amp with infinite gain for all frequencies. PA52 is a power device with frequency response shown in Figure 2. L and Rm are the motor inductance and resistance. The current-sensing resistor Rs has a resistance value of 0.2 Ohm. R4=2k Ohm. R5=10k Ohm. Rm=3.8 Ohm. L=6 mH.

- 1 -

- (2) (30 marks) Looking at the voltage stage only, with input V_c and output V_o .
- Design resistors R_1 and R_2 so that the voltage stage DC gain is: $V_o = -9V_c$ at DC.
 - Is this voltage stage stable? If yes, what's the negative loop transmission crossover frequency of the voltage stage, and what's its phase margin?
- (3) (40 marks) This section investigates the current controller design. The goal is to design a current controller with 10 kHz bandwidth. To simplify the current controller design process, the voltage stage is simplified as a constant gain element ($V_o = -9V_c$) for all frequencies.
- Select R_3 , R_6 , and C so that the overall system is stable with 10kHz bandwidth and at least 60 degree phase margin.
 - Draw Bode plots for the current controller transfer function from V_s to V_c .
 - Draw Bode plots for the current loop NLT(negative loop transmission).

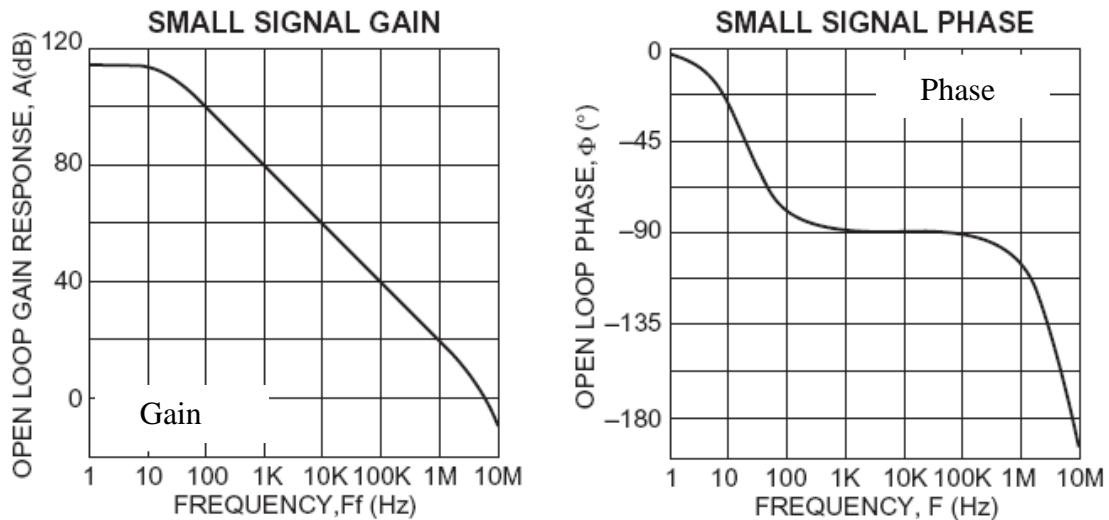


Figure 2: PA52 open loop frequency response.