

**THE UNIVERSITY OF BRITISH COLUMBIA  
DEPARTMENT OF MECHANICAL ENGINEERING**

**MECH 420 SENSORS AND ACTUATORS**


**Mid-Term Examination  
30 October 2019**

- **Duration: 50 minutes**
- **Closed Book/Notes**
- **An 8.5"×11" Fact Sheet (two-sided) is allowed**
- **Calculators are allowed, only in the arithmetic (numerical computation) mode**
- **Fully answer both questions for full credit**
- **Clearly state all your assumptions and give all your steps of the derivations**
- **Define any new variables or parameters that you may use**
- **This question paper contains four (4) pages including this cover sheet.**

### Question 1

Consider the circuit shown in Figure 1, which consists of two stages A and B. The input signal to the circuit is  $v_i$  and the output signal is  $v_o$ .

- (a) What is the function of the circuit segment A? What is the function of the circuit segment B? **(5%)**
- (b) Derive the time-domain differential equation of the entire circuit, relating  $v_i$  and  $v_o$ , in terms of the resistance and capacitance parameters shown in Figure 1. Determine the corresponding transfer function  $\frac{v_o}{v_i}$  in the Laplace domain. Also, determine the DC gain  $k$  and the time constant  $\tau$  of the overall circuit in terms of the given circuit parameters. **(30%)**
- (c) Suppose that  $R_1 = 100 \text{ k}\Omega$ ,  $R_2 = 200 \text{ k}\Omega$ ,  $R = 100 \text{ k}\Omega$ , and  $C = 0.2 \text{ }\mu\text{F}$ . Compute the half-power bandwidth of the entire circuit in rad/s. **(5%)**
- (d) Suppose that the signal  $v_i$  is generated by a sensor. With proper justification, suggest a suitable (maximum) time constant for the sensor. **(10%)**

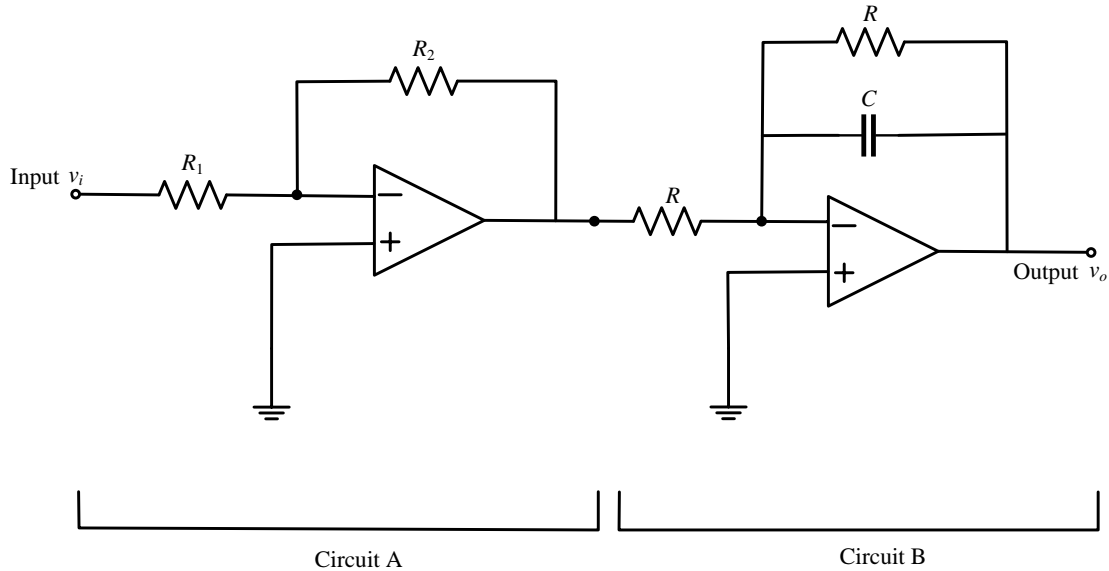

**Figure 1: An analog circuit consisting of two stages.**

## **Question 2**

(i)

The sensitivities of several sensors, as found in their commercial data sheets, are given in Table 2. Carefully explain the meaning of each of these sensitivity values.

**Table 2: Sensitivities of some practical sensors.**

<b>Sensor</b>	<b>Sensitivity</b>
Blood Pressure Sensor	10 mV/V/mm Hg
Capacitive Displacement Sensor	10.0 V/mm
DC Tachometer	7 VDC $\pm$ 3% for 1000 rpm
Light Sensor (digital output with ADC)	50 counts/lux
Strain Gauge (gauge factor)	150 $\Delta R/R$ /strain (dimensionless)

**(15%)**

(ii)

A Wheatstone bridge circuit is shown in Figure 2. The resistance of the four arms are as indicated in the figure. The supply voltage to the bridge is  $v_{ref}$  and the output voltage of the bridge is  $v_o$ .

(a) Giving sufficient details of the derivation, show that the output voltage of the

bridge is given by  $v_o = \frac{R_1 v_{ref}}{(R_1 + R_2)} - \frac{R_3 v_{ref}}{(R_3 + R_4)}$ . If  $\frac{R_1}{R_2} = \frac{R_3}{R_4}$  what is the output

voltage? **(10%)**

(b) In sufficient detail derive the sensitivity of the bridge output to a change in the


arm resistance  $R_1$ . Specifically, derive an expression for  $\frac{\partial v_o}{\partial R_1}$  in terms of  $R_1$ ,  $R_2$ ,

and  $v_{ref}$ . Using suitable normalizing quantities, determine an expression for the corresponding normalized (i.e., non-dimensional) sensitivity. If  $R_1 = R_2$ , evaluate the non-dimensional sensitivity. **(20%)**

(c) Suppose that  $R_1$  is the only active element in the bridge circuit of Figure 1, and this active element is a semiconductor strain gauge. Also, suppose that initially, the bridge is balanced with  $R_1 = R_2 = R_3 = R_4 = R$ . For a strain  $\varepsilon$ , the strain gauge

changes its resistance by  $\delta R$  according to the relation  $\frac{\delta R}{R} = S_1 \varepsilon + S_2 \varepsilon^2$ , where  $S_1$  and  $S_2$  are parameters of the strain gauge, which may be obtained from the data sheet of the strain gauge. Derive an expression for the corresponding bridge output  $\delta v_o$  in terms of the measurand  $\varepsilon$  and the quantities  $S_1$ ,  $S_2$ , and  $v_{\text{ref}}$ . **(5%)**

- (d) Suggest a suitable way to express the sensitivity of the overall device (strain gauge and bridge combination) in Part (c), where the output is in mV and the input is in microstrains ( $\mu$ -strain). Give an approximate (linearized) expression for this sensitivity. What is the maximum possible sensitivity error? **(Bonus 5%)**

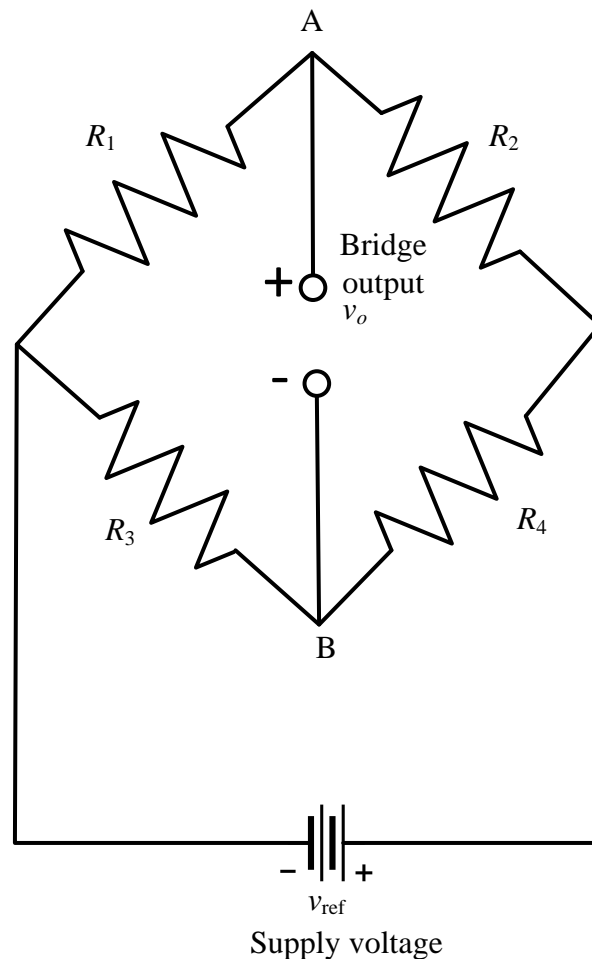

**Figure 2: A Wheatstone bridge circuit.**