

## Homework 3

Assigned: Feb 5, 2021

Due: Feb 12, 2021

### Problem 1

Let us consider an op-amp circuit in Figure 1. We assume that the op-amp input impedance is infinite, the output impedance is  $R_o$ , and the open-loop gain is  $A(s)$ . Note that the output impedance  $R_o$  is pulled out of the op-amp.


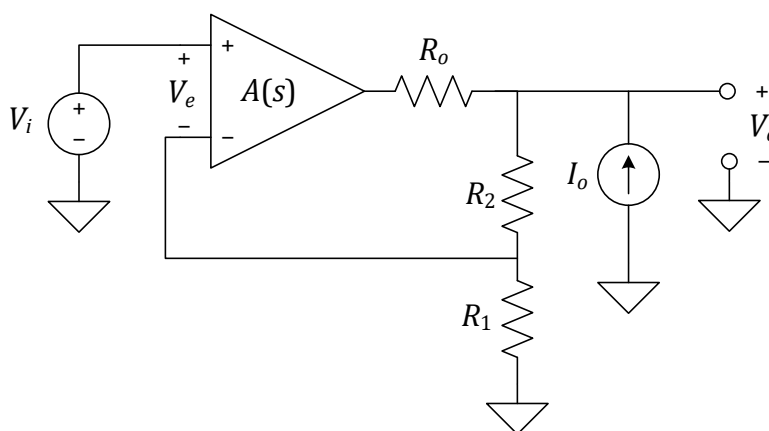


Figure 1: Schematic of a non-inverting amplifier.

- (a) Draw a block diagram that shows the relation between the input voltage  $V_i$ , disturbance current  $I_o$ , and the output voltage  $V_o$ . The block diagram should show a feedback loop around  $A(s)$ .

**Answer:**

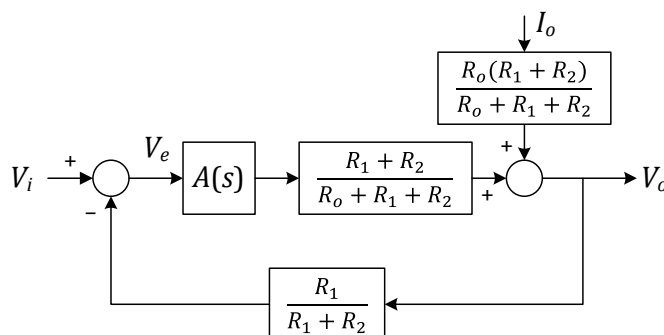

Refer to the **Homework 2 – Problem 1** for the derivation.

- (b) Find the expression for the loop transfer function  $L(s)$ . Also, find the expression for the output impedance  $Z_o(s) = V_o/I_o$  in terms of  $L(s)$ ,  $R_o$ ,  $R_1$ , and  $R_2$ .

**Answer:**

The loop transfer function is

$$L(s) = A(s) \frac{R_1}{R_o + R_1 + R_2}.$$

The output impedance is

$$\begin{aligned} Z_o(s) &= R_o \parallel (R_1 + R_2) \left( \frac{1}{1 + L(s)} \right) \\ &= \frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2} \left( \frac{1}{1 + L(s)} \right). \end{aligned}$$

- (c) Assuming the op-amp high-frequency open-loop gain is zero, i.e.,  $A(j\omega)|_{\omega \rightarrow \infty} = 0$ , find the expression for the high-frequency output impedance  $Z_o(j\omega)|_{\omega \rightarrow \infty}$  in terms of  $R_o$ ,  $R_1$ , and  $R_2$ . Also, find the expression for the output impedance normalized to the high-frequency value, i.e.,

$$\hat{Z}(s) \equiv \frac{Z_o(s)}{Z_o(j\omega)|_{\omega \rightarrow \infty}}$$

in terms of  $L(s)$ .

**Answer:**

If  $A(j\omega)|_{\omega \rightarrow \infty} = 0$ , then  $L(j\omega)|_{\omega \rightarrow \infty} = 0$  as well. Therefore,

$$\begin{aligned} Z_o(j\omega)|_{\omega \rightarrow \infty} &= \frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2} \left( \frac{1}{1 + L} \right) \xrightarrow{\omega \rightarrow \infty} \frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2} \\ &= \frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2} \end{aligned}$$

Thus, the normalized output impedance is

$$\hat{Z}(s) = \frac{1}{1 + L(s)} \equiv S(s)$$

- (d) Using MATLAB, draw the Bode plots of  $L(s)$  and  $\hat{Z}(s)$  for

$$R_o = 50 \, \Omega \quad R_1 = 1 \, \text{k}\Omega \quad R_2 = 1 \, \text{k}\Omega \quad A(s) = \frac{10^4}{(s + 1)(0.001s + 1)}$$

on the same graph. Find the gain crossover frequency  $\omega_c$  and phase margin  $\phi_m$  of  $L(s)$ , and also find the cutoff frequency  $\omega_l$  where  $|\hat{Z}(j\omega_l)| = 0.7071(-3 \text{ dB})$ . Discuss how the shapes of  $|L(j\omega)|$  and  $|\hat{Z}(j\omega)|$  are related at frequencies below  $\omega_c$ .

**Answer:**

The gain crossover frequency and phase margin of  $L(s)$  are


$$\omega_c = 2098 \text{ rad/s}$$

$$\phi_m = 25.5^\circ$$

The cutoff frequency  $\omega_l$  where  $|S(j\omega_l)| = 0.7071(-3 \text{ dB})$  is

$$\omega_l = 1370 \text{ rad/s}$$

The Bode plots are as follows.

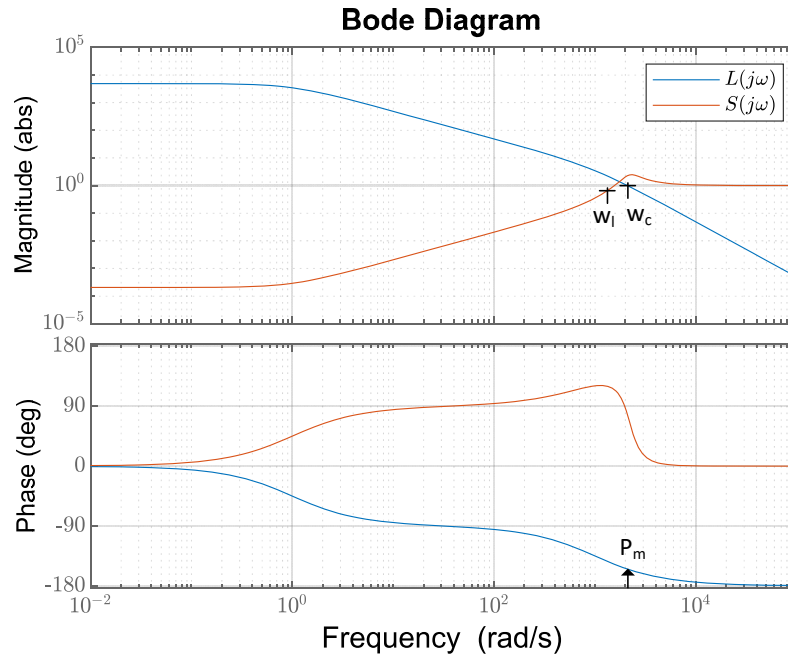

Note that below  $\omega_l$ , the shapes of  $|L(j\omega)|$  and  $|S(j\omega)|$  are symmetric with respect to the unity line (zero dB line) and the shapes of  $\angle L(j\omega)$  and  $\angle S(j\omega)$  are symmetric with respect to the zero angle line.

(e) Find the output dc impedance  $Z_o(j\omega)|_{\omega=0}$

**Answer:**

$$\begin{aligned}
Z_o(j\omega)|_{\omega=0} &= \frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2} \left( \frac{1}{1 + L(j\omega)|_{\omega=0}} \right) \\
&= \frac{R_o(R_1 + R_2)}{R_o + R_1 + R_2} \left( \frac{1}{1 + \frac{R_1}{R_o + R_1 + R_2} A(j\omega)|_{\omega=0}} \right) \\
&= 48.78 \Omega \frac{1}{1 + 0.4878 \times 10^4} \\
&= 0.01 \Omega
\end{aligned}$$

Alternatively, one can find the approximate output DC impedance as follows. Since  $R_o \ll R_1 + R_2$ ,

$$\begin{aligned}
R_o \parallel (R_1 + R_2) &\approx R_o = 50 \Omega \\
f &= \frac{R_1}{R_o + R_1 + R_2} \approx \frac{R_1}{R_1 + R_2} = 0.5
\end{aligned}$$

Also, since  $f A(j\omega)|_{\omega=0} \gg 1$

$$\frac{1}{1 + f A(j\omega)|_{\omega=0}} \approx \frac{1}{f A(j\omega)|_{\omega=0}} = \frac{1}{5000}$$

Therefore,

$$Z_o(j\omega)|_{\omega=0} \approx \frac{50 \Omega}{5000} = 0.01 \Omega.$$

Note that this is quite close to the exact value.

## Problem 2

Let us consider a brushed dc motor driven by a voltage amplifier shown in Figure ?? . Here,  $L_m$  is the winding inductance,  $R_m$  is the winding resistance,  $J_m$  is the rotor rotational inertia, and  $K_t$  is the motor torque constant. There is a wheel mounted on the motor shaft, whose rotational inertia is  $J_w$ . On the current return path, there is a shunt resistor  $R_s$  to measure the current through the motor winding.


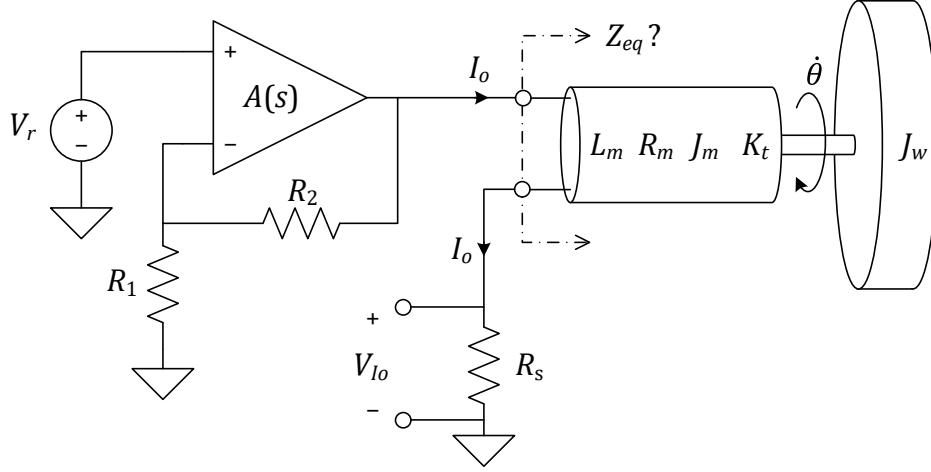


Figure 2: Brushed dc motor driven by an op-amp circuit.

- (a) Find the electrical impedance  $Z_{eq}(s)$  looking into the electrical port of the motor.

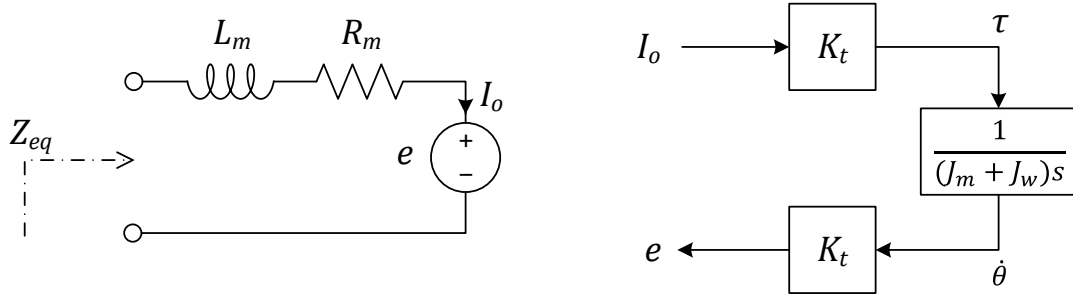**Answer:**

The electrical part of the motor can be modeled as follows.




Here, the back EMF is modeled as a speed-dependent voltage source  $e$ . The apparent impedance of this element is the ratio between the voltage drop across the element and the current through the element, i.e.,  $e/I_o = \frac{K_t^2}{(J_m + J_w)s}$ , which can be found from the block diagram on the right. Therefore, the total impedance  $Z_{eq}(s)$  is

$$Z_{eq}(s) = L_ms + R_m + \frac{K^2}{(J_m + J_w)s}$$

- (b) Draw an equivalent circuit diagram where all mechanical elements are referred to the electrical domain as passive electrical elements. Find the parameter(s) of the equivalent circuit element(s) in terms of  $L_m$ ,  $R_m$ ,  $J_m$ ,  $K_t$ , and  $J_w$ .

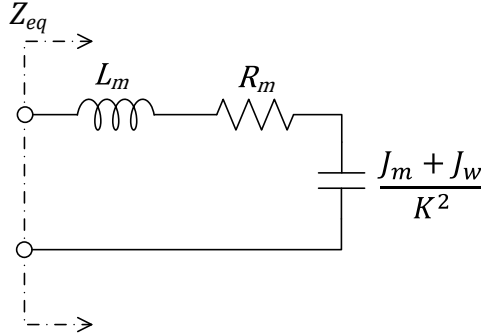**Answer:**

When the mechanical load is pure inertia, the speed-dependent voltage source appears as a capacitor whose capacitance is  $\frac{J_m + J_w}{K_t^2}$ . Therefore, an equivalent circuit diagram is as follows.



- (c) Find the analytic expression for the transconductance from  $V_r(s)$  to  $I_o(s)$ . Then, draw the Bode plot of  $I_o(s)/V_r(s)$  using MATLAB for


$$\begin{aligned}
 A(s) &= \frac{10^7}{s} & R_1 &= 1 \text{ k}\Omega & R_2 &= 9 \text{ k}\Omega \\
 R_m &= 4.8 \Omega & L_m &= 1 \text{ mH} & R_s &= 0.2 \Omega \\
 K_t &= 250 \text{ mNm/A} & J_m &= 1 \text{ kg} \cdot \text{cm}^2 & J_w &= 9 \text{ kg} \cdot \text{cm}^2
 \end{aligned}$$

**Answer:**

The analytical expression for the transconductance is

$$\frac{I_o(s)}{V_r(s)} = \underbrace{\frac{A(s)}{1 + A(s) \frac{R_1}{R_1 + R_2}}}_{V_o/V_r} \underbrace{\frac{1}{L_m s + R_m + R_s + \frac{K^2}{(J_m + J_w)s}}}_{I_o/V_o}$$

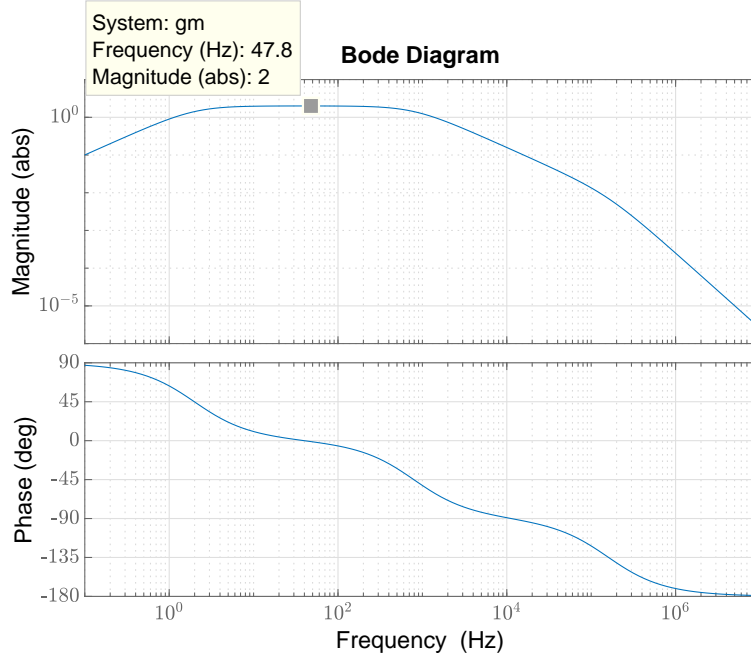Note that the second factor  $I_o/V_o$  also depends on the shunt resistor  $R_s$ . If  $R_s \ll R_m$ , we can ignore the effect of  $R_s$ . The bode plot of  $I_o/V_r$  is as follows.



Note that there are three break frequencies in the magnitude curve, and the bandwidth of the transconductance is limited between the first two break frequencies. The first one around 20 Hz is related with the motor mechanical time constant  $\tau_m = J_{\text{net}}/b_{\text{net}}$ , where  $b_{\text{net}} = \frac{K_t^2}{R}$  is the apparent damping. Note that this time constant not only depends on the rotor inertia but also depends on the load inertia. The second one around 1 kHz is related with the motor electrical time constant  $\tau_e = L/R$ . The last one around 200 kHz is from the voltage amplifier bandwidth.

- (d) Let us assume that the shunt resistor  $R_s$  is rated for 1 W power. That is, the resistor fails when it dissipates more than 1 W. What is the maximum rms current  $I_{o,\text{rms}}$  allowed for the shunt resistor?

**Answer:**

The maximum permissible rms current for the shunt resistor is

$$I_{o,\text{rms}} = \sqrt{\frac{1 \text{ W}}{R_s}} = 2.2361 \text{ A}_{\text{rms}}.$$

- (e) Let the input voltage  $V_r$  be sinusoidal at 50 Hz. What is the maximum rms voltage  $V_{r,\text{rms}}$  that the shunt resistor can accommodate for its power rating?

**Answer:**

The transconductance at 50 Hz is 2 A/V. Therefore, the maximum permissible rms reference voltage at 50 Hz is

$$V_{r,\text{rms}} = \frac{I_{o,\text{rms}}}{2 \text{ A/V}} = 1.118 \text{ V}_{\text{rms}}$$