


# < Current - controlled Brushed DC Motors >

Minkyam Noh.  
2021 / 2 / 8

## Objectives


- Understand the dynamics of current-controlled dc motors.
- Torque response & output impedance
- Transconductance amplifier design

$$G_i(s) = \frac{I_o}{U} \text{ [A/V]}$$

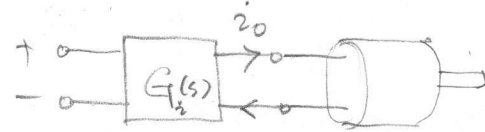


## Review

$$G_v(s) = \frac{V_o}{U} \text{ [V/V]}$$

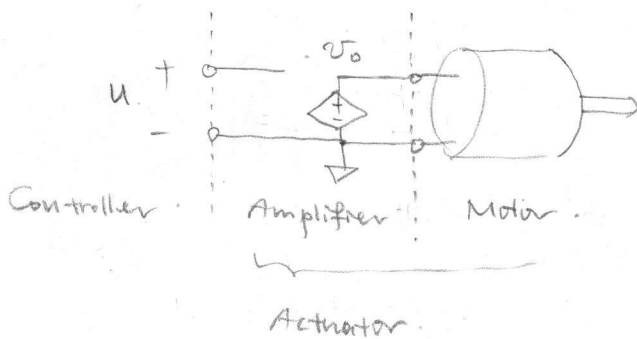

Assuming High-bandwidth  $G_v(s)$ .

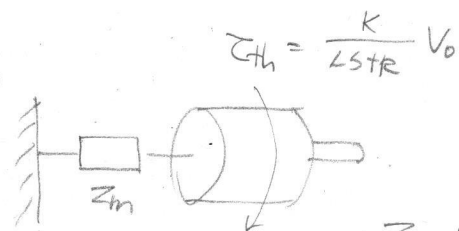


$$Z_m = \frac{K^2}{Z_e}$$

① slow torque resp.  $\therefore \omega_e = \frac{R}{L}$


② Actuator output impedance:  $Z_m = \frac{K^2}{Z_e}$

• What if we drive the motor with a current source?

$$G_i(s) = \frac{I_o}{U} \text{ [A/V]}$$

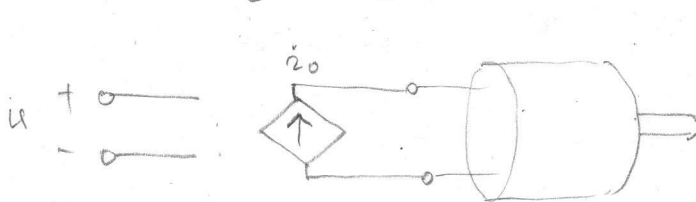

Assuming High-bandwidth  $G_i(s)$ .

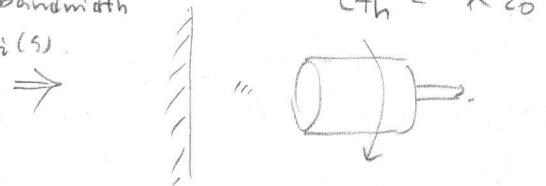

$$Z_m = \frac{K^2}{Z_e} \rightarrow 0$$

① Fast torque response:  $\tau = K \cdot i$

② Low output impedance

$\Rightarrow$  Closer to an ideal torque (or force) source

e.g.  $Z_m \rightarrow 0$  is important for vibration isolation

