


(a)

$$Z \equiv \frac{V}{I}$$

$$\gamma \equiv \frac{I}{V}$$



=

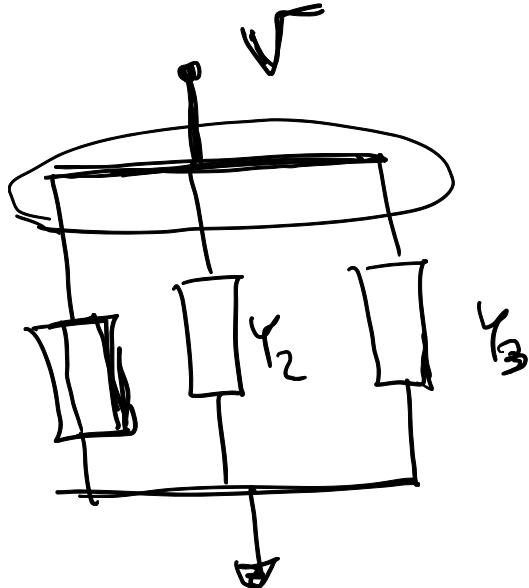

$$\gamma_1 V + \gamma_2 V + \gamma_3 V = \gamma_{eq} V$$

$$\Rightarrow \gamma_{eq} = \gamma_1 + \gamma_2 + \gamma_3$$


$$V_o(V_s, \gamma_1, \gamma_L) = ?$$

$$(V_o - V_s) \gamma_1 + (V_o - 0) \gamma_L = 0$$

$$\Rightarrow (\gamma_1 + \gamma_L) V_o = \gamma_1 V_s$$

$$\Rightarrow V_o = \frac{\gamma_1}{\gamma_1 + \gamma_L} V_s$$
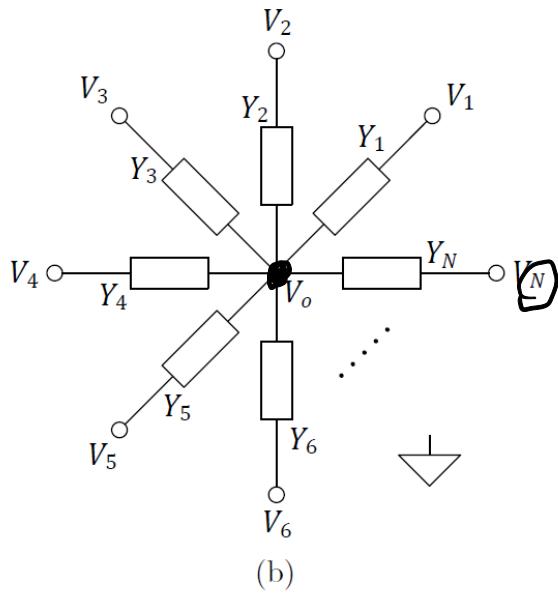
$$V_0 = \frac{\psi_1}{\sum_{i=1}^n \psi_i}$$



$$V_o(V_j, \gamma_i)$$


$$(V_0 - V_1)\gamma_1 + (V_0 - V_2)\gamma_2 + (V_0 - V_3)\gamma_3 = 0$$

$$(V_0 - V_1)\gamma_1 + (V_0 - V_2)\gamma_2 + (V_0 - V_3)\gamma_3 = 0$$

$$\gamma_1 V_1 + \gamma_2 V_2 + \gamma_3 V_3$$

$$\Rightarrow V_o = \frac{\gamma_1 V_1 + \gamma_2 V_2 + \gamma_3 V_3}{\gamma_1 + \gamma_2 + \gamma_3}$$

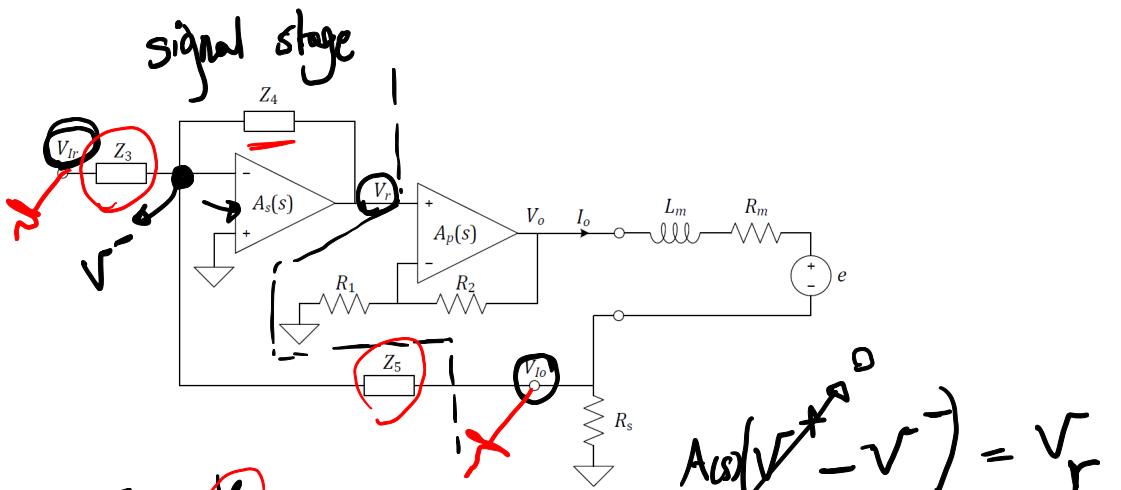
$$V_o = \frac{\sum_{i=1}^N \gamma_i \cdot V_i}{\gamma_j}$$



$$\checkmark V_{Ir}, \checkmark V_{Io}, \checkmark V_r$$

Superposition:
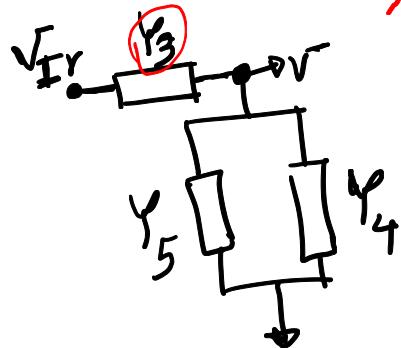
$$\begin{array}{ll} \checkmark V_{Ir} \\ \times V_r \\ \times V_{Io} \end{array}$$






$$A(s)(\checkmark - \cancel{\checkmark}) = \checkmark V_r$$

$$\boxed{V_r = -A(s) \checkmark}$$

$$Y_3 = \frac{1}{Z_3}$$

$$\checkmark V_1^- = \frac{Y_3}{Y_4 + Y_5 + Y_3} V_{Ir}$$
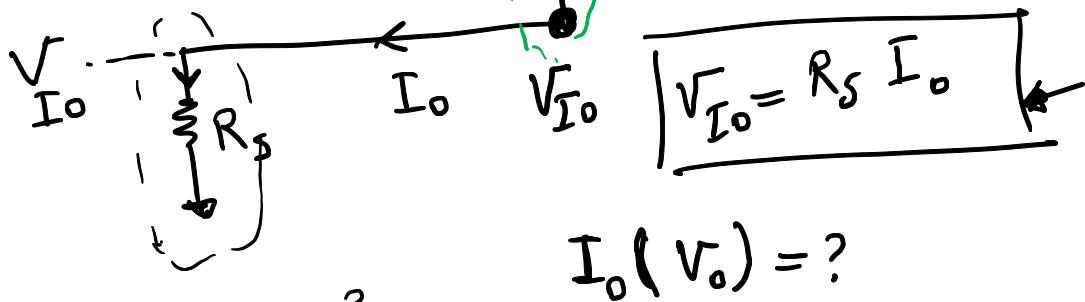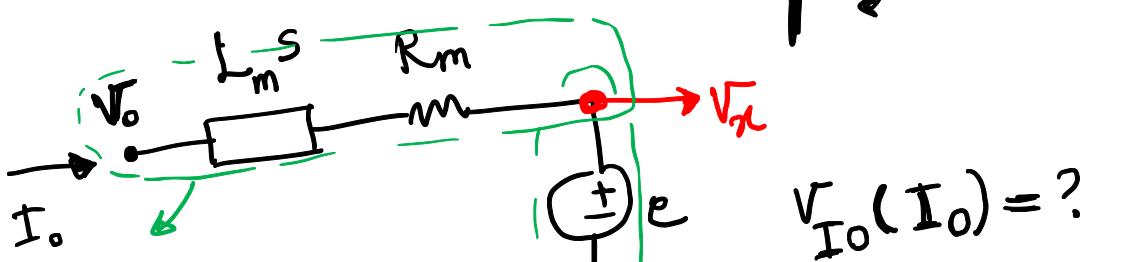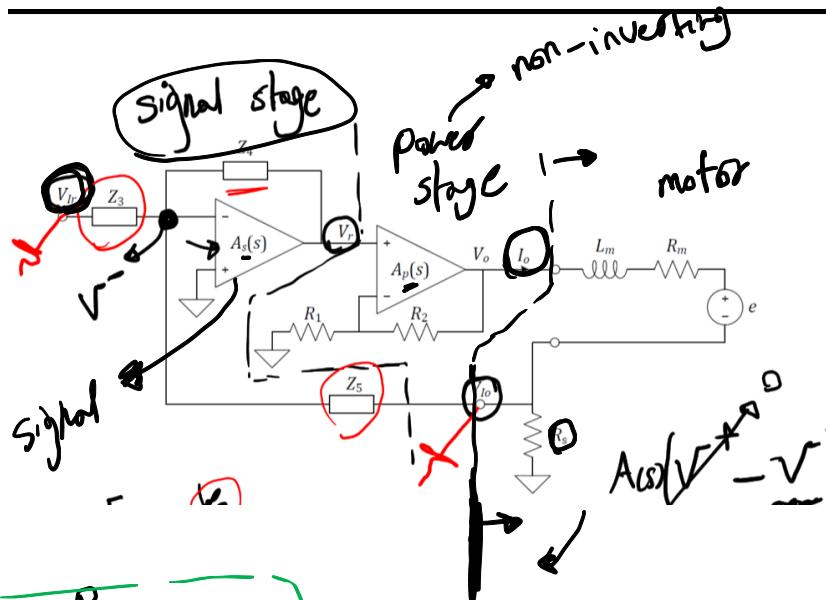
$$\begin{array}{ll} \checkmark V_r \\ \times V_{Ir} \\ \times V_{Io} \end{array}$$



$$I_o(V_o) = ?$$




$$\left\{ \begin{array}{l} \frac{V_o - V_n}{R_m + L_m s} = I_o \\ V_o - V_{I_o} = e \end{array} \right.$$

$$V_n - R_s I_o = e \Rightarrow V_n - R_s I_o = e \Rightarrow V_n = e + R_s I_o$$

$$(1) V_o - (e + R_s I_o) = I_o (R_m + L_m s)$$

$$V_o - e = I_o (R_m + L_m s + R_s)$$

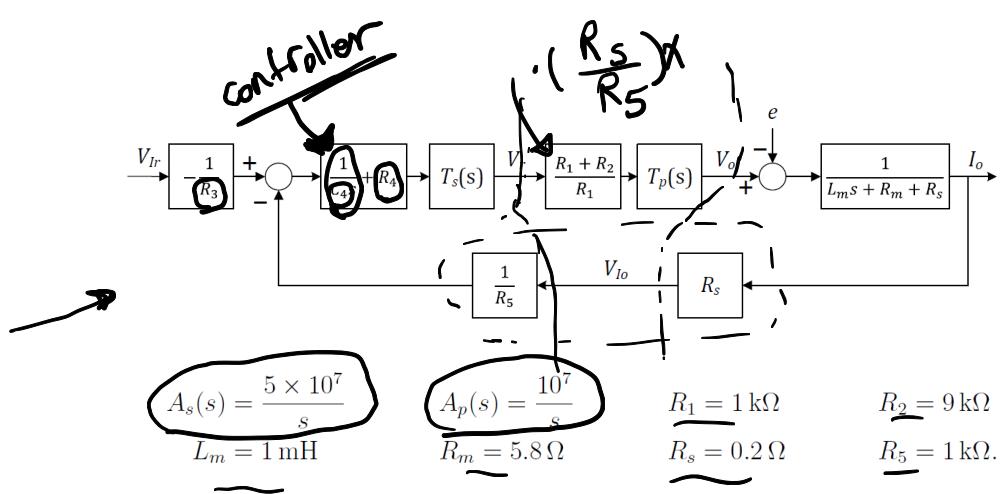
$$\Rightarrow I_o = \frac{V_o - e}{R_m + R_s + L_m s}$$




Select R_3 :

DAC $\sqrt{V_{Ir}}$

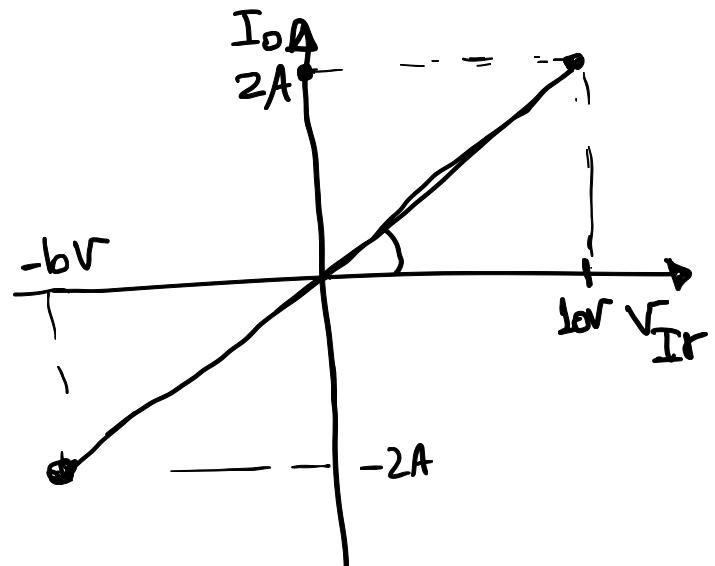DAC $\rightarrow \pm 10V \rightarrow \sqrt{V_{Ir}} \rightsquigarrow I_o \rightarrow \text{motor}$
 $\pm 2A$



$$|L(j\omega)| \xrightarrow[\omega=0]{} \infty$$

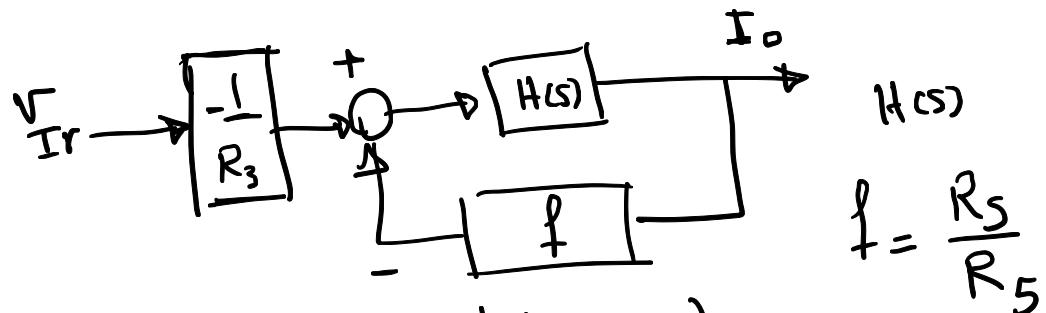

$$G = \frac{I_o}{\sqrt{V_{Ir}}} = \frac{\left(-\frac{1}{R_3}\right)(H(s))}{1 + f H(s)}$$

$$\left. \frac{I_o(j\omega)}{\sqrt{V_{Ir}(j\omega)}} \right|_{\omega=0} = \frac{-1/R_3}{f}$$


Selecting R_4 :

$$T_s(s) = 1$$


$$C_4 \rightarrow \infty$$

$$R_4 = ?$$

$$T_p(s) = \frac{L_p(s)}{1 + L_p(s)}$$

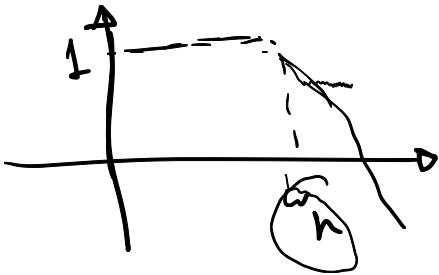

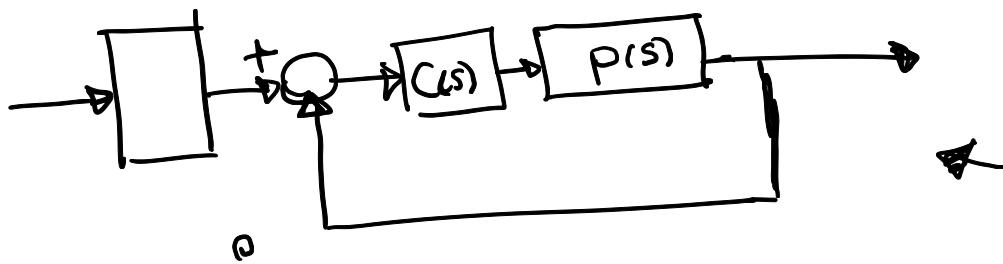- $L(s)$ have largest crossover frequency (ω_c) while $\phi_m > 90^\circ$



$$C(s) = \frac{1}{Q_4 s} + R_4$$

$$P(s) = \left(\frac{R_1 + R_2}{R_1} \right) \left(\frac{1}{L_m s + R_m + R_s} \right) \left(\frac{R_s}{R_5} \right) T_p(s) T_s(s)$$

$$T_p(s) = \frac{L_p(s)}{L_p(s) + 1}, \quad L_p(s) = f_p \frac{A(s)}{P(s)},$$

$$f_p = \frac{R_1}{R_1 + R_2}$$

$$\underline{L}(s) = \underline{C}(s) \underline{P}(s) = \underbrace{(R_4)}_{\text{phase}} \underbrace{P(s)}_{\text{phase}}$$

